



4

*In a major matter, no
details are small.*


French Proverb

The Processor

- 4.1 Introduction** 236
- 4.2 Logic Design Conventions** 240
- 4.3 Building a Datapath** 243
- 4.4 A Simple Implementation Scheme** 251
- 4.5 An Overview of Pipelining** 262
- 4.6 Pipelined Datapath and Control** 276
- 4.7 Data Hazards: Forwarding versus Stalling** 294
- 4.8 Control Hazards** 307
- 4.9 Exceptions** 315
- 4.10 Parallelism via Instructions** 321

 - 4.11 Real Stuff: The ARM Cortex-A53 and Intel Core i7 Pipelines** 334
 - 4.12 Going Faster: Instruction-Level Parallelism and Matrix Multiply** 342
 -  **4.13 Advanced Topic: An Introduction to Digital Design Using a Hardware Design Language to Describe and Model a Pipeline and More Pipelining Illustrations** 345
 - 4.14 Fallacies and Pitfalls** 345
 - 4.15 Concluding Remarks** 346
 -  **4.16 Historical Perspective and Further Reading** 347
 - 4.17 Exercises** 347
-

The Five Classic Components of a Computer



4.1 Introduction

[Chapter 1](#) explains that the performance of a computer is determined by three key factors: instruction count, clock cycle time, and *clock cycles per instruction* (CPI). [Chapter 2](#) explains that the compiler and the instruction set architecture determine the instruction count required for a given program. However, the implementation of the processor determines both the clock cycle time and the number of clock cycles per instruction. In this chapter, we construct the datapath and control unit for two different implementations of the RISC-V instruction set.

This chapter contains an explanation of the principles and techniques used in implementing a processor, starting with a highly abstract and simplified overview in this section. It is followed by a section that builds up a datapath and constructs a simple version of a processor sufficient to implement an instruction set like RISC-V. The bulk of the chapter covers a more realistic **pipelined** RISC-V implementation, followed by a section that develops the concepts necessary to implement more complex instruction sets, like the x86.

For the reader interested in understanding the high-level interpretation of instructions and its impact on program performance, this initial section and [Section 4.5](#) present the basic concepts of pipelining. Current trends are covered in [Section 4.10](#), and [Section 4.11](#) describes the recent Intel Core i7 and ARM Cortex-A53 architectures. [Section 4.12](#) shows how to use instruction-level parallelism to more than double the performance of the matrix multiply from [Section 3.9](#). These sections provide enough background to understand the pipeline concepts at a high level.

For the reader interested in understanding the processor and its performance in more depth, [Sections 4.3, 4.4, and 4.6](#) will be useful. Those interested in learning how to build a processor should also cover [Sections 4.2, 4.7–4.9](#). For readers with an interest in modern hardware design, [Section 4.13](#) describes how hardware design languages and CAD tools are used to implement hardware, and then how to use a hardware design language to describe a pipelined implementation. It also gives several more illustrations of how pipelining hardware executes.

A Basic RISC-V Implementation

We will be examining an implementation that includes a subset of the core RISC-V instruction set:

- The memory-reference instructions *load doubleword* (ld) and *store doubleword* (sd)
- The arithmetic-logical instructions *add*, *sub*, *and*, and *or*
- The conditional branch instruction *branch if equal* (beq)

This subset does not include all the integer instructions (for example, shift, multiply, and divide are missing), nor does it include any floating-point instructions.



However, it illustrates the key principles used in creating a datapath and designing the control. The implementation of the remaining instructions is similar.

In examining the implementation, we will have the opportunity to see how the instruction set architecture determines many aspects of the implementation, and how the choice of various implementation strategies affects the clock rate and CPI for the computer. Many of the key design principles introduced in [Chapter 1](#) can be illustrated by looking at the implementation, such as *Simplicity favors regularity*. In addition, most concepts used to implement the RISC-V subset in this chapter are the same basic ideas that are used to construct a broad spectrum of computers, from high-performance servers to general-purpose microprocessors to embedded processors.

An Overview of the Implementation

In [Chapter 2](#), we looked at the core RISC-V instructions, including the integer arithmetic-logical instructions, the memory-reference instructions, and the branch instructions. Much of what needs to be done to implement these instructions is the same, independent of the exact class of instruction. For every instruction, the first two steps are identical:

1. Send the *program counter* (PC) to the memory that contains the code and fetch the instruction from that memory.
2. Read one or two registers, using fields of the instruction to select the registers to read. For the `ld` instruction, we need to read only one register, but most other instructions require reading two registers.

After these two steps, the actions required to complete the instruction depend on the instruction class. Fortunately, for each of the three instruction classes (memory-reference, arithmetic-logical, and branches), the actions are largely the same, independent of the exact instruction. The simplicity and regularity of the RISC-V instruction set simplify the implementation by making the execution of many of the instruction classes similar.

For example, all instruction classes use the arithmetic-logical unit (ALU) after reading the registers. The memory-reference instructions use the ALU for an address calculation, the arithmetic-logical instructions for the operation execution, and conditional branches for the equality test. After using the ALU, the actions required to complete various instruction classes differ. A memory-reference instruction will need to access the memory either to read data for a load or write data for a store. An arithmetic-logical or load instruction must write the data from the ALU or memory back into a register. Lastly, for a conditional branch instruction, we may need to change the next instruction address based on the comparison; otherwise, the PC should be incremented by four to get the address of the subsequent instruction.

[Figure 4.1](#) shows the high-level view of a RISC-V implementation, focusing on the various functional units and their interconnection. Although this figure shows most of the flow of data through the processor, it omits two important aspects of instruction execution.

First, in several places, [Figure 4.1](#) shows data going to a particular unit as coming from two different sources. For example, the value written into the PC can come

from one of two adders, the data written into the register file can come from either the ALU or the data memory, and the second input to the ALU can come from a register or the immediate field of the instruction. In practice, these data lines cannot simply be wired together; we must add a logic element that chooses from among the multiple sources and steers one of those sources to its destination. This selection is commonly done with a device called a *multiplexor*, although this device might better be called a *data selector*. [Appendix A](#) describes the multiplexor, which selects from among several inputs based on the setting of its control lines. The control lines are set based primarily on information taken from the instruction being executed.

The second omission in [Figure 4.1](#) is that several of the units must be controlled depending on the type of instruction. For example, the data memory must read on a load and write on a store. The register file must be written only on a load or

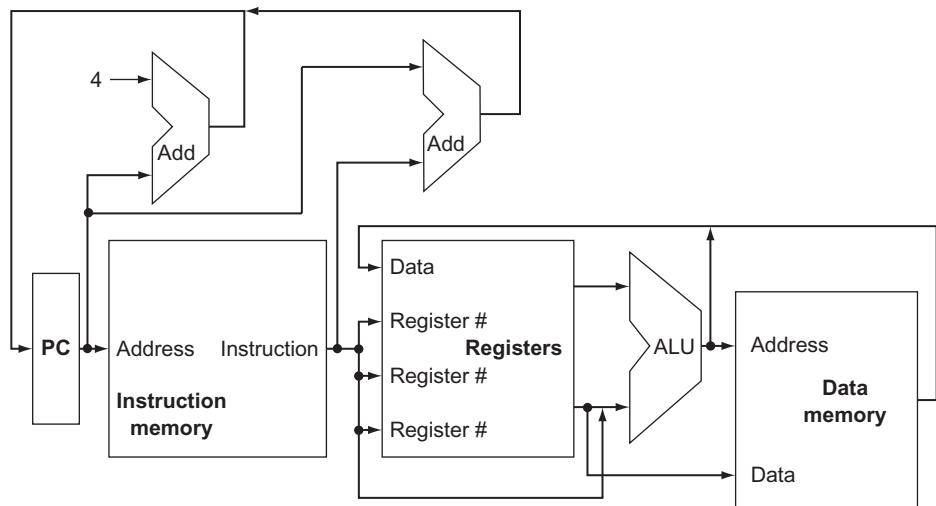


FIGURE 4.1 An abstract view of the implementation of the RISC-V subset showing the major functional units and the major connections between them. All instructions start by using the program counter to supply the instruction address to the instruction memory. After the instruction is fetched, the register operands used by an instruction are specified by fields of that instruction. Once the register operands have been fetched, they can be operated on to compute a memory address (for a load or store), to compute an arithmetic result (for an integer arithmetic-logical instruction), or an equality check (for a branch). If the instruction is an arithmetic-logical instruction, the result from the ALU must be written to a register. If the operation is a load or store, the ALU result is used as an address to either store a value from the registers or load a value from memory into the registers. The result from the ALU or memory is written back into the register file. Branches require the use of the ALU output to determine the next instruction address, which comes either from the adder (where the PC and branch offset are summed) or from an adder that increments the current PC by four. The thick lines interconnecting the functional units represent buses, which consist of multiple signals. The arrows are used to guide the reader in knowing how information flows. Since signal lines may cross, we explicitly show when crossing lines are connected by the presence of a dot where the lines cross.

an arithmetic-logical instruction. And, of course, the ALU must perform one of several operations. (Appendix A describes the detailed design of the ALU.) Like the multiplexors, control lines that are set based on various fields in the instruction direct these operations.

Figure 4.2 shows the datapath of Figure 4.1 with the three required multiplexors added, as well as control lines for the major functional units. A *control unit*, which has the instruction as an input, is used to determine how to set the control lines for the functional units and two of the multiplexors. The top multiplexor, which

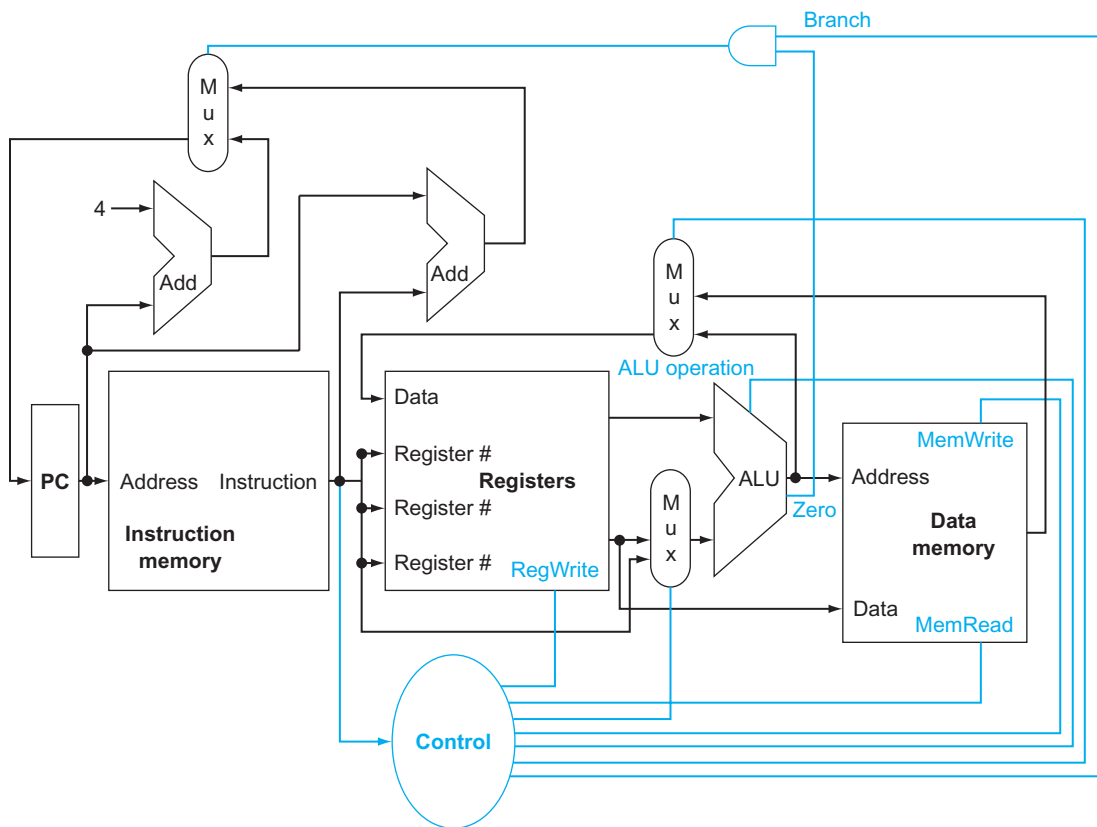


FIGURE 4.2 The basic implementation of the RISC-V subset, including the necessary multiplexors and control lines. The top multiplexor (“Mux”) controls what value replaces the PC ($PC + 4$ or the branch destination address); the multiplexor is controlled by the gate that “ANDs” together the Zero output of the ALU and a control signal that indicates that the instruction is a branch. The middle multiplexor, whose output returns to the register file, is used to steer the output of the ALU (in the case of an arithmetic-logical instruction) or the output of the data memory (in the case of a load) for writing into the register file. Finally, the bottom-most multiplexor is used to determine whether the second ALU input is from the registers (for an arithmetic-logical instruction or a branch) or from the offset field of the instruction (for a load or store). The added control lines are straightforward and determine the operation performed at the ALU, whether the data memory should read or write, and whether the registers should perform a write operation. The control lines are shown in color to make them easier to see.

determines whether $PC + 4$ or the branch destination address is written into the PC, is set based on the Zero output of the ALU, which is used to perform the comparison of a `beq` instruction. The regularity and simplicity of the RISC-V instruction set mean that a simple decoding process can be used to determine how to set the control lines.

In the remainder of the chapter, we refine this view to fill in the details, which requires that we add further functional units, increase the number of connections between units, and, of course, enhance a control unit to control what actions are taken for different instruction classes. Sections 4.3 and 4.4 describe a simple implementation that uses a single long clock cycle for every instruction and follows the general form of Figures 4.1 and 4.2. In this first design, every instruction begins execution on one clock edge and completes execution on the next clock edge.

While easier to understand, this approach is not practical, since the clock cycle must be severely stretched to accommodate the longest instruction. After designing the control for this simple computer, we will look at pipelined implementation with all its complexities, including exceptions.

Check Yourself

How many of the five classic components of a computer—shown on page 235—do Figures 4.1 and 4.2 include?

4.2

Logic Design Conventions

To discuss the design of a computer, we must decide how the hardware logic implementing the computer will operate and how the computer is clocked. This section reviews a few key ideas in digital logic that we will use extensively in this chapter. If you have little or no background in digital logic, you will find it helpful to read Appendix A before continuing.

The datapath elements in the RISC-V implementation consist of two different types of logic elements: elements that operate on data values and elements that contain state. The elements that operate on data values are all **combinational**, which means that their outputs depend only on the current inputs. Given the same input, a combinational element always produces the same output. The ALU shown in Figure 4.1 and discussed in Appendix A is an example of a combinational element. Given a set of inputs, it always produces the same output because it has no internal storage.

Other elements in the design are not combinational, but instead contain *state*. An element contains state if it has some internal storage. We call these elements **state elements** because, if we pulled the power plug on the computer, we could restart it accurately by loading the state elements with the values they contained before we pulled the plug. Furthermore, if we saved and restored the state elements, it would be as if the computer had never lost power. Thus, these state elements completely characterize the computer. In Figure 4.1, the instruction and data memories, as well as the registers, are all examples of state elements.

combinational element

An operational element, such as an AND gate or an ALU

state element A memory element, such as a register or a memory.

A state element has at least two inputs and one output. The required inputs are the data value to be written into the element and the clock, which determines when the data value is written. The output from a state element provides the value that was written in an earlier clock cycle. For example, one of the logically simplest state elements is a D-type flip-flop (see [Appendix A](#)), which has exactly these two inputs (a value and a clock) and one output. In addition to flip-flops, our RISC-V implementation uses two other types of state elements: memories and registers, both of which appear in [Figure 4.1](#). The clock is used to determine when the state element should be written; a state element can be read at any time.

Logic components that contain state are also called *sequential*, because their outputs depend on both their inputs and the contents of the internal state. For example, the output from the functional unit representing the registers depends both on the register numbers supplied and on what was written into the registers previously. [Appendix A](#) discusses the operation of both the combinational and sequential elements and their construction in more detail.

Clocking Methodology

A **clocking methodology** defines when signals can be read and when they can be written. It is important to specify the timing of reads and writes, because if a signal is written at the same time that it is read, the value of the read could correspond to the old value, the newly written value, or even some mix of the two! Computer designs cannot tolerate such unpredictability. A clocking methodology is designed to make hardware predictable.

For simplicity, we will assume an **edge-triggered clocking** methodology. An edge-triggered clocking methodology means that any values stored in a sequential logic element are updated only on a clock edge, which is a quick transition from low to high or vice versa (see [Figure 4.3](#)). Because only state elements can store a data value, any collection of combinational logic must have its inputs come from a set of state elements and its outputs written into a set of state elements. The inputs are values that were written in a previous clock cycle, while the outputs are values that can be used in a following clock cycle.

clocking

methodology The approach used to determine when data are valid and stable relative to the clock.

edge-triggered

clocking A clocking scheme in which all state changes occur on a clock edge.

 


FIGURE 4.3 Combinational logic, state elements, and the clock are closely related. In a synchronous digital system, the clock determines when elements with state will write values into internal storage. Any inputs to a state element must reach a stable value (that is, have reached a value from which they will not change until after the clock edge) before the active clock edge causes the state to be updated. All state elements in this chapter, including memory, are assumed positive edge-triggered; that is, they change on the rising clock edge.

control signal A signal used for multiplexor selection or for directing the operation of a functional unit; contrasts with a *data signal*, which contains information that is operated on by a functional unit.

asserted The signal is logically high or true.

deasserted The signal is logically low or false.

Figure 4.3 shows the two state elements surrounding a block of combinational logic, which operates in a single clock cycle: all signals must propagate from state element 1, through the combinational logic, and to state element 2 in the time of one clock cycle. The time necessary for the signals to reach state element 2 defines the length of the clock cycle.

For simplicity, we do not show a write **control signal** when a state element is written on every active clock edge. In contrast, if a state element is not updated on every clock, then an explicit write control signal is required. Both the clock signal and the write control signal are inputs, and the state element is changed only when the write control signal is asserted and a clock edge occurs.

We will use the word **asserted** to indicate a signal that is logically high and *assert* to specify that a signal should be driven logically high, and *deassert* or **deasserted** to represent logically low. We use the terms *assert* and *deassert* because when we implement hardware, at times 1 represents logically high and at times it can represent logically low.

An edge-triggered methodology allows us to read the contents of a register, send the value through some combinational logic, and write that register in the same clock cycle. Figure 4.4 gives a generic example. It doesn't matter whether we assume that all writes take place on the rising clock edge (from low to high) or on the falling clock edge (from high to low), since the inputs to the combinational logic block cannot change except on the chosen clock edge. In this book, we use the rising clock edge. With an edge-triggered timing methodology, there is *no* feedback within a single clock cycle, and the logic in Figure 4.4 works correctly. In Appendix A, we briefly discuss additional timing constraints (such as setup and hold times) as well as other timing methodologies.

For the 64-bit RISC-V architecture, nearly all of these state and logic elements will have inputs and outputs that are 64 bits wide, since that is the width of most of the data handled by the processor. We will make it clear whenever a unit has an input or output that is other than 64 bits in width. The figures will indicate *buses*, which are signals wider than 1 bit, with thicker lines. At times, we will want to combine several buses to form a wider bus; for example, we may want to obtain a 64-bit bus by combining two 32-bit buses. In such cases, labels on the bus lines

 


FIGURE 4.4 An edge-triggered methodology allows a state element to be read and written in the same clock cycle without creating a race that could lead to indeterminate data values. Of course, the clock cycle still must be long enough so that the input values are stable when the active clock edge occurs. Feedback cannot occur within one clock cycle because of the edge-triggered update of the state element. If feedback were possible, this design could not work properly. Our designs in this chapter and the next rely on the edge-triggered timing methodology and on structures like the one shown in this figure.

will make it clear that we are concatenating buses to form a wider bus. Arrows are also added to help clarify the direction of the flow of data between elements. Finally, **color** indicates a control signal contrary to a signal that carries data; this distinction will become clearer as we proceed through this chapter.

True or false: Because the register file is both read and written on the same clock cycle, any RISC-V datapath using edge-triggered writes must have more than one copy of the register file.

Check Yourself

Elaboration: There is also a 32-bit version of the RISC-V architecture, and, naturally enough, most paths in its implementation would be 32 bits wide.


4.3 Building a Datapath

A reasonable way to start a datapath design is to examine the major components required to execute each class of RISC-V instructions. Let's start at the top by looking at which **datapath elements** each instruction needs, and then work our way down through the levels of **abstraction**. When we show the datapath elements, we will also show their control signals. We use abstraction in this explanation, starting from the bottom up.

Figure 4.5a shows the first element we need: a memory unit to store the instructions of a program and supply instructions given an address. Figure 4.5b also shows the **program counter (PC)**, which as we saw in Chapter 2 is a register that holds the address of the current instruction. Lastly, we will need an adder to increment the PC to the address of the next instruction. This adder, which is combinational, can be built from the ALU described in detail in Appendix A simply by wiring the control lines so that the control always specifies an add operation. We will draw such an ALU with the label *Add*, as in Figure 4.5c, to indicate that it has been permanently made an adder and cannot perform the other ALU functions.

To execute any instruction, we must start by fetching the instruction from memory. To prepare for executing the next instruction, we must also increment the program counter so that it points at the next instruction, 4 bytes later. Figure 4.6 shows how to combine the three elements from Figure 4.5 to form a datapath that fetches instructions and increments the PC to obtain the address of the next sequential instruction.

Now let's consider the R-format instructions (see Figure 2.19 on page 120). They all read two registers, perform an ALU operation on the contents of the registers, and write the result to a register. We call these instructions either *R-type instructions* or *arithmetic-logical instructions* (since they perform arithmetic or logical operations). This instruction class includes *add*, *sub*, *and*, and *or*, which

 

ABSTRACTION

datapath element A unit used to operate on or hold data within a processor. In the RISC-V implementation, the datapath elements include the instruction and data memories, the register file, the ALU, and adders.

program counter (PC) The register containing the address of the instruction in the program being executed.

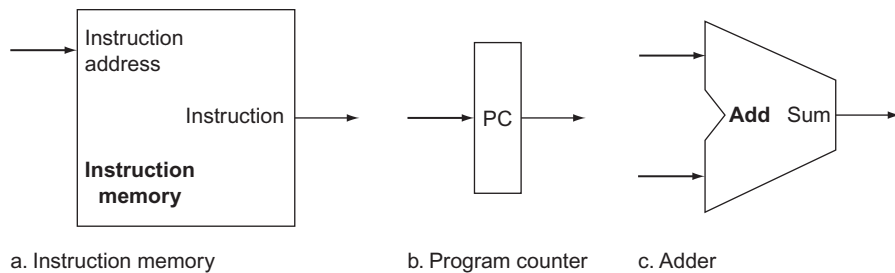


FIGURE 4.5 Two state elements are needed to store and access instructions, and an adder is needed to compute the next instruction address. The state elements are the instruction memory and the program counter. The instruction memory need only provide read access because the datapath does not write instructions. Since the instruction memory only reads, we treat it as combinational logic: the output at any time reflects the contents of the location specified by the address input, and no read control signal is needed. (We will need to write the instruction memory when we load the program; this is not hard to add, and we ignore it for simplicity.) The program counter is a 64-bit register that is written at the end of every clock cycle and thus does not need a write control signal. The adder is an ALU wired to always add its two 64-bit inputs and place the sum on its output.

were introduced in [Chapter 2](#). Recall that a typical instance of such an instruction is `add x1, x2, x3`, which reads `x2` and `x3` and writes the sum into `x1`.

The processor's 32 general-purpose registers are stored in a structure called a **register file**. A register file is a collection of registers in which any register can be read or written by specifying the number of the register in the file. The register file contains the register state of the computer. In addition, we will need an ALU to operate on the values read from the registers.

R-format instructions have three register operands, so we will need to read two data words from the register file and write one data word into the register file for each instruction. For each data word to be read from the registers, we need an input to the register file that specifies the *register number* to be read and an output from the register file that will carry the value that has been read from the registers. To write a data word, we will need two inputs: one to specify the register number to be written and one to supply the *data* to be written into the register. The register file always outputs the contents of whatever register numbers are on the Read register inputs. Writes, however, are controlled by the write control signal, which must be asserted for a write to occur at the clock edge. [Figure 4.7a](#) shows the result; we need a total of three inputs (two for register numbers and one for data) and two outputs (both for data). The register number inputs are 5 bits wide to specify one of 32 registers ($32 = 2^5$), whereas the data input and two data output buses are each 64 bits wide.

[Figure 4.7b](#) shows the ALU, which takes two 64-bit inputs and produces a 64-bit result, as well as a 1-bit signal if the result is 0. The 4-bit control signal of the ALU is described in detail in [Appendix A](#); we will review the ALU control shortly when we need to know how to set it.

register file A state element that consists of a set of registers that can be read and written by supplying a register number to be accessed.

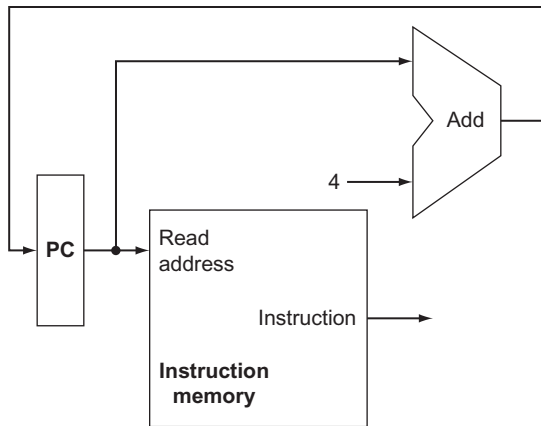


FIGURE 4.6 A portion of the datapath used for fetching instructions and incrementing the program counter. The fetched instruction is used by other parts of the datapath.

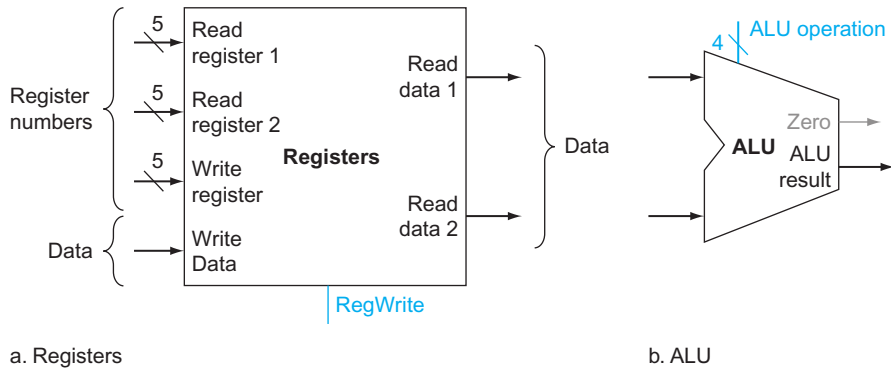


FIGURE 4.7 The two elements needed to implement R-format ALU operations are the register file and the ALU. The register file contains all the registers and has two read ports and one write port. The design of multiported register files is discussed in [Section A.8 of Appendix A](#). The register file always outputs the contents of the registers corresponding to the Read register inputs on the outputs; no other control inputs are needed. In contrast, a register write must be explicitly indicated by asserting the write control signal. Remember that writes are edge-triggered, so that all the write inputs (i.e., the value to be written, the register number, and the write control signal) must be valid at the clock edge. Since writes to the register file are edge-triggered, our design can legally read and write the same register within a clock cycle: the read will get the value written in an earlier clock cycle, while the value written will be available to a read in a subsequent clock cycle. The inputs carrying the register number to the register file are all 5 bits wide, whereas the lines carrying data values are 64 bits wide. The operation to be performed by the ALU is controlled with the ALU operation signal, which will be 4 bits wide, using the ALU designed in [Appendix A](#). We will use the Zero detection output of the ALU shortly to implement conditional branches.

Next, consider the RISC-V load register and store register instructions, which have the general form `ld x1, offset(x2)` or `sd x1, offset(x2)`. These instructions compute a memory address by adding the base register, which is `x2`, to the 12-bit signed offset field contained in the instruction. If the instruction is a store, the value to be stored must also be read from the register file where it resides in `x1`. If the instruction is a load, the value read from memory must be written into the register file in the specified register, which is `x1`. Thus, we will need both the register file and the ALU from [Figure 4.7](#).

In addition, we will need a unit to **sign-extend** the 12-bit offset field in the instruction to a 64-bit signed value, and a data memory unit to read from or write to. The data memory must be written on store instructions; hence, data memory has read and write control signals, an address input, and an input for the data to be written into memory. [Figure 4.8](#) shows these two elements.

The `beq` instruction has three operands, two registers that are compared for equality, and a 12-bit offset used to compute the **branch target address** relative to the branch instruction address. Its form is `beq x1, x2, offset`. To implement this instruction, we must compute the branch target address by adding the sign-extended offset field of the instruction to the PC. There are two details in the definition of branch instructions (see [Chapter 2](#)) to which we must pay attention:

- The instruction set architecture specifies that the base for the branch address calculation is the address of the branch instruction.
- The architecture also states that the offset field is shifted left 1 bit so that it is a half word offset; this shift increases the effective range of the offset field by a factor of 2.

To deal with the latter complication, we will need to shift the offset field by 1.

As well as computing the branch target address, we must also determine whether the next instruction is the instruction that follows sequentially or the instruction at the branch target address. When the condition is true (i.e., two operands are equal), the branch target address becomes the new PC, and we say that the **branch is taken**. If the operand is not zero, the incremented PC should replace the current PC (just as for any other normal instruction); in this case, we say that the **branch is not taken**.

Thus, the branch datapath must do two operations: compute the branch target address and test the register contents. (Branches also affect the instruction fetch portion of the datapath, as we will deal with shortly.) [Figure 4.9](#) shows the structure of the datapath segment that handles branches. To compute the branch target address, the branch datapath includes an immediate generation unit, from [Figure 4.8](#) and an adder. To perform the compare, we need to use the register file shown in [Figure 4.7a](#) to supply two register operands (although we will not need to write into the register file). In addition, the equality comparison can be done using the ALU we designed in [Appendix A](#). Since that ALU provides an output signal that indicates whether the result was 0, we can send both register operands to the ALU

sign-extend To increase the size of a data item by replicating the high-order sign bit of the original data item in the high-order bits of the larger, destination data item.

branch target address The address specified in a branch, which becomes the new program counter (PC) if the branch is taken. In the RISC-V architecture, the branch target is given by the sum of the offset field of the instruction and the address of the branch.

branch taken A branch where the branch condition is satisfied and the program counter (PC) becomes the branch target. All unconditional branches are taken branches.

branch not taken or (untaken branch) A branch where the branch condition is false and the program counter (PC) becomes the address of the instruction that sequentially follows the branch.

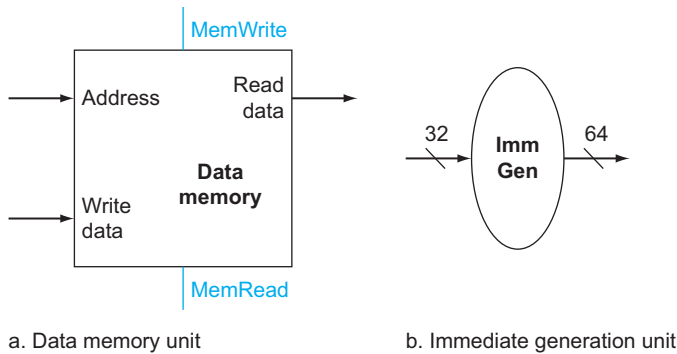


FIGURE 4.8 The two units needed to implement loads and stores, in addition to the register file and ALU of Figure 4.7, are the data memory unit and the immediate generation unit. The memory unit is a state element with inputs for the address and the write data, and a single output for the read result. There are separate read and write controls, although only one of these may be asserted on any given clock. The memory unit needs a read signal, since, unlike the register file, reading the value of an invalid address can cause problems, as we will see in Chapter 5. The immediate generation unit (ImmGen) has a 32-bit instruction as input that selects a 12-bit field for load, store, and branch if equal that is sign-extended into a 64-bit result appearing on the output (see Chapter 2). We assume the data memory is edge-triggered for writes. Standard memory chips actually have a write enable signal that is used for writes. Although the write enable is not edge-triggered, our edge-triggered design could easily be adapted to work with real memory chips. See Section A.8 of Appendix A for further discussion of how real memory chips work.

with the control set to subtract two values. If the Zero signal out of the ALU unit is asserted, we know that the register values are equal. Although the Zero output always signals if the result is 0, we will be using it only to implement the equality test of conditional branches. Later, we will show exactly how to connect the control signals of the ALU for use in the datapath.

The branch instruction operates by adding the PC with the 12 bits of the instruction shifted left by 1 bit. Simply concatenating 0 to the branch offset accomplishes this shift, as described in Chapter 2.

Creating a Single Datapath

Now that we have examined the datapath components needed for the individual instruction classes, we can combine them into a single datapath and add the control to complete the implementation. This simplest datapath will attempt to execute all instructions in one clock cycle. This design means that no datapath resource can be used more than once per instruction, so any element needed more than once must be duplicated. We therefore need a memory for instructions separate from one for data. Although some of the functional units will need to be duplicated, many of the elements can be shared by different instruction flows.

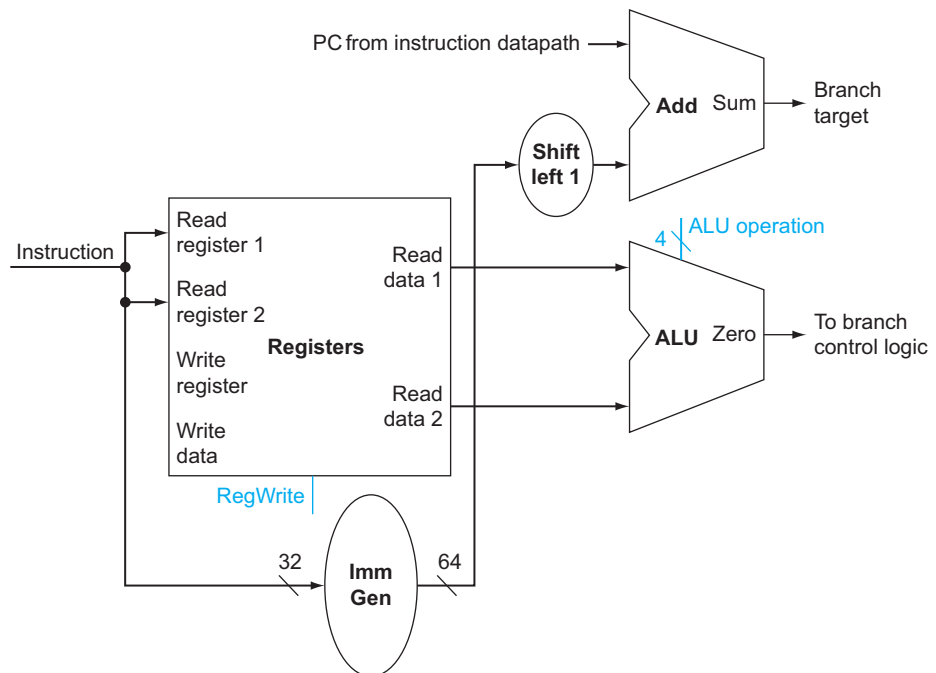


FIGURE 4.9 The datapath for a branch uses the ALU to evaluate the branch condition and a separate adder to compute the branch target as the sum of the PC and the sign-extended 12 bits of the instruction (the branch displacement), shifted left 1 bit. The unit labeled *Shift left 1* is simply a routing of the signals between input and output that adds 0_{two} to the low-order end of the sign-extended offset field; no actual shift hardware is needed, since the amount of the “shift” is constant. Since we know that the offset was sign-extended from 12 bits, the shift will throw away only “sign bits.” Control logic is used to decide whether the incremented PC or branch target should replace the PC, based on the Zero output of the ALU.

To share a datapath element between two different instruction classes, we may need to allow multiple connections to the input of an element, using a multiplexor and control signal to select among the multiple inputs.

EXAMPLE

Building a Datapath

The operations of arithmetic-logical (or R-type) instructions and the memory instructions datapath are quite similar. The key differences are the following:

- The arithmetic-logical instructions use the ALU, with the inputs coming from the two registers. The memory instructions can also use the ALU to do the address calculation, although the second input is the sign-extended 12-bit offset field from the instruction.

- The value stored into a destination register comes from the ALU (for an R-type instruction) or the memory (for a load).

Show how to build a datapath for the operational portion of the memory-reference and arithmetic-logical instructions that uses a single register file and a single ALU to handle both types of instructions, adding any necessary multiplexors.

To create a datapath with only a single register file and a single ALU, we must support two different sources for the second ALU input, as well as two different sources for the data stored into the register file. Thus, one multiplexor is placed at the ALU input and another at the data input to the register file. [Figure 4.10](#) shows the operational portion of the combined datapath.

ANSWER

Now we can combine all the pieces to make a simple datapath for the core RISC-V architecture by adding the datapath for instruction fetch (Figure 4.6), the datapath from R-type and memory instructions (Figure 4.10), and the datapath for branches (Figure 4.9). Figure 4.11 shows the datapath we obtain by composing the separate pieces. The branch instruction uses the main ALU to compare two register operands for equality, so we must keep the adder from Figure 4.9 for computing the branch target address. An additional multiplexor is required to select either the sequentially following instruction address ($PC + 4$) or the branch target address to be written into the PC.

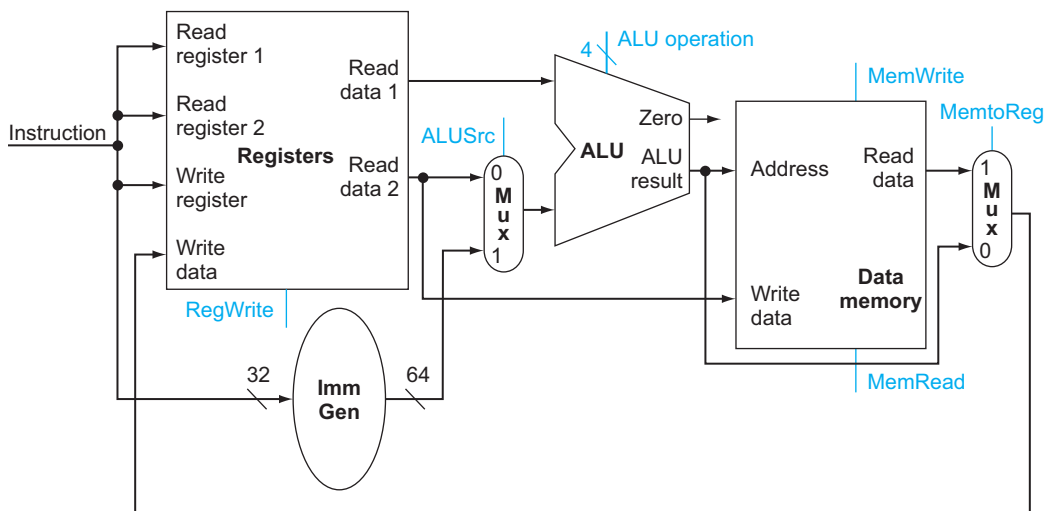


FIGURE 4.10 The datapath for the memory instructions and the R-type instructions. This example shows how a single datapath can be assembled from the pieces in Figures 4.7 and 4.8 by adding multiplexors. Two multiplexors are needed, as described in the example.

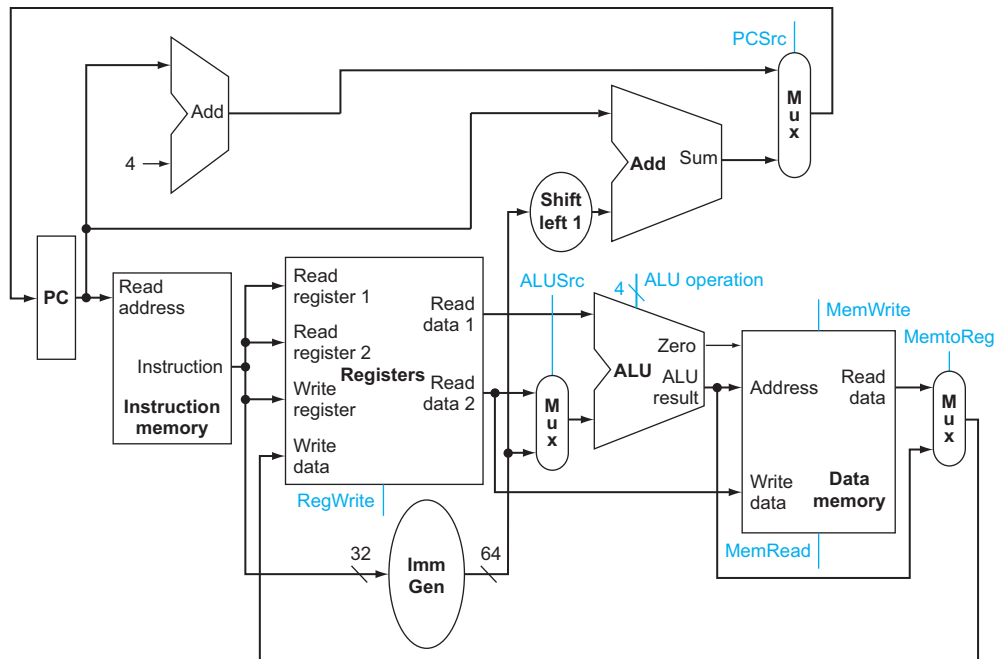


FIGURE 4.11 The simple datapath for the core RISC-V architecture combines the elements required by different instruction classes. The components come from Figures 4.6, 4.9, and 4.10. This datapath can execute the basic instructions (load-store register, ALU operations, and branches) in a single clock cycle. Just one additional multiplexor is needed to integrate branches.

Check Yourself

- I. Which of the following is correct for a load instruction? Refer to Figure 4.10.
 - a. MemtoReg should be set to cause the data from memory to be sent to the register file.
 - b. MemtoReg should be set to cause the correct register destination to be sent to the register file.
 - c. We do not care about the setting of MemtoReg for loads.
- II. The single-cycle datapath conceptually described in this section *must* have separate instruction and data memories, because
 - a. the formats of data and instructions are different in RISC-V, and hence different memories are needed;
 - b. having separate memories is less expensive;
 - c. the processor operates in one cycle and cannot use a (single-ported) memory for two different accesses within that cycle.

Now that we have completed this simple datapath, we can add the control unit. The control unit must be able to take inputs and generate a write signal for each state element, the selector control for each multiplexor, and the ALU control. The ALU control is different in a number of ways, and it will be useful to design it first before we design the rest of the control unit.

Elaboration: The immediate generation logic must choose between sign-extending a 12-bit field in instruction bits 31:20 for load instructions, bits 31:25 and 11:7 for store instructions, or bits 31, 7, 30:25, and 11:8 for the conditional branch. Since the input is all 32 bits of the instruction, it can use the opcode bits of the instruction to select the proper field. RISC-V opcode bit 6 happens to be 0 for data transfer instructions and 1 for conditional branches, and RISC-V opcode bit 5 happens to be 0 for load instructions and 1 for store instructions. Thus, bits 5 and 6 can control a 3:1 multiplexor inside the immediate generation logic that selects the appropriate 12-bit field for load, store, and conditional branch instructions.

4.4

A Simple Implementation Scheme

In this section, we look at what might be thought of as a simple implementation of our RISC-V subset. We build this simple implementation using the datapath of the last section and adding a simple control function. This simple implementation covers *load doubleword* (`ld`), *store doubleword* (`sd`), *branch if equal* (`beq`), and the arithmetic-logical instructions `add`, `sub`, `and`, and `or`.

The ALU Control

The RISC-V ALU in [Appendix A](#) defines the four following combinations of four control inputs:

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract

Depending on the instruction class, the ALU will need to perform one of these four functions. For load and store instructions, we use the ALU to compute the memory address by addition. For the R-type instructions, the ALU needs to perform one of the four actions (AND, OR, add, or subtract), depending on the value of the 7-bit `funct7` field (bits 31:25) and 3-bit `funct3` field (bits 14:12) in the instruction (see [Chapter 2](#)). For the conditional branch if equal instruction, the ALU subtracts two operands and tests to see if the result is 0.

We can generate the 4-bit ALU control input using a small control unit that has as inputs the funct7 and funct3 fields of the instruction and a 2-bit control field, which we call ALUOp. ALUOp indicates whether the operation to be performed should be add (00) for loads and stores, subtract and test if zero (01) for `beq`, or be determined by the operation encoded in the funct7 and funct3 fields (10). The output of the ALU control unit is a 4-bit signal that directly controls the ALU by generating one of the 4-bit combinations shown previously.

In [Figure 4.12](#), we show how to set the ALU control inputs based on the 2-bit ALUOp control, funct7, and funct3 fields. Later in this chapter, we will see how the ALUOp bits are generated from the main control unit.

This style of using multiple levels of decoding—that is, the main control unit generates the ALUOp bits, which then are used as input to the ALU control that generates the actual signals to control the ALU unit—is a common implementation technique. Using multiple levels of control can reduce the size of the main control unit. Using several smaller control units may also potentially reduce the latency of the control unit. Such optimizations are important, since the latency of the control unit is often a critical factor in determining the clock cycle time.

There are several different ways to implement the mapping from the 2-bit ALUOp field and the funct fields to the four ALU operation control bits. Because only a small number of the possible funct field values are of interest and funct fields are used only when the ALUOp bits equal 10, we can use a small piece of logic that recognizes the subset of possible values and generates the appropriate ALU control signals.

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract

Instruction opcode	ALUOp	Operation	Funct7 field	Funct3 field	Desired ALU action	ALU control input
ld	00	load doubleword	XXXXXXX	XXX	add	0010
sd	00	store doubleword	XXXXXXX	XXX	add	0010
beq	01	branch if equal	XXXXXXX	XXX	subtract	0110
R-type	10	add	0000000	000	add	0010
R-type	10	sub	0100000	000	subtract	0110
R-type	10	and	0000000	111	AND	0000
R-type	10	or	0000000	110	OR	0001

FIGURE 4.12 How the ALU control bits are set depends on the ALUOp control bits and the different opcodes for the R-type instruction. The instruction, listed in the first column, determines the setting of the ALUOp bits. All the encodings are shown in binary. Notice that when the ALUOp code is 00 or 01, the desired ALU action does not depend on the funct7 or funct3 fields; in this case, we say that we “don’t care” about the value of the opcode, and the bits are shown as Xs. When the ALUOp value is 10, then the funct7 and funct3 fields are used to set the ALU control input. See [Appendix A](#).

As a step in designing this logic, it is useful to create a *truth table* for the interesting combinations of funct fields and the ALUOp signals, as we've done in [Figure 4.13](#); this **truth table** shows how the 4-bit ALU control is set depending on these input fields. Since the full truth table is very large, and we don't care about the value of the ALU control for many of these input combinations, we show only the truth table entries for which the ALU control must have a specific value. Throughout this chapter, we will use this practice of showing only the truth table entries for outputs that must be asserted and not showing those that are all deasserted or don't care. (This practice has a disadvantage, which we discuss in [Section C.2](#) of [Appendix C](#).)

Because in many instances we do not care about the values of some of the inputs, and because we wish to keep the tables compact, we also include **don't-care terms**. A don't-care term in this truth table (represented by an X in an input column) indicates that the output does not depend on the value of the input corresponding to that column. For example, when the ALUOp bits are 00, as in the first row of [Figure 4.13](#), we always set the ALU control to 0010, independent of the funct fields. In this case, then, the funct inputs will be don't cares in this line of the truth table. Later, we will see examples of another type of don't-care term. If you are unfamiliar with the concept of don't-care terms, see [Appendix A](#) for more information.

Once the truth table has been constructed, it can be optimized and then turned into gates. This process is completely mechanical. Thus, rather than show the final steps here, we describe the process and the result in [Section C.2](#) of [Appendix C](#).

truth table From logic, a representation of a logical operation by listing all the values of the inputs and then in each case showing what the resulting outputs should be.

don't-care term An element of a logical function in which the output does not depend on the values of all the inputs. Don't-care terms may be specified in different ways.

Designing the Main Control Unit

Now that we have described how to design an ALU that uses the opcode and a 2-bit signal as its control inputs, we can return to looking at the rest of the control. To start this process, let's identify the fields of an instruction and the control lines that are needed for the datapath we constructed in [Figure 4.11](#). To understand how to connect the fields of an instruction to the datapath, it is useful to review

ALUOp		Funct7 field								Funct3 field			Operation
ALUOp1	ALUOp0	I[31]	I[30]	I[29]	I[28]	I[27]	I[26]	I[25]	I[14]	I[13]	I[12]		
0	0	X	X	X	X	X	X	X	X	X	X	0010	
X	1	X	X	X	X	X	X	X	X	X	X	0110	
1	X	0	0	0	0	0	0	0	0	0	0	0010	
1	X	0	1	0	0	0	0	0	0	0	0	0110	
1	X	0	0	0	0	0	0	0	1	1	1	0000	
1	X	0	0	0	0	0	0	0	1	1	0	0001	

FIGURE 4.13 The truth table for the 4 ALU control bits (called Operation). The inputs are the ALUOp and funct fields. Only the entries for which the ALU control is asserted are shown. Some don't-care entries have been added. For example, the ALUOp does not use the encoding 11, so the truth table can contain entries 1X and X1, rather than 10 and 01. While we show all 10 bits of funct fields, note that the only bits with different values for the four R-format instructions are bits 30, 14, 13, and 12. Thus, we only need these four funct field bits as input for ALU control instead of all 10.

Name (Bit position)	Fields					
	31:25	24:20	19:15	14:12	11:7	6:0
(a) R-type	funct7	rs2	rs1	funct3	rd	opcode
(b) I-type	immediate[11:0]		rs1	funct3	rd	opcode
(c) S-type	immed[11:5]	rs2	rs1	funct3	immed[4:0]	opcode
(d) SB-type	immed[12,10:5]	rs2	rs1	funct3	immed[4:1,11]	opcode

FIGURE 4.14 The four instruction classes (arithmetic, load, store, and conditional branch) use four different instruction formats. (a) Instruction format for R-type arithmetic instructions (opcode = 51_{ten}), which have three register operands: rs1, rs2, and rd. Fields rs1 and rd are sources, and rd is the destination. The ALU function is in the funct3 and funct7 fields and is decoded by the ALU control design in the previous section. The R-type instructions that we implement are `add`, `sub`, `and`, and `or`. (b) Instruction format for I-type load instructions (opcode = 3_{ten}). The register rs1 is the base register that is added to the 12-bit immediate field to form the memory address. Field rd is the destination register for the loaded value. (c) Instruction format for S-type store instructions (opcode = 35_{ten}). The register rs1 is the base register that is added to the 12-bit immediate field to form the memory address. (The immediate field is split into a 7-bit piece and a 5-bit piece.) Field rs2 is the source register whose value should be stored into memory. (d) Instruction format for SB-type conditional branch instructions (opcode = 99_{ten}). The registers rs1 and rs2 compared. The 12-bit immediate address field is sign-extended, shifted left 1 bit, and added to the PC to compute the branch target address.

the formats of the four instruction classes: arithmetic, load, store, and conditional branch instructions. [Figure 4.14](#) shows these formats.

There are several major observations about this instruction format that we will rely on:

opcode The field that denotes the operation and format of an instruction.

- The **opcode** field, which as we saw in [Chapter 2](#), is always in bits 6:0. Depending on the opcode, the funct3 field (bits 14:12) and funct7 field (bits 31:25) serve as an extended opcode field.
- The first register operand is always in bit positions 19:15 (rs1) for R-type instructions and branch instructions. This field also specifies the base register for load and store instructions.
- The second register operand is always in bit positions 24:20 (rs2) for R-type instructions and branch instructions. This field also specifies the register operand that gets copied to memory for store instructions.
- Another operand can also be a 12-bit offset for branch or load-store instructions.
- The destination register is always in bit positions 11:7 (rd) for R-type instructions and load instructions.

The first design principle from [Chapter 2](#)—*simplicity favors regularity*—pays off here in specifying control.

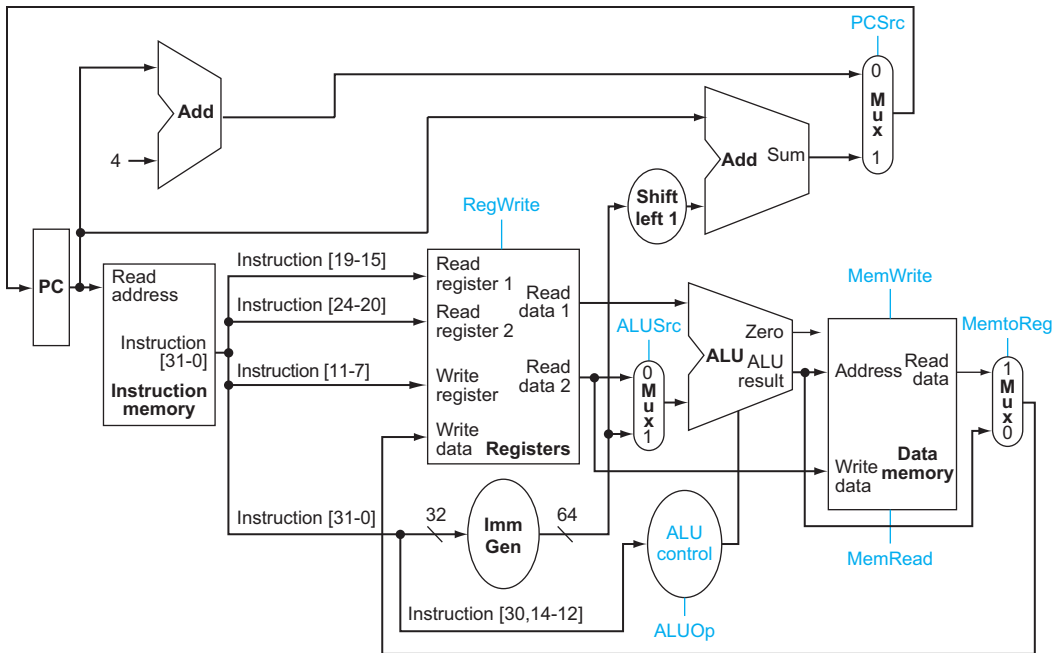


FIGURE 4.15 The datapath of Figure 4.11 with all necessary multiplexors and all control lines identified. The control lines are shown in color. The ALU control block has also been added, which depends on the funct3 field and part of the funct7 field. The PC does not require a write control, since it is written once at the end of every clock cycle; the branch control logic determines whether it is written with the incremented PC or the branch target address.

Using this information, we can add the instruction labels to the simple datapath. Figure 4.15 shows these additions plus the ALU control block, the write signals for state elements, the read signal for the data memory, and the control signals for the multiplexors. Since all the multiplexors have two inputs, they each require a single control line.

Figure 4.15 shows six single-bit control lines plus the 2-bit ALUOp control signal. We have already defined how the ALUOp control signal works, and it is useful to define what the six other control signals do informally before we determine how to set these control signals during instruction execution. Figure 4.16 describes the function of these six control lines.

Now that we have looked at the function of each of the control signals, we can look at how to set them. The control unit can set all but one of the control signals based solely on the opcode and funct fields of the instruction. The PCSrc control line is the exception. That control line should be asserted if the instruction is branch if equal (a decision that the control unit can make) *and* the Zero output of the ALU, which is used for the equality test, is asserted. To generate the PCSrc signal, we will need to AND together a signal from the control unit, which we call *Branch*, with the Zero signal out of the ALU.

Signal name	Effect when deasserted	Effect when asserted
RegWrite	None.	The register on the Write register input is written with the value on the Write data input.
ALUSrc	The second ALU operand comes from the second register file output (Read data 2).	The second ALU operand is the sign-extended, 12 bits of the instruction.
PCSrc	The PC is replaced by the output of the adder that computes the value of $PC + 4$.	The PC is replaced by the output of the adder that computes the branch target.
MemRead	None.	Data memory contents designated by the address input are put on the Read data output.
MemWrite	None.	Data memory contents designated by the address input are replaced by the value on the Write data input.
MemtoReg	The value fed to the register Write data input comes from the ALU.	The value fed to the register Write data input comes from the data memory.

FIGURE 4.16 The effect of each of the six control signals. When the 1-bit control to a two-way multiplexor is asserted, the multiplexor selects the input corresponding to 1. Otherwise, if the control is deasserted, the multiplexor selects the 0 input. Remember that the state elements all have the clock as an implicit input and that the clock is used in controlling writes. Gating the clock externally to a state element can create timing problems. (See [Appendix A](#) for further discussion of this problem.)

These eight control signals (six from [Figure 4.16](#) and two for $ALUOp$) can now be set based on the input signals to the control unit, which are the opcode bits 6:0. [Figure 4.17](#) shows the datapath with the control unit and the control signals.

Before we try to write a set of equations or a truth table for the control unit, it will be useful to try to define the control function informally. Because the setting of the control lines depends only on the opcode, we define whether each control signal should be 0, 1, or don't care (X) for each of the opcode values. [Figure 4.18](#) defines how the control signals should be set for each opcode; this information follows directly from [Figures 4.12, 4.16, and 4.17](#).

Operation of the Datapath

With the information contained in [Figures 4.16 and 4.18](#), we can design the control unit logic, but before we do that, let's look at how each instruction uses the datapath. In the next few figures, we show the flow of three different instruction classes through the datapath. The asserted control signals and active datapath elements are highlighted in each of these. Note that a multiplexor whose control is 0 has a definite action, even if its control line is not highlighted. Multiple-bit control signals are highlighted if any constituent signal is asserted.

[Figure 4.19](#) shows the operation of the datapath for an R-type instruction, such as `add x1, x2, x3`. Although everything occurs in one clock cycle, we can think

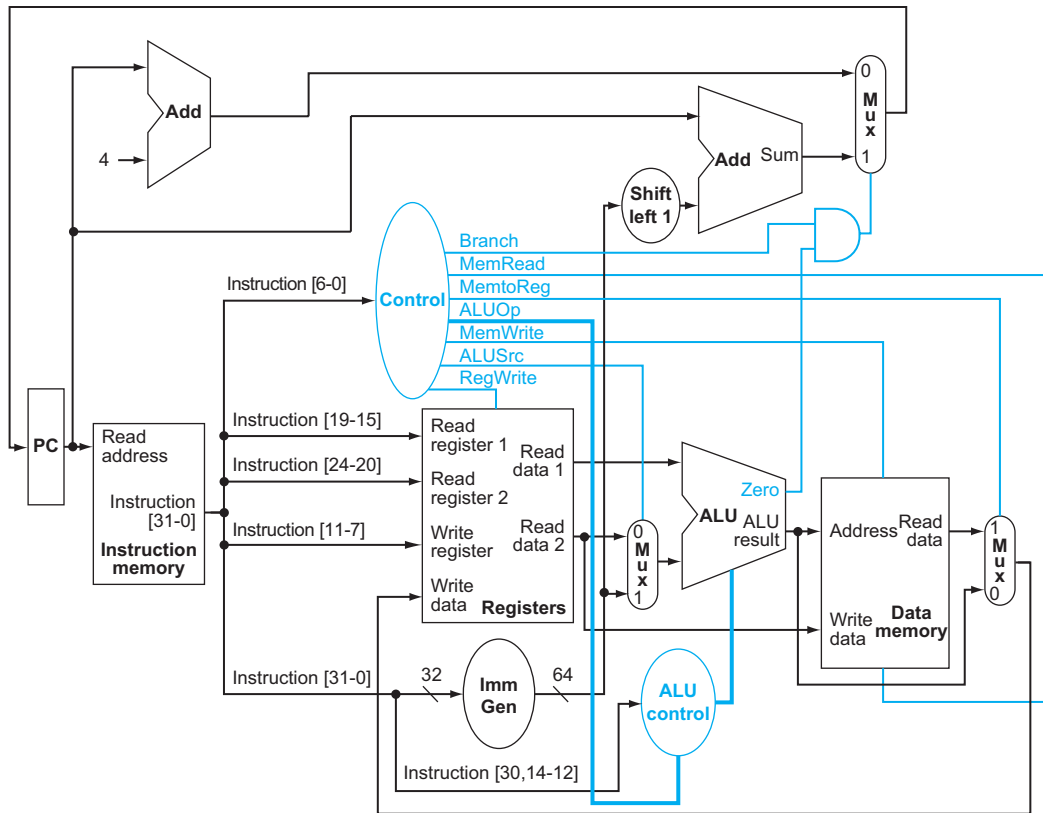


FIGURE 4.17 The simple datapath with the control unit. The input to the control unit is the 7-bit opcode field from the instruction. The outputs of the control unit consist of two 1-bit signals that are used to control multiplexors (ALUSrc and MemtoReg), three signals for controlling reads and writes in the register file and data memory (RegWrite, MemRead, and MemWrite), a 1-bit signal used in determining whether to possibly branch (Branch), and a 2-bit control signal for the ALU (ALUOp). An AND gate is used to combine the branch control signal and the Zero output from the ALU; the AND gate output controls the selection of the next PC. Notice that PCSrc is now a derived signal, rather than one coming directly from the control unit. Thus, we drop the signal name in subsequent figures.

of four steps to execute the instruction; these steps are ordered by the flow of information:

1. The instruction is fetched, and the PC is incremented.
2. Two registers, x_2 and x_3 , are read from the register file; also, the main control unit computes the setting of the control lines during this step.
3. The ALU operates on the data read from the register file, using portions of the opcode to generate the ALU function.
4. The result from the ALU is written into the destination register (x_1) in the register file.

Instruction	ALUSrc	Memto-Reg	Reg-Write	Mem-Read	Mem-Write	Branch	ALUOp1	ALUOp0
R-format	0	0	1	0	0	0	1	0
ld	1	1	1	1	0	0	0	0
sd	1	X	0	0	1	0	0	0
beq	0	X	0	0	0	1	0	1

FIGURE 4.18 The setting of the control lines is completely determined by the opcode fields of the instruction. The first row of the table corresponds to the R-format instructions (add, sub, and, and or). For all these instructions, the source register fields are rs1 and rs2, and the destination register field is rd; this defines how the signals ALUSrc is set. Furthermore, an R-type instruction writes a register (RegWrite = 1), but neither reads nor writes data memory. When the Branch control signal is 0, the PC is unconditionally replaced with PC + 4; otherwise, the PC is replaced by the branch target if the Zero output of the ALU is also high. The ALUOp field for R-type instructions is set to 10 to indicate that the ALU control should be generated from the funct fields. The second and third rows of this table give the control signal settings for ld and sd. These ALUSrc and ALUOp fields are set to perform the address calculation. The MemRead and MemWrite are set to perform the memory access. Finally, RegWrite is set for a load to cause the result to be stored in the rd register. The ALUOp field for branch is set for subtract (ALU control = 01), which is used to test for equality. Notice that the MemtoReg field is irrelevant when the RegWrite signal is 0: since the register is not being written, the value of the data on the register data write port is not used. Thus, the entry MemtoReg in the last two rows of the table is replaced with X for don't care. This type of don't care must be added by the designer, since it depends on knowledge of how the datapath works.

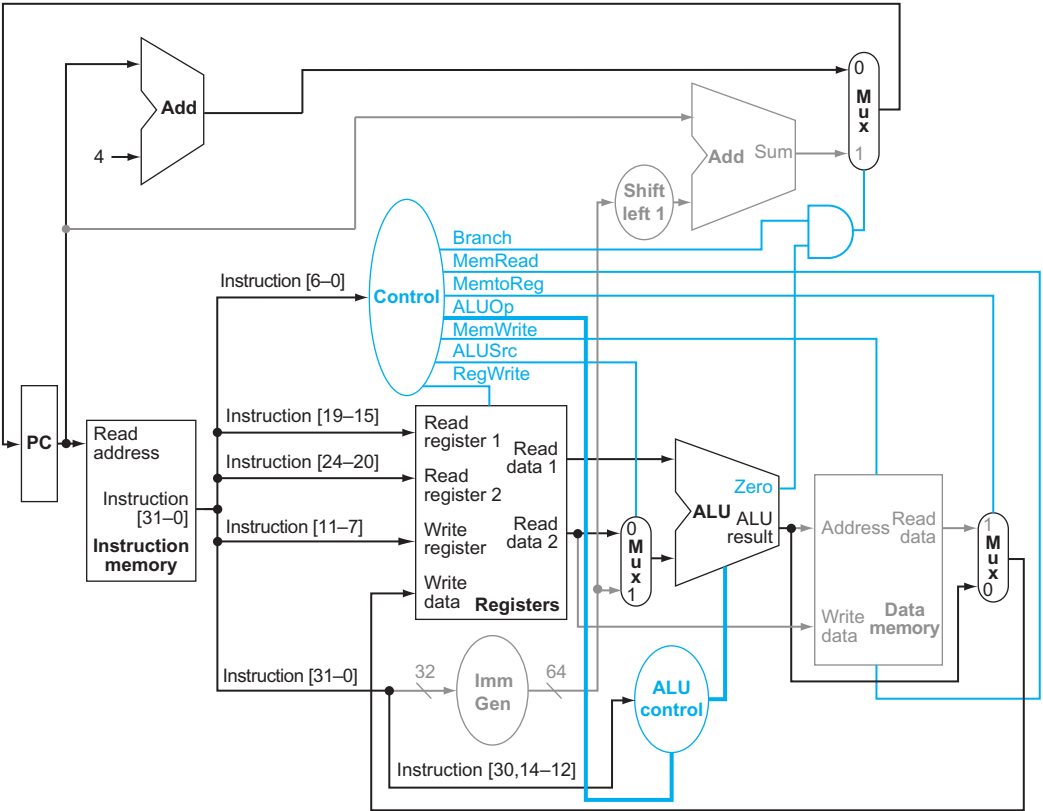


FIGURE 4.19 The datapath in operation for an R-type instruction, such as add x1, x2, x3. The control lines, datapath units, and connections that are active are highlighted.

Similarly, we can illustrate the execution of a load register, such as

```
ld x1, offset(x2)
```

in a style similar to Figure 4.19. Figure 4.20 shows the active functional units and asserted control lines for a load. We can think of a load instruction as operating in five steps (similar to how the R-type executed in four):

1. An instruction is fetched from the instruction memory, and the PC is incremented.
2. A register (x2) value is read from the register file.
3. The ALU computes the sum of the value read from the register file and the sign-extended 12 bits of the instruction (offset).
4. The sum from the ALU is used as the address for the data memory.
5. The data from the memory unit is written into the register file (x1).

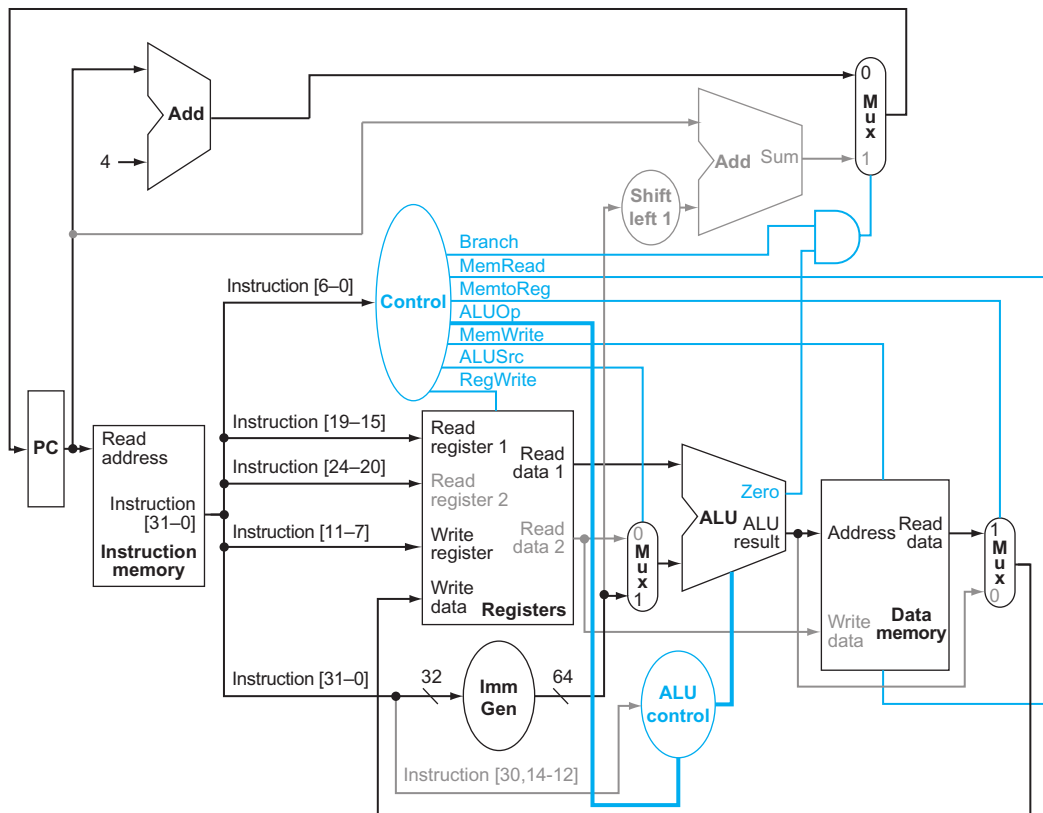


FIGURE 4.20 The datapath in operation for a load instruction. The control lines, datapath units, and connections that are active are highlighted. A store instruction would operate very similarly. The main difference would be that the memory control would indicate a write rather than a read, the second register value read would be used for the data to store, and the operation of writing the data memory value to the register file would not occur.

Finally, we can show the operation of the branch-if-equal instruction, such as `beq x1, x2, offset`, in the same fashion. It operates much like an R-format instruction, but the ALU output is used to determine whether the PC is written with $PC + 4$ or the branch target address. Figure 4.21 shows the four steps in execution:

1. An instruction is fetched from the instruction memory, and the PC is incremented.
2. Two registers, `x1` and `x2`, are read from the register file.
3. The ALU subtracts one data value from the other data value, both read from the register file. The value of PC is added to the sign-extended, 12 bits of the instruction (`offset`) left shifted by one; the result is the branch target address.
4. The Zero status information from the ALU is used to decide which adder result to store in the PC.

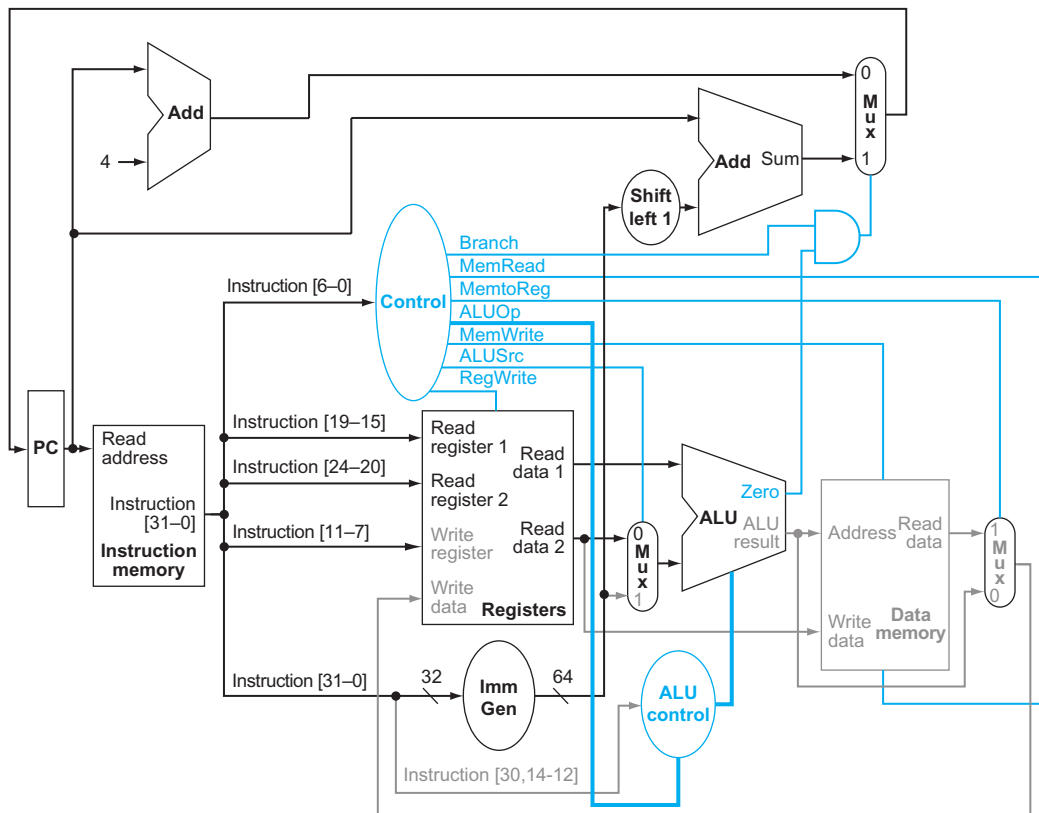


FIGURE 4.21 The datapath in operation for a branch-if-equal instruction. The control lines, datapath units, and connections that are active are highlighted. After using the register file and ALU to perform the compare, the Zero output is used to select the next program counter from between the two candidates.

Finalizing Control

Now that we have seen how the instructions operate in steps, let's continue with the control implementation. The control function can be precisely defined using the contents of Figure 4.18. The outputs are the control lines, and the inputs are the opcode bits. Thus, we can create a truth table for each of the outputs based on the binary encoding of the opcodes.

Figure 4.22 defines the logic in the control unit as one large truth table that combines all the outputs and that uses the opcode bits as inputs. It completely specifies the control function, and we can implement it directly in gates in an automated fashion. We show this final step in Section C.2 in [Appendix C](#).

Why a Single-Cycle Implementation is not Used Today

Although the single-cycle design will work correctly, it is too inefficient to be used in modern designs. To see why this is so, notice that the clock cycle must have the same length for every instruction in this single-cycle design. Of course, the longest possible path in the processor determines the clock cycle. This path is most likely a load instruction, which uses five functional units in series: the instruction memory,

Input or output	Signal name	R-format	ld	sd	beq
Inputs	I[6]	0	0	0	1
	I[5]	1	0	1	1
	I[4]	1	0	0	0
	I[3]	0	0	0	0
	I[2]	0	0	0	0
	I[1]	1	1	1	1
	I[0]	1	1	1	1
Outputs	ALUSrc	0	1	1	0
	MemtoReg	0	1	X	X
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

FIGURE 4.22 The control function for the simple single-cycle implementation is completely specified by this truth table. The top half of the table gives the combinations of input signals that correspond to the four instruction classes, one per column, that determine the control output settings. The bottom portion of the table gives the outputs for each of the four opcodes. Thus, the output RegWrite is asserted for two different combinations of the inputs. If we consider only the four opcodes shown in this table, then we can simplify the truth table by using don't cares in the input portion. For example, we can detect an R-format instruction with the expression $Op4 \cdot Op5$, since this is sufficient to distinguish the R-format instructions from ld, sd, and beq. We do not take advantage of this simplification, since the rest of the RISC-V opcodes are used in a full implementation.

the register file, the ALU, the data memory, and the register file. Although the CPI is 1 (see [Chapter 1](#)), the overall performance of a single-cycle implementation is likely to be poor, since the clock cycle is too long.

The penalty for using the single-cycle design with a fixed clock cycle is significant, but might be considered acceptable for this small instruction set. Historically, early computers with very simple instruction sets did use this implementation technique. However, if we tried to implement the floating-point unit or an instruction set with more complex instructions, this single-cycle design wouldn't work well at all.

Because we must assume that the clock cycle is equal to the worst-case delay for all instructions, it's useless to try implementation techniques that reduce the delay of the common case but do not improve the worst-case cycle time. A single-cycle implementation thus violates the great idea from [Chapter 1](#) of making the **common case fast**.

In next section, we'll look at another implementation technique, called **pipelining**, that uses a datapath very similar to the single-cycle datapath but is much more efficient by having a much higher throughput. Pipelining improves efficiency by executing multiple instructions simultaneously.



COMMON CASE FAST

Check Yourself

Look at the control signals in [Figure 4.22](#). Can you combine any together? Can any control signal output in the figure be replaced by the inverse of another? (Hint: take into account the don't cares.) If so, can you use one signal for the other without adding an inverter?

4.5

An Overview of Pipelining

Never waste time.
American proverb


pipelining An implementation technique in which multiple instructions are overlapped in execution, much like an assembly line.

Pipelining is an implementation technique in which multiple instructions are overlapped in execution. Today, **pipelining** is nearly universal.

This section relies heavily on one analogy to give an overview of the pipelining terms and issues. If you are interested in just the big picture, you should concentrate on this section and then skip to [Sections 4.10 and 4.11](#) to see an introduction to the advanced pipelining techniques used in recent processors such as the Intel Core i7 and ARM Cortex-A53. If you are curious about exploring the anatomy of a pipelined computer, this section is a good introduction to [Sections 4.6 through 4.9](#).

Anyone who has done a lot of laundry has intuitively used pipelining. The *non-pipelined* approach to laundry would be as follows:

 1. Place one dirty load of clothes in the washer.
2. When the washer is finished, place the wet load in the dryer.
3. When the dryer is finished, place the dry load on a table and fold.
4. When folding is finished, ask your roommate to put the clothes away.



PIPELINING

When your roommate is done, start over with the next dirty load.

The *pipelined* approach takes much less time, as Figure 4.23 shows. As soon as the washer is finished with the first load and placed in the dryer, you load the washer with the second dirty load. When the first load is dry, you place it on the table to start folding, move the wet load to the dryer, and put the next dirty load into the washer. Next, you have your roommate put the first load away, you start folding the second load, the dryer has the third load, and you put the fourth load into the washer. At this point all steps—called *stages* in pipelining—are operating concurrently. As long as we have separate resources for each stage, we can pipeline the tasks.

The pipelining paradox is that the time from placing a single dirty sock in the washer until it is dried, folded, and put away is not shorter for pipelining; the reason pipelining is faster for many loads is that everything is working in parallel, so more loads are finished per hour. Pipelining improves *throughput* of our laundry system. Hence, pipelining would not decrease the time to complete one load of laundry,

 


FIGURE 4.23 The laundry analogy for pipelining. Ann, Brian, Cathy, and Don each have dirty clothes to be washed, dried, folded, and put away. The washer, dryer, “folder,” and “storer” each take 30 minutes for their task. Sequential laundry takes 8 hours for four loads of washing, while pipelined laundry takes just 3.5 hours. We show the pipeline stage of different loads over time by showing copies of the four resources on this two-dimensional time line, but we really have just one of each resource.

but when we have many loads of laundry to do, the improvement in throughput decreases the total time to complete the work.

If all the stages take about the same amount of time and there is enough work to do, then the speed-up due to pipelining is equal to the number of stages in the pipeline, in this case four: washing, drying, folding, and putting away. Therefore, pipelined laundry is potentially four times faster than nonpipelined: 20 loads would take about five times as long as one load, while 20 loads of sequential laundry takes 20 times as long as one load. It's only 2.3 times faster in [Figure 4.23](#), because we only show four loads. Notice that at the beginning and end of the workload in the pipelined version in [Figure 4.23](#), the pipeline is not completely full; this start-up and wind-down affects performance when the number of tasks is not large compared to the number of stages in the pipeline. If the number of loads is much larger than four, then the stages will be full most of the time and the increase in throughput will be very close to four.

The same principles apply to processors where we pipeline instruction execution. RISC-V instructions classically take five steps:

1. Fetch instruction from memory.
2. Read registers and decode the instruction.
3. Execute the operation or calculate an address.
4. Access an operand in data memory (if necessary).
5. Write the result into a register (if necessary).

Hence, the RISC-V pipeline we explore in this chapter has five stages. The following example shows that pipelining speeds up instruction execution just as it speeds up the laundry.

EXAMPLE

Single-Cycle versus Pipelined Performance

To make this discussion concrete, let's create a pipeline. In this example, and in the rest of this chapter, we limit our attention to seven instructions: load doubleword (`ld`), store doubleword (`sd`), add (`add`), subtract (`sub`), AND (`and`), OR (`or`), and branch if equal (`beq`).

Contrast the average time between instructions of a single-cycle implementation, in which all instructions take one clock cycle, to a pipelined implementation. Assume that the operation times for the major functional units in this example are 200ps for memory access for instructions or data, 200ps for ALU operation, and 100ps for register file read or write. In the

single-cycle model, every instruction takes exactly one clock cycle, so the clock cycle must be stretched to accommodate the slowest instruction.

Figure 4.24 shows the time required for each of the seven instructions. The single-cycle design must allow for the slowest instruction—in Figure 4.24 it is `ld`—so the time required for every instruction is 800 ps. Similarly to Figure 4.23, Figure 4.25 compares nonpipelined and pipelined execution of three load register instructions. Thus, the time between the first and fourth instructions in the nonpipelined design is 3×800 ps or 2400 ps.

All the pipeline stages take a single clock cycle, so the clock cycle must be long enough to accommodate the slowest operation. Just as the single-cycle design must take the worst-case clock cycle of 800 ps, even though some instructions can be as fast as 500 ps, the pipelined execution clock cycle must have the worst-case clock cycle of 200 ps, even though some stages take only 100 ps. Pipelining still offers a fourfold performance improvement: the time between the first and fourth instructions is 3×200 ps or 600 ps.

We can turn the pipelining speed-up discussion above into a formula. If the stages are perfectly balanced, then the time between instructions on the pipelined processor—assuming ideal conditions—is equal to

$$\text{Time between instructions}_{\text{pipelined}} = \frac{\text{Time between instructions}_{\text{nonpipelined}}}{\text{Number of pipe stages}}$$

Under ideal conditions and with a large number of instructions, the speed-up from pipelining is approximately equal to the number of pipe stages; a five-stage pipeline is nearly five times faster.

The formula suggests that a five-stage pipeline should offer nearly a fivefold improvement over the 800 ps nonpipelined time, or a 160 ps clock cycle. The

ANSWER

Instruction class	Instruction fetch	Register read	ALU operation	Data access	Register write	Total time
Load doubleword (<code>ld</code>)	200 ps	100 ps	200 ps	200 ps	100 ps	800 ps
Store doubleword (<code>sd</code>)	200 ps	100 ps	200 ps	200 ps		700 ps
R-format (<code>add</code> , <code>sub</code> , <code>and</code> , <code>or</code>)	200 ps	100 ps	200 ps		100 ps	600 ps
Branch (<code>beq</code>)	200 ps	100 ps	200 ps			500 ps

FIGURE 4.24 Total time for each instruction calculated from the time for each component.

This calculation assumes that the multiplexors, control unit, PC accesses, and sign extension unit have no delay.

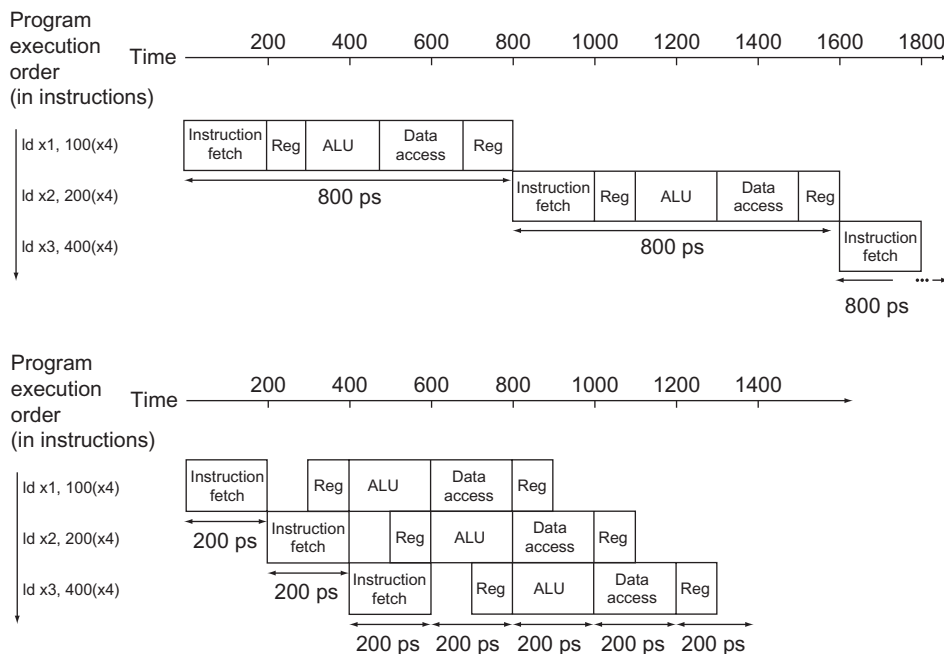


FIGURE 4.25 Single-cycle, nonpipelined execution (top) versus pipelined execution (bottom). Both use the same hardware components, whose time is listed in Figure 4.24. In this case, we see a fourfold speed-up on average time between instructions, from 800 ps down to 200 ps. Compare this figure to Figure 4.23. For the laundry, we assumed all stages were equal. If the dryer were slowest, then the dryer stage would set the stage time. The pipeline stage times of a computer are also limited by the slowest resource, either the ALU operation or the memory access. We assume the write to the register file occurs in the first half of the clock cycle and the read from the register file occurs in the second half. We use this assumption throughout this chapter.

example shows, however, that the stages may be imperfectly balanced. Moreover, pipelining involves some overhead, the source of which will be clearer shortly. Thus, the time per instruction in the pipelined processor will exceed the minimum possible, and speed-up will be less than the number of pipeline stages.

However, even our claim of fourfold improvement for our example is not reflected in the total execution time for the three instructions: it's 1400 ps versus 2400 ps. Of course, this is because the number of instructions is not large. What would happen if we increased the number of instructions? We could extend the previous figures to 1,000,003 instructions. We would add 1,000,000 instructions in the pipelined example; each instruction adds 200 ps to the total execution time. The total execution time would be $1,000,000 \times 200 \text{ ps} + 1400 \text{ ps}$, or 200,001,400 ps. In the nonpipelined example, we would add 1,000,000 instructions, each taking 800 ps, so total execution time would be $1,000,000 \times 800 \text{ ps} + 2400 \text{ ps}$, or 800,002,400 ps. Under these

conditions, the ratio of total execution times for real programs on nonpipelined to pipelined processors is close to the ratio of times between instructions:

$$\frac{800,002,400 \text{ ps}}{200,001,400 \text{ ps}} \approx \frac{800 \text{ ps}}{200 \text{ ps}} \approx 4.00$$

Pipelining improves performance by *increasing instruction throughput*, in contrast to *decreasing the execution time of an individual instruction*, but instruction throughput is the important metric because real programs execute billions of instructions.

Designing Instruction Sets for Pipelining

Even with this simple explanation of pipelining, we can get insight into the design of the RISC-V instruction set, which was designed for pipelined execution.

First, all RISC-V instructions are the same length. This restriction makes it much easier to fetch instructions in the first pipeline stage and to decode them in the second stage. In an instruction set like the x86, where instructions vary from 1 byte to 15 bytes, pipelining is considerably more challenging. Modern implementations of the x86 architecture actually translate x86 instructions into simple operations that look like RISC-V instructions and then pipeline the simple operations rather than the native x86 instructions! (See [Section 4.10](#).)

Second, RISC-V has just a few instruction formats, with the source and destination register fields being located in the same place in each instruction.

Third, memory operands only appear in loads or stores in RISC-V. This restriction means we can use the execute stage to calculate the memory address and then access memory in the following stage. If we could operate on the operands in memory, as in the x86, stages 3 and 4 would expand to an address stage, memory stage, and then execute stage. We will shortly see the downside of longer pipelines.

Pipeline Hazards

There are situations in pipelining when the next instruction cannot execute in the following clock cycle. These events are called *hazards*, and there are three different types.

Structural Hazard

The first hazard is called a **structural hazard**. It means that the hardware cannot support the combination of instructions that we want to execute in the same clock cycle. A structural hazard in the laundry room would occur if we used a washer-dryer combination instead of a separate washer and dryer, or if our roommate was busy doing something else and wouldn't put clothes away. Our carefully scheduled pipeline plans would then be foiled.

structural hazard When a planned instruction cannot execute in the proper clock cycle because the hardware does not support the combination of instructions that are set to execute.

As we said above, the RISC-V instruction set was designed to be pipelined, making it fairly easy for designers to avoid structural hazards when designing a pipeline. Suppose, however, that we had a single memory instead of two memories. If the pipeline in Figure 4.25 had a fourth instruction, we would see that in the same clock cycle, the first instruction is accessing data from memory while the fourth instruction is fetching an instruction from that same memory. Without two memories, our pipeline could have a structural hazard.

Data Hazards

data hazard Also called a **pipeline data hazard**. When a planned instruction cannot execute in the proper clock cycle because data that are needed to execute the instruction are not yet available.

Data hazards occur when the pipeline must be stalled because one step must wait for another to complete. Suppose you found a sock at the folding station for which no match existed. One possible strategy is to run down to your room and search through your clothes bureau to see if you can find the match. Obviously, while you are doing the search, loads that have completed drying are ready to fold and those that have finished washing are ready to dry.

In a computer pipeline, data hazards arise from the dependence of one instruction on an earlier one that is still in the pipeline (a relationship that does not really exist when doing laundry). For example, suppose we have an add instruction followed immediately by a subtract instruction that uses that sum ($\times 19$):

```
add  x19, x0, x1
sub  x2, x19, x3
```

Without intervention, a data hazard could severely stall the pipeline. The add instruction doesn't write its result until the fifth stage, meaning that we would have to waste three clock cycles in the pipeline.

Although we could try to rely on compilers to remove all such hazards, the results would not be satisfactory. These dependences happen just too often and the delay is far too long to expect the compiler to rescue us from this dilemma.

The primary solution is based on the observation that we don't need to wait for the instruction to complete before trying to resolve the data hazard. For the code sequence above, as soon as the ALU creates the sum for the add, we can supply it as an input for the subtract. Adding extra hardware to retrieve the missing item early from the internal resources is called **forwarding** or **bypassing**.

forwarding Also called **bypassing**. A method of resolving a data hazard by retrieving the missing data element from internal buffers rather than waiting for it to arrive from programmer-visible registers or memory.

EXAMPLE

Forwarding with Two Instructions

For the two instructions above, show what pipeline stages would be connected by forwarding. Use the drawing in Figure 4.26 to represent the datapath during the five stages of the pipeline. Align a copy of the datapath for each instruction, similar to the laundry pipeline in Figure 4.23.

 


FIGURE 4.26 Graphical representation of the instruction pipeline, similar in spirit to the laundry pipeline in Figure 4.23. Here we use symbols representing the physical resources with the abbreviations for pipeline stages used throughout the chapter. The symbols for the five stages: *IF* for the instruction fetch stage, with the box representing instruction memory; *ID* for the instruction decode/register file read stage, with the drawing showing the register file being read; *EX* for the execution stage, with the drawing representing the ALU; *MEM* for the memory access stage, with the box representing data memory; and *WB* for the write-back stage, with the drawing showing the register file being written. The shading indicates the element is used by the instruction. Hence, *MEM* has a white background because *add* does not access the data memory. Shading on the right half of the register file or memory means the element is read in that stage, and shading of the left half means it is written in that stage. Hence the right half of *ID* is shaded in the second stage because the register file is read, and the left half of *WB* is shaded in the fifth stage because the register file is written.

Figure 4.27 shows the connection to forward the value in *x1* after the execution stage of the *add* instruction as input to the execution stage of the *sub* instruction.

ANSWER

In this graphical representation of events, forwarding paths are valid only if the destination stage is later in time than the source stage. For example, there cannot be a valid forwarding path from the output of the memory access stage in the first instruction to the input of the execution stage of the following, since that would mean going backward in time.

Forwarding works very well and is described in detail in Section 4.7. It cannot prevent all pipeline stalls, however. For example, suppose the first instruction was a load of *x1* instead of an *add*. As we can imagine from looking at Figure 4.27, the

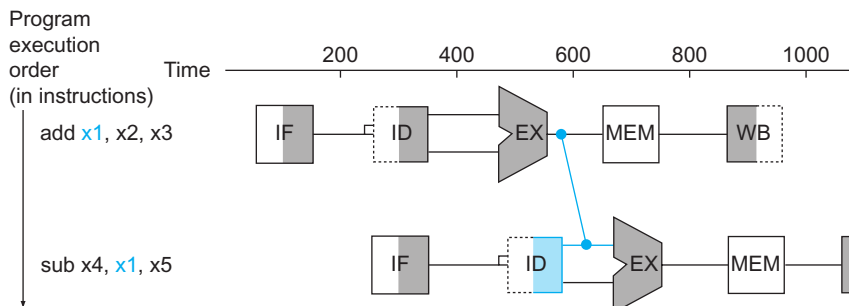


FIGURE 4.27 Graphical representation of forwarding. The connection shows the forwarding path from the output of the *EX* stage of *add* to the input of the *EX* stage for *sub*, replacing the value from register *x1* read in the second stage of *sub*.

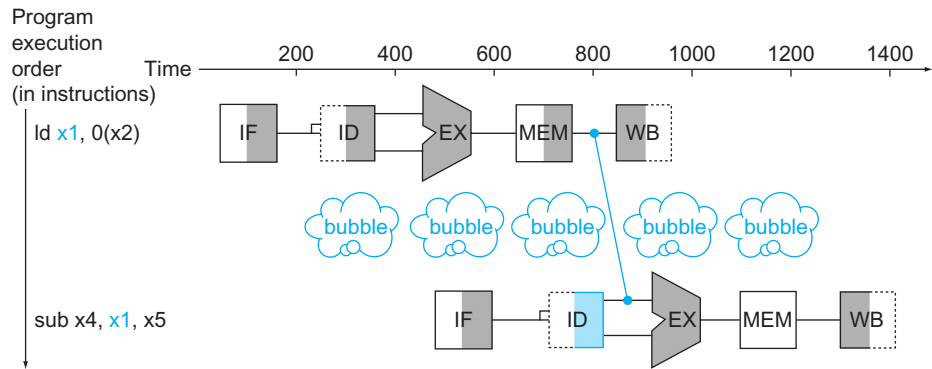


FIGURE 4.28 We need a stall even with forwarding when an R-format instruction following a load tries to use the data. Without the stall, the path from memory access stage output to execution stage input would be going backward in time, which is impossible. This figure is actually a simplification, since we cannot know until after the subtract instruction is fetched and decoded whether or not a stall will be necessary. Section 4.7 shows the details of what really happens in the case of a hazard.

load-use data hazard

A specific form of data hazard in which the data being loaded by a load instruction have not yet become available when they are needed by another instruction.

pipeline stall Also called **bubble**. A stall initiated in order to resolve a hazard.

desired data would be available only *after* the fourth stage of the first instruction in the dependence, which is too late for the *input* of the third stage of `sub`. Hence, even with forwarding, we would have to stall one stage for a **load-use data hazard**, as Figure 4.28 shows. This figure shows an important pipeline concept, officially called a **pipeline stall**, but often given the nickname **bubble**. We shall see stalls elsewhere in the pipeline. Section 4.7 shows how we can handle hard cases like these, using either hardware detection and stalls or software that reorders code to try to avoid load-use pipeline stalls, as this example illustrates.

Reordering Code to Avoid Pipeline Stalls

Consider the following code segment in C:

```
a = b + e;
c = b + f;
```

Here is the generated RISC-V code for this segment, assuming all variables are in memory and are addressable as offsets from `x31`:

```
ld    x1, 0(x31)    // Load b
ld    x2, 8(x31)    // Load e
add   x3, x1, x2    // b + e
sd    x3, 24(x31)   // Store a
ld    x4, 16(x31)   // Load f
add   x5, x1, x4    // b + f
sd    x5, 32(x31)   // Store c
```

EXAMPLE

Find the hazards in the preceding code segment and reorder the instructions to avoid any pipeline stalls.

Both add instructions have a hazard because of their respective dependence on the previous ld instruction. Notice that forwarding eliminates several other potential hazards, including the dependence of the first add on the first ld and any hazards for store instructions. Moving up the third ld instruction to become the third instruction eliminates both hazards:

ANSWER

```
ld    x1, 0(x31)
ld    x2, 8(x31)
ld    x4, 16(x31)
add   x3, x1, x2
sd    x3, 24(x31)
add   x5, x1, x4
sd    x5, 32(x31)
```

On a pipelined processor with forwarding, the reordered sequence will complete in two fewer cycles than the original version.

Forwarding yields another insight into the RISC-V architecture, in addition to the three mentioned on page 267. Each RISC-V instruction writes at most one result and does this in the last stage of the pipeline. Forwarding is harder if there are multiple results to forward per instruction or if there is a need to write a result early on in instruction execution.

Elaboration: The name “forwarding” comes from the idea that the result is passed forward from an earlier instruction to a later instruction. “Bypassing” comes from passing the result around the register file to the desired unit.

Control Hazards

The third type of hazard is called a **control hazard**, arising from the need to make a decision based on the results of one instruction while others are executing.

Suppose our laundry crew was given the happy task of cleaning the uniforms of a football team. Given how filthy the laundry is, we need to determine whether the detergent and water temperature setting we select are strong enough to get the uniforms clean but not so strong that the uniforms wear out sooner. In our laundry pipeline, we have to wait until the second stage to examine the dry uniform to see if we need to change the washer setup or not. What to do?

Here is the first of two solutions to control hazards in the laundry room and its computer equivalent.

Stall: Just operate sequentially until the first batch is dry and then repeat until you have the right formula.

This conservative option certainly works, but it is slow.

control hazard Also called **branch hazard**. When the proper instruction cannot execute in the proper pipeline clock cycle because the instruction that was fetched is not the one that is needed; that is, the flow of instruction addresses is not what the pipeline expected.

The equivalent decision task in a computer is the conditional branch instruction. Notice that we must begin fetching the instruction following the branch on the following clock cycle. Nevertheless, the pipeline cannot possibly know what the next instruction should be, since it *only just received* the branch instruction from memory! Just as with laundry, one possible solution is to stall immediately after we fetch a branch, waiting until the pipeline determines the outcome of the branch and knows what instruction address to fetch from.

Let’s assume that we put in enough extra hardware so that we can test a register, calculate the branch address, and update the PC during the second stage of the pipeline (see [Section 4.8](#) for details). Even with this added hardware, the pipeline involving conditional branches would look like [Figure 4.29](#). The instruction to be executed if the branch fails is stalled one extra 200 ps clock cycle before starting.

EXAMPLE

Performance of “Stall on Branch”

Estimate the impact on the *clock cycles per instruction* (CPI) of stalling on branches. Assume all other instructions have a CPI of 1.

ANSWER

[Figure 3.28](#) in [Chapter 3](#) shows that conditional branches are 17% of the instructions executed in SPECint2006. Since the other instructions run have a CPI of 1, and conditional branches took one extra clock cycle for the stall, then we would see a CPI of 1.17 and hence a slowdown of 1.17 versus the ideal case.

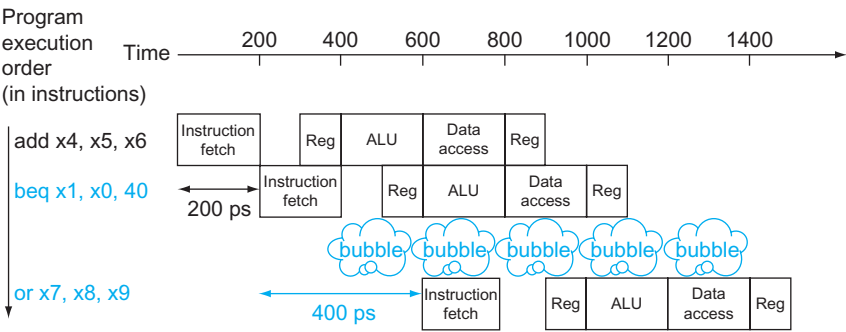


FIGURE 4.29 Pipeline showing stalling on every conditional branch as solution to control hazards. This example assumes the conditional branch is taken, and the instruction at the destination of the branch is the `or` instruction. There is a one-stage pipeline stall, or bubble, after the branch. In reality, the process of creating a stall is slightly more complicated, as we will see in [Section 4.8](#). The effect on performance, however, is the same as would occur if a bubble were inserted.

If we cannot resolve the branch in the second stage, as is often the case for longer pipelines, then we'd see an even larger slowdown if we stall on conditional branches. The cost of this option is too high for most computers to use and motivates a second solution to the control hazard using one of our great ideas from [Chapter 1](#):

Predict: If you're sure you have the right formula to wash uniforms, then just *predict* that it will work and wash the second load while waiting for the first load to dry.

This option does not slow down the pipeline when you are correct. When you are wrong, however, you need to redo the load that was washed while guessing the decision.

Computers do indeed use **prediction** to handle conditional branches. One simple approach is to predict always that conditional branches will be untaken. When you're right, the pipeline proceeds at full speed. Only when conditional branches are taken does the pipeline stall. [Figure 4.30](#) shows such an example.


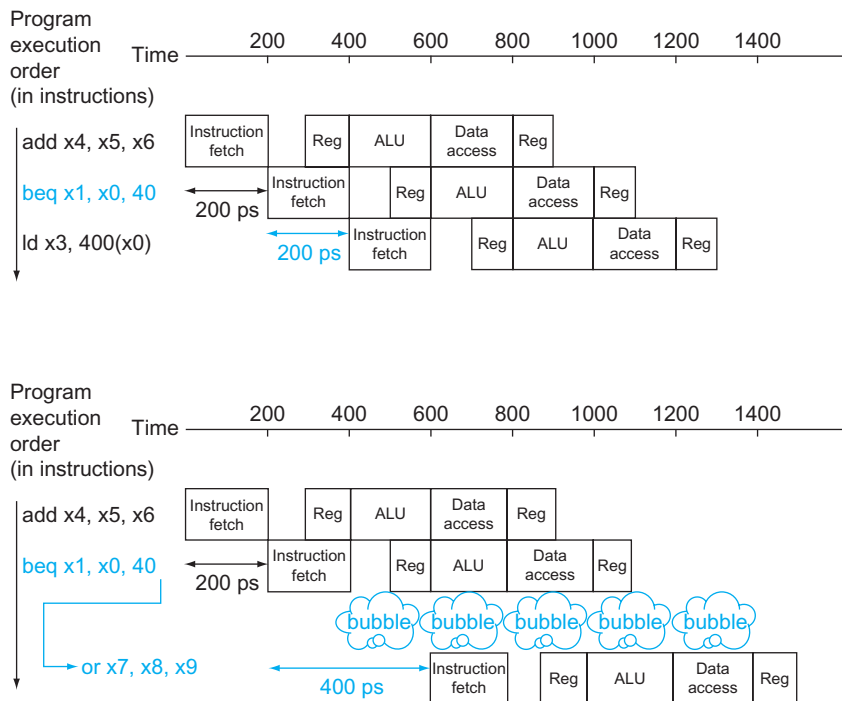


FIGURE 4.30 Predicting that branches are not taken as a solution to control hazard. The top drawing shows the pipeline when the branch is not taken. The bottom drawing shows the pipeline when the branch is taken. As we noted in [Figure 4.29](#), the insertion of a bubble in this fashion simplifies what actually happens, at least during the first clock cycle immediately following the branch. [Section 4.8](#) will reveal the details.

branch prediction

 A method of resolving a branch hazard that assumes a given outcome for the conditional branch and proceeds from that assumption rather than waiting to ascertain the actual outcome.



PREDICTION

A more sophisticated version of **branch prediction** would have some conditional branches predicted as taken and some as untaken. In our analogy, the dark or home uniforms might take one formula while the light or road uniforms might take another. In the case of programming, at the bottom of loops are conditional branches that branch back to the top of the loop. Since they are likely to be taken and they branch backward, we could always predict taken for conditional branches that branch to an earlier address.

Such rigid approaches to branch prediction rely on stereotypical behavior and don't account for the individuality of a specific branch instruction. *Dynamic* hardware predictors, in stark contrast, make their guesses depending on the behavior of each conditional branch and may change predictions for a conditional branch over the life of a program. Following our analogy, in dynamic prediction a person would look at how dirty the uniform was and guess at the formula, adjusting the next **prediction** depending on the success of recent guesses.

One popular approach to dynamic prediction of conditional branches is keeping a history for each conditional branch as taken or untaken, and then using the recent past behavior to predict the future. As we will see later, the amount and type of history kept have become extensive, with the result being that dynamic branch predictors can correctly predict conditional branches with more than 90% accuracy (see [Section 4.8](#)). When the guess is wrong, the pipeline control must ensure that the instructions following the wrongly guessed conditional branch have no effect and must restart the pipeline from the proper branch address. In our laundry analogy, we must stop taking new loads so that we can restart the load that we incorrectly predicted.

As in the case of all other solutions to control hazards, longer pipelines exacerbate the problem, in this case by raising the cost of misprediction. Solutions to control hazards are described in more detail in [Section 4.8](#).

Elaboration: There is a third approach to the control hazard, called a *delayed decision*. In our analogy, whenever you are going to make such a decision about laundry, just place a load of non-football clothes in the washer while waiting for football uniforms to dry. As long as you have enough dirty clothes that are not affected by the test, this solution works fine.

Called the *delayed branch* in computers, this is the solution actually used by the MIPS architecture. The delayed branch always executes the next sequential instruction, with the branch taking place *after* that one instruction delay. It is hidden from the MIPS assembly language programmer because the assembler can automatically arrange the instructions to get the branch behavior desired by the programmer. MIPS software will place an instruction immediately after the delayed branch instruction that is not affected by the branch, and a taken branch changes the address of the instruction that *follows* this safe instruction. In our example, the `add` instruction before the branch in [Figure 4.29](#) does not affect the branch and can be moved after the branch to hide the branch delay fully. Since delayed branches are useful when the branches are short, it is rare to see a processor with a delayed branch of more than one cycle. For longer branch delays, hardware-based branch prediction is usually used.

Pipeline Overview Summary

Pipelining is a technique that exploits **parallelism** between the instructions in a sequential instruction stream. It has the substantial advantage that, unlike programming a multiprocessor (see [Chapter 6](#)), it is fundamentally invisible to the programmer.

In the next few sections of this chapter, we cover the concept of pipelining using the RISC-V instruction subset from the single-cycle implementation in [Section 4.4](#) and show a simplified version of its pipeline. We then look at the problems that **pipelining** introduces and the performance attainable under typical situations.

If you wish to focus more on the software and the performance implications of pipelining, you now have sufficient background to skip to [Section 4.10](#). [Section 4.10](#) introduces advanced pipelining concepts, such as superscalar and dynamic scheduling, and [Section 4.11](#) examines the pipelines of recent microprocessors.


Alternatively, if you are interested in understanding how pipelining is implemented and the challenges of dealing with hazards, you can proceed to examine the design of a pipelined datapath and the basic control, explained in [Section 4.6](#). You can then use this understanding to explore the implementation of forwarding and stalls in [Section 4.7](#). You can next read [Section 4.8](#) to learn more about solutions to branch hazards, and finally see how exceptions are handled in [Section 4.9](#).

For each code sequence below, state whether it must stall, can avoid stalls using only forwarding, or can execute without stalling or forwarding.

Sequence 1	Sequence 2	Sequence 3
ld x10, 0(x10)	add x11, x10, x10	addi x11, x10, 1
add x11, x10, x10	addi x12, x10, 5	addi x12, x10, 2
	addi x14, x11, 5	addi x13, x10, 3
		addi x14, x10, 4
		addi x15, x10, 5



PARALLELISM

 

PIPELINING

Check Yourself

Outside the memory system, the effective operation of the pipeline is usually the most important factor in determining the CPI of the processor and hence its performance. As we will see in [Section 4.10](#), understanding the performance of a modern multiple-issue pipelined processor is complex and requires understanding more than just the issues that arise in a simple pipelined processor. Nonetheless, structural, data, and control hazards remain important in both simple pipelines and more sophisticated ones.

For modern pipelines, structural hazards usually revolve around the floating-point unit, which may not be fully pipelined, while control hazards are usually more of a problem in integer programs, which tend to have higher conditional branch frequencies as well as less predictable branches. Data hazards can be

Understanding Program Performance



performance bottlenecks in both integer and floating-point programs. Often it is easier to deal with data hazards in floating-point programs because the lower conditional branch frequency and more regular memory access patterns allow the compiler to try to schedule instructions to avoid hazards. It is more difficult to perform such optimizations in integer programs that have less regular memory accesses, involving more use of pointers. As we will see in [Section 4.10](#), there are more ambitious compiler and hardware techniques for reducing data dependences through scheduling.

The BIG Picture

latency (pipeline) The number of stages in a pipeline or the number of stages between two instructions during execution.



There is less in this than meets the eye.

Tallulah
Bankhead, remark
to Alexander
Woollcott, 1922

Pipelining increases the number of simultaneously executing instructions and the rate at which instructions are started and completed. Pipelining does not reduce the time it takes to complete an individual instruction, also called the **latency**. For example, the five-stage pipeline still takes five clock cycles for the instruction to complete. In the terms used in [Chapter 1](#), pipelining improves instruction *throughput* rather than individual instruction *execution time* or *latency*.

Instruction sets can either make life harder or simpler for pipeline designers, who must already cope with structural, control, and data hazards. Branch **prediction** and forwarding help make a computer fast while still getting the right answers.

4.6

Pipelined Datapath and Control

[Figure 4.31](#) shows the single-cycle datapath from [Section 4.4](#) with the pipeline stages identified. The division of an instruction into five stages means a five-stage pipeline, which in turn means that up to five instructions will be in execution during any single clock cycle. Thus, we must separate the datapath into five pieces, with each piece named corresponding to a stage of instruction execution:

1. IF: Instruction fetch
2. ID: Instruction decode and register file read
3. EX: Execution or address calculation
4. MEM: Data memory access
5. WB: Write back

In [Figure 4.31](#), these five components correspond roughly to the way the datapath is drawn; instructions and data move generally from left to right through the

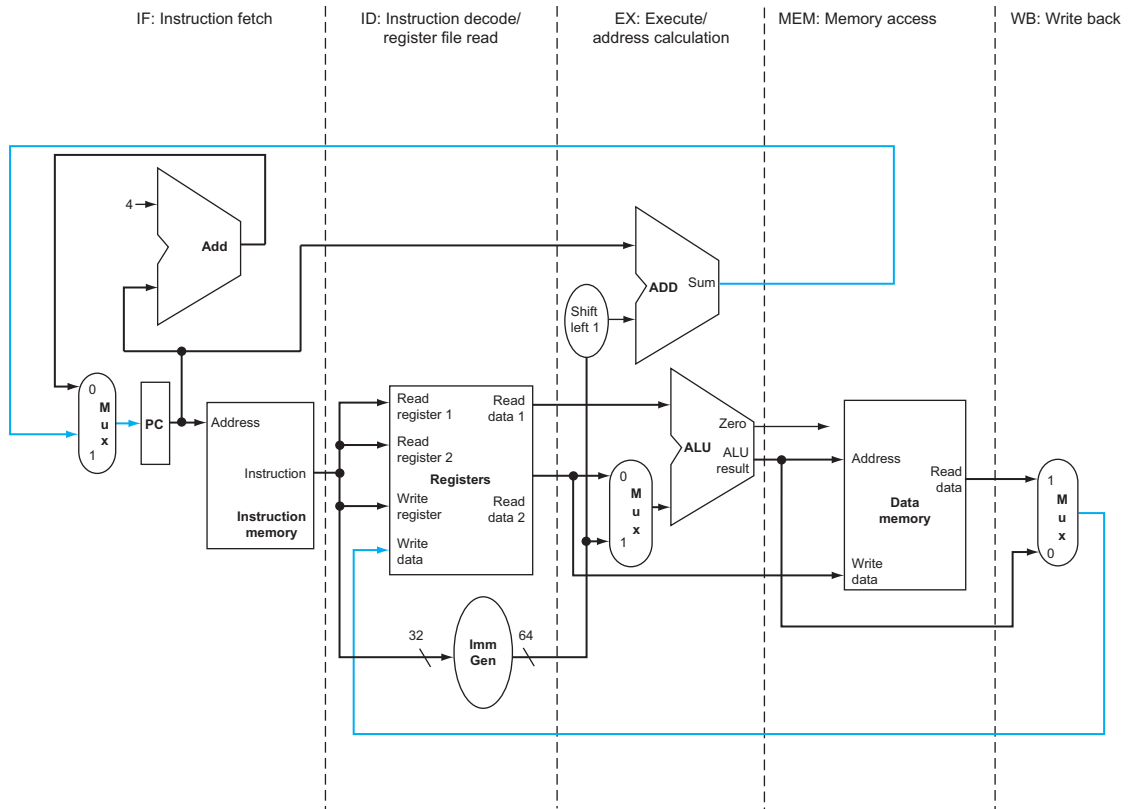


FIGURE 4.31 The single-cycle datapath from Section 4.4 (similar to Figure 4.17). Each step of the instruction can be mapped onto the datapath from left to right. The only exceptions are the update of the PC and the write-back step, shown in color, which sends either the ALU result or the data from memory to the left to be written into the register file. (Normally we use color lines for control, but these are data lines.)

five stages as they complete execution. Returning to our laundry analogy, clothes get cleaner, drier, and more organized as they move through the line, and they never move backward.

There are, however, two exceptions to this left-to-right flow of instructions:

- The write-back stage, which places the result back into the register file in the middle of the datapath
- The selection of the next value of the PC, choosing between the incremented PC and the branch address from the MEM stage

Data flowing from right to left do not affect the current instruction; these reverse data movements influence only later instructions in the pipeline. Note that the first

right-to-left flow of data can lead to data hazards and the second leads to control hazards.

One way to show what happens in pipelined execution is to pretend that each instruction has its own datapath, and then to place these datapaths on a timeline to show their relationship. Figure 4.32 shows the execution of the instructions in Figure 4.25 by displaying their private datapaths on a common timeline. We use a stylized version of the datapath in Figure 4.31 to show the relationships in Figure 4.32.

Figure 4.32 seems to suggest that three instructions need three datapaths. Instead, we add registers to hold data so that portions of a single datapath can be shared during instruction execution.

For example, as Figure 4.32 shows, the instruction memory is used during only one of the five stages of an instruction, allowing it to be shared by following instructions during the other four stages. To retain the value of an individual instruction for its other four stages, the value read from instruction memory must be saved in a register. Similar arguments apply to every pipeline stage, so we must place registers wherever there are dividing lines between stages in Figure 4.31. Returning to our laundry analogy, we might have a basket between each pair of stages to hold the clothes for the next step.

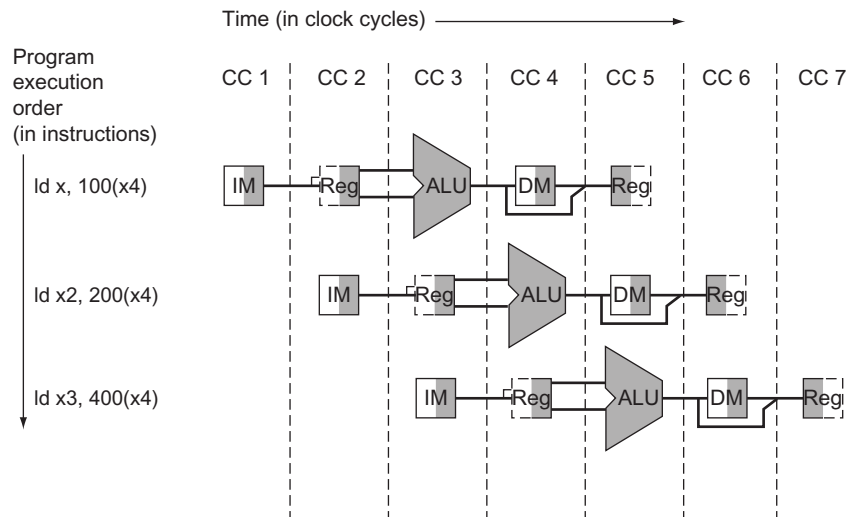


FIGURE 4.32 Instructions being executed using the single-cycle datapath in Figure 4.31, assuming pipelined execution. Similar to Figures 4.26 through 4.28, this figure pretends that each instruction has its own datapath, and shades each portion according to use. Unlike those figures, each stage is labeled by the physical resource used in that stage, corresponding to the portions of the datapath in Figure 4.31. *IM* represents the instruction memory and the PC in the instruction fetch stage, *Reg* stands for the register file and sign extender in the instruction decode/register file read stage (ID), and so on. To maintain proper time order, this stylized datapath breaks the register file into two logical parts: registers read during register fetch (ID) and registers written during write back (WB). This dual use is represented by drawing the unshaded left half of the register file using dashed lines in the ID stage, when it is not being written, and the unshaded right half in dashed lines in the WB stage, when it is not being read. As before, we assume the register file is written in the first half of the clock cycle and the register file is read during the second half.

Of course, every instruction updates the PC, whether by incrementing it or by setting it to a branch destination address. The PC can be thought of as a pipeline register: one that feeds the IF stage of the pipeline. Unlike the shaded pipeline registers in [Figure 4.33](#), however, the PC is part of the visible architectural state; its contents must be saved when an exception occurs, while the contents of the pipeline registers can be discarded. In the laundry analogy, you could think of the PC as corresponding to the basket that holds the load of dirty clothes before the wash step.

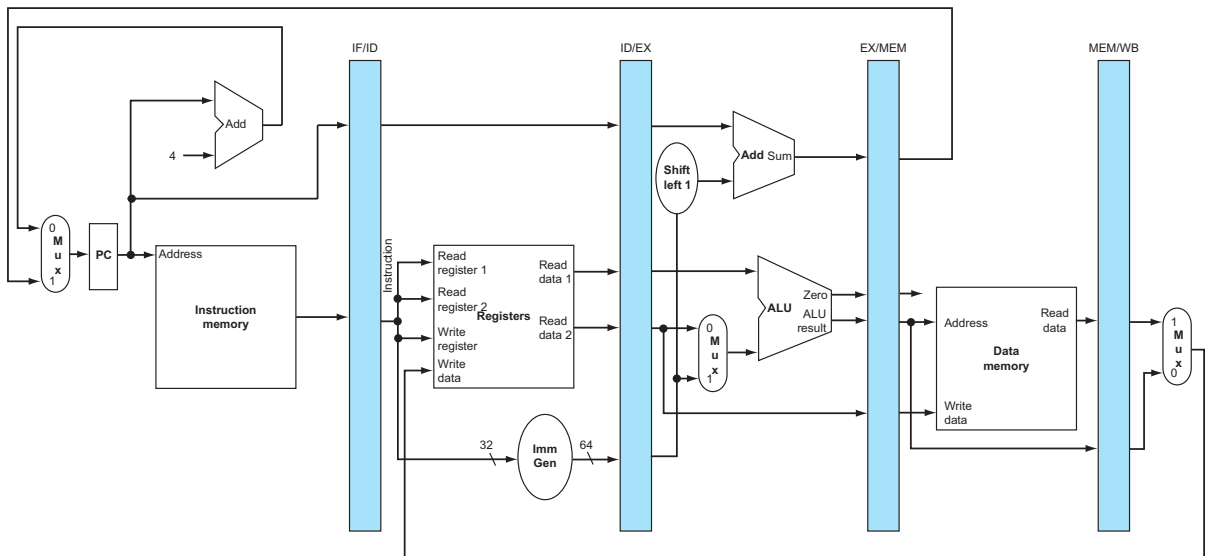


FIGURE 4.33 The pipelined version of the datapath in Figure 4.31. The pipeline registers, in color, separate each pipeline stage. They are labeled by the stages that they separate; for example, the first is labeled *IF/ID* because it separates the instruction fetch and instruction decode stages. The registers must be wide enough to store all the data corresponding to the lines that go through them. For example, the IF/ID register must be 96 bits wide, because it must hold both the 32-bit instruction fetched from memory and the incremented 64-bit PC address. We will expand these registers over the course of this chapter, but for now the other three pipeline registers contain 256, 193, and 128 bits, respectively.

less time than it might appear, because you can compare them to see what changes occur in each clock cycle. [Section 4.7](#) describes what happens when there are data hazards between pipelined instructions; ignore them for now.

[Figures 4.34 through 4.37](#), our first sequence, show the active portions of the datapath highlighted as a load instruction goes through the five stages of pipelined execution. We show a load first because it is active in all five stages. As in [Figures 4.26 through 4.28](#), we highlight the *right half* of registers or memory when they are being *read* and highlight the *left half* when they are being *written*.

We show the instruction `ld` with the name of the pipe stage that is active in each figure. The five stages are the following:

1. *Instruction fetch*: The top portion of [Figure 4.34](#) shows the instruction being read from memory using the address in the PC and then being placed in the IF/ID pipeline register. The PC address is incremented by 4 and then written back into the PC to be ready for the next clock cycle. This PC is also saved in the IF/ID pipeline register in case it is needed later for an instruction, such as `beq`. The computer cannot know which type of instruction is being fetched, so it must prepare for any instruction, passing potentially needed information down the pipeline.
2. *Instruction decode and register file read*: The bottom portion of [Figure 4.34](#) shows the instruction portion of the IF/ID pipeline register supplying the immediate field, which is sign-extended to 64 bits, and the register numbers to read the two registers. All three values are stored in the ID/EX pipeline register, along with the PC address. We again transfer everything that might be needed by any instruction during a later clock cycle.
3. *Execute or address calculation*: [Figure 4.35](#) shows that the load instruction reads the contents of a register and the sign-extended immediate from the ID/EX pipeline register and adds them using the ALU. That sum is placed in the EX/MEM pipeline register.
4. *Memory access*: The top portion of [Figure 4.36](#) shows the load instruction reading the data memory using the address from the EX/MEM pipeline register and loading the data into the MEM/WB pipeline register.
5. *Write-back*: The bottom portion of [Figure 4.36](#) shows the final step: reading the data from the MEM/WB pipeline register and writing it into the register file in the middle of the figure.

This walk-through of the load instruction shows that any information needed in a later pipe stage must be passed to that stage via a pipeline register. Walking through a store instruction shows the similarity of instruction execution, as well as passing the information for later stages. Here are the five pipe stages of the store instruction:

 


FIGURE 4.34 IF and ID: First and second pipe stages of an instruction, with the active portions of the datapath in Figure 4.33 highlighted. The highlighting convention is the same as that used in Figure 4.26. As in Section 4.2, there is no confusion when reading and writing registers, because the contents change only on the clock edge. Although the load needs only the top register in stage 2, it doesn't hurt to do potentially extra work, so it sign-extends the constant and reads both registers into the ID/EX pipeline register. We don't need all three operands, but it simplifies control to keep all three.

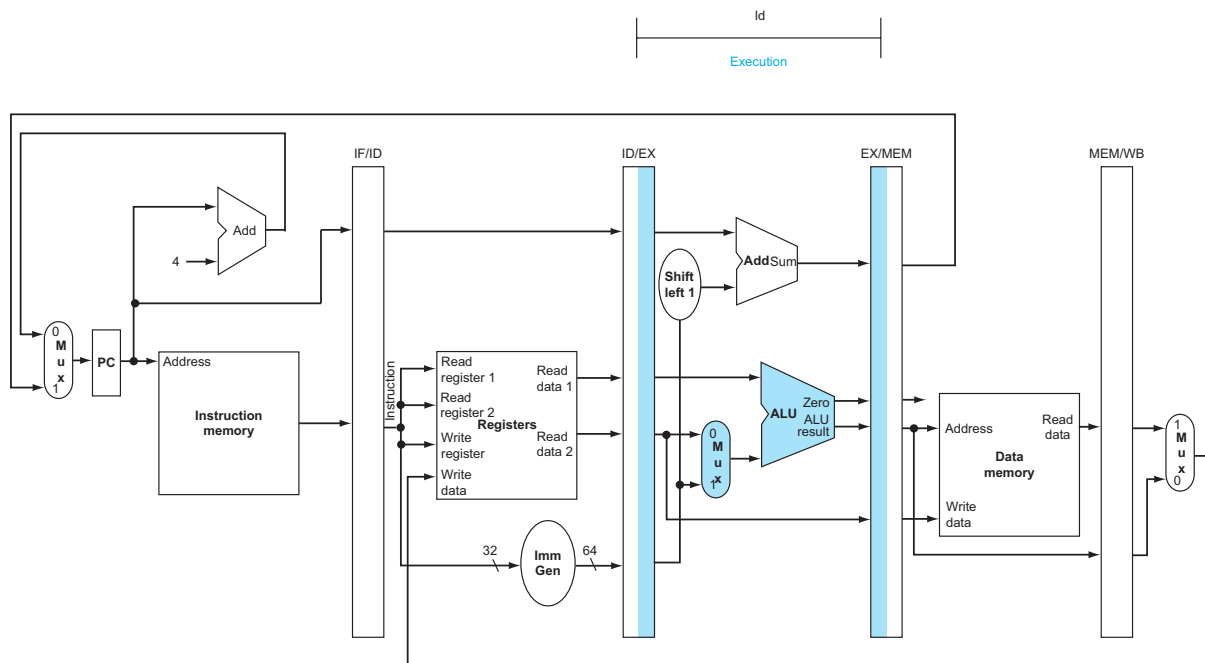


FIGURE 4.35 EX: The third pipe stage of a load instruction, highlighting the portions of the datapath in Figure 4.33 used in this pipe stage. The register is added to the sign-extended immediate, and the sum is placed in the EX/MEM pipeline register.

1. *Instruction fetch:* The instruction is read from memory using the address in the PC and then is placed in the IF/ID pipeline register. This stage occurs before the instruction is identified, so the top portion of Figure 4.34 works for store as well as load.
2. *Instruction decode and register file read:* The instruction in the IF/ID pipeline register supplies the register numbers for reading two registers and extends the sign of the immediate operand. These three 64-bit values are all stored in the ID/EX pipeline register. The bottom portion of Figure 4.34 for load instructions also shows the operations of the second stage for stores. These first two stages are executed by all instructions, since it is too early to know the type of the instruction. (While the store instruction uses the rs2 field to read the second register in this pipe stage, that detail is not shown in this pipeline diagram, so we can use the same figure for both.)
3. *Execute and address calculation:* Figure 4.37 shows the third step; the effective address is placed in the EX/MEM pipeline register.
4. *Memory access:* The top portion of Figure 4.38 shows the data being written to memory. Note that the register containing the data to be stored was read in an earlier stage and stored in ID/EX. The only way to make the data available during the MEM stage is to place the data into the EX/MEM pipeline register in the EX stage, just as we stored the effective address into EX/MEM.

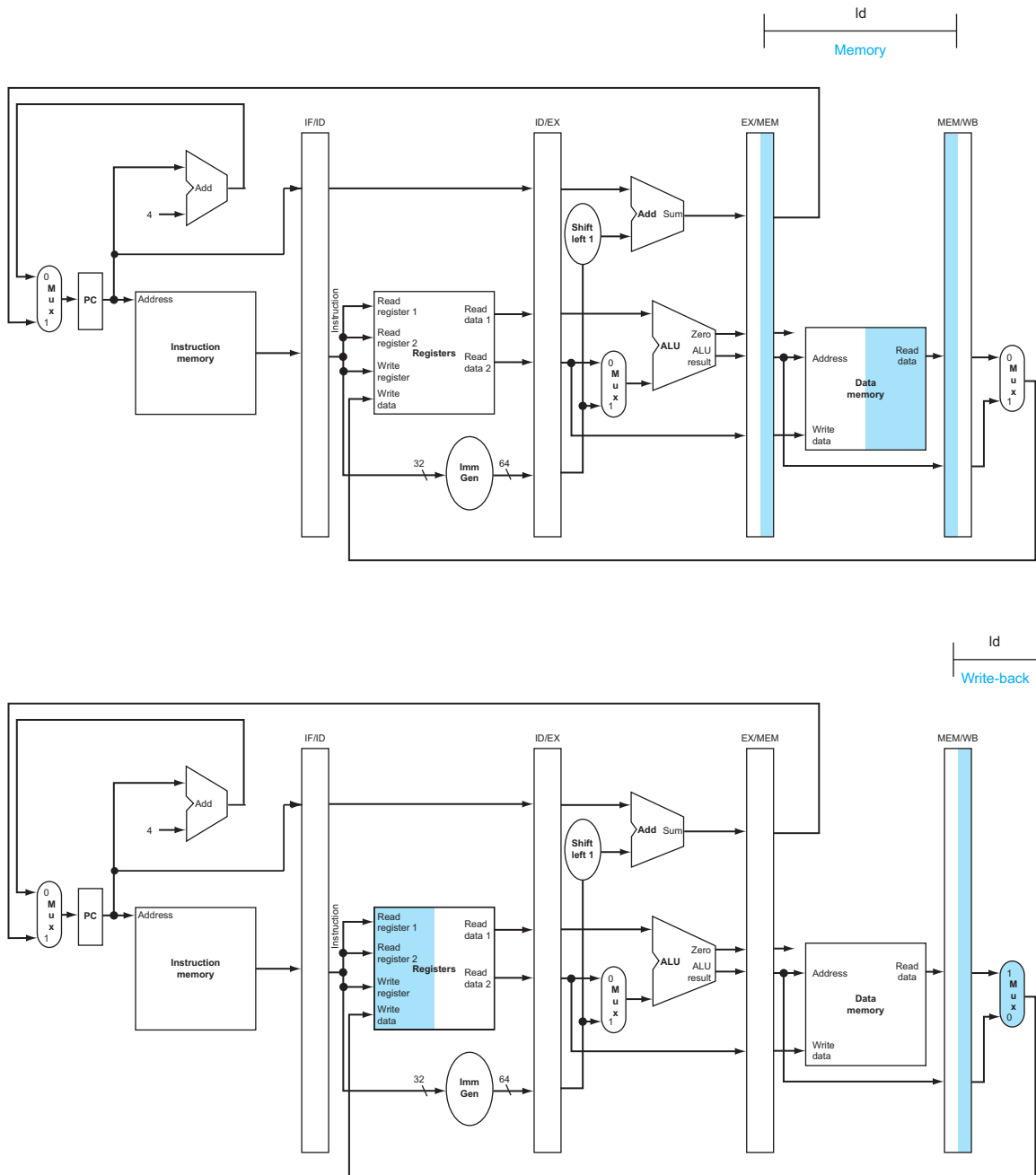


FIGURE 4.36 MEM and WB: The fourth and fifth pipe stages of a load instruction, highlighting the portions of the datapath in Figure 4.33 used in this pipe stage. Data memory is read using the address in the EX/MEM pipeline registers, and the data are placed in the MEM/WB pipeline register. Next, data are read from the MEM/WB pipeline register and written into the register file in the middle of the datapath. Note: there is a bug in this design that is repaired in Figure 4.39.

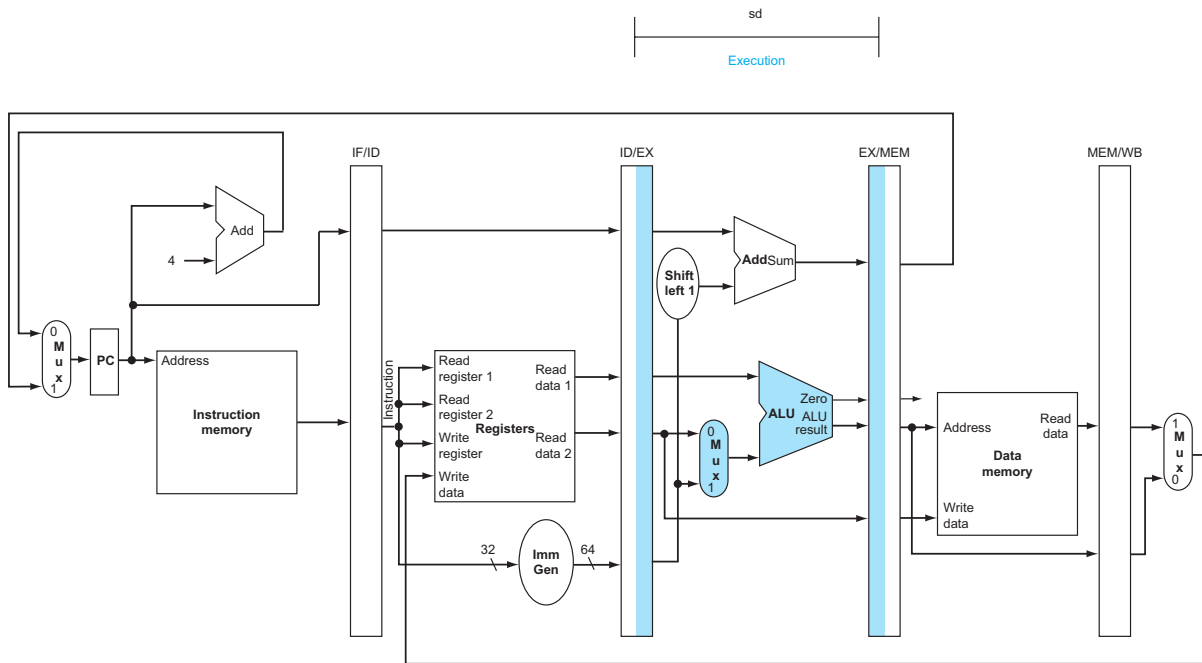


FIGURE 4.37 EX: The third pipe stage of a store instruction. Unlike the third stage of the load instruction in [Figure 4.35](#), the second register value is loaded into the EX/MEM pipeline register to be used in the next stage. Although it wouldn't hurt to always write this second register into the EX/MEM pipeline register, we write the second register only on a store instruction to make the pipeline easier to understand.

5. *Write-back:* The bottom portion of [Figure 4.38](#) shows the final step of the store. For this instruction, nothing happens in the write-back stage. Since every instruction behind the store is already in progress, we have no way to accelerate those instructions. Hence, an instruction passes through a stage even if there is nothing to do, because later instructions are already progressing at the maximum rate.

The store instruction again illustrates that to pass something from an early pipe stage to a later pipe stage, the information must be placed in a pipeline register; otherwise, the information is lost when the next instruction enters that pipeline stage. For the store instruction, we needed to pass one of the registers read in the ID stage to the MEM stage, where it is stored in memory. The data were first placed in the ID/EX pipeline register and then passed to the EX/MEM pipeline register.

Load and store illustrate a second key point: each logical component of the datapath—such as instruction memory, register read ports, ALU, data memory, and register write port—can be used only within a *single* pipeline stage. Otherwise, we would have a *structural hazard* (see page 267). Hence, these components, and their control, can be associated with a single pipeline stage.

Now we can uncover a bug in the design of the load instruction. Did you see it? Which register is changed in the final stage of the load? More specifically,

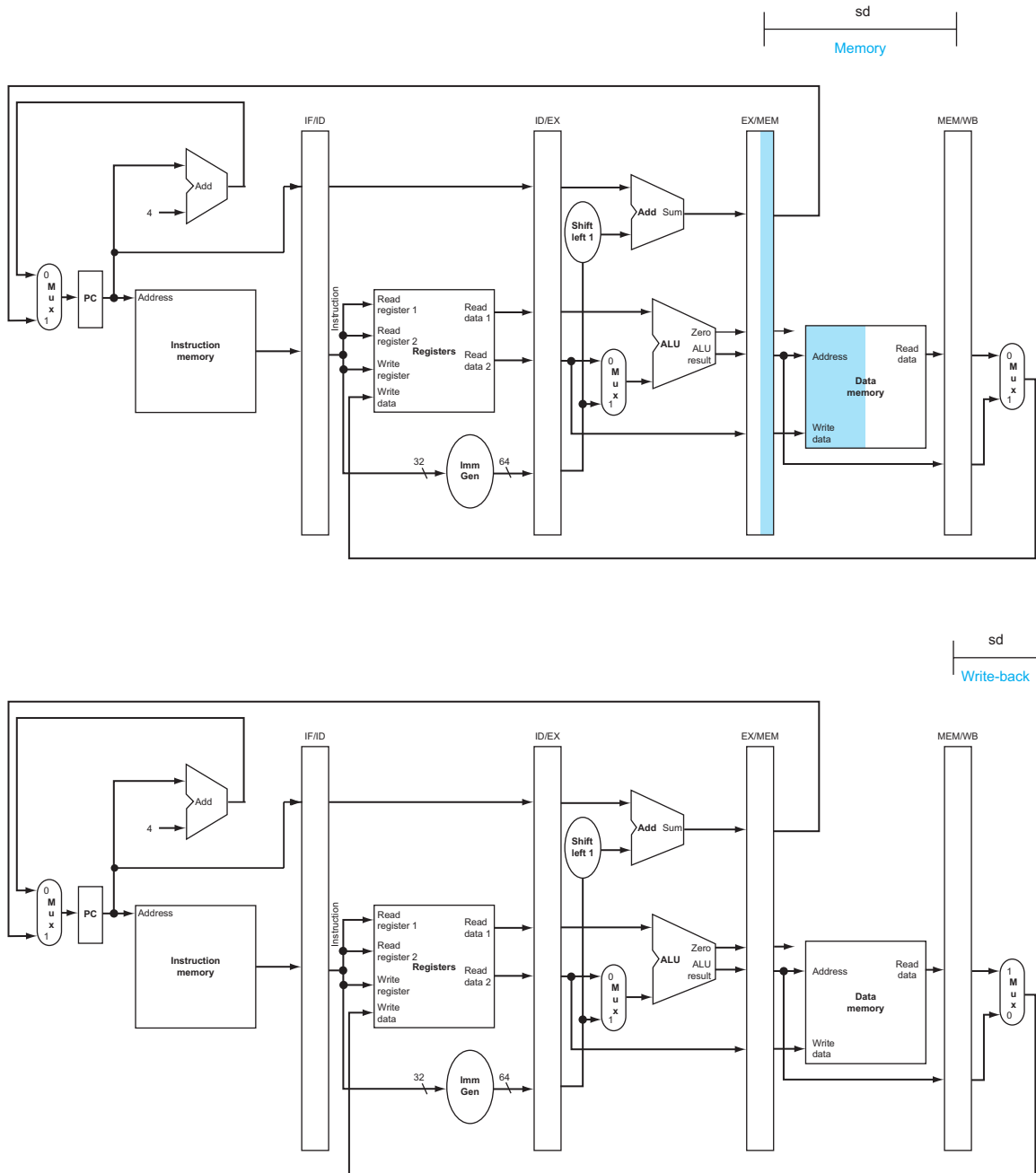


FIGURE 4.38 MEM and WB: The fourth and fifth pipe stages of a store instruction. In the fourth stage, the data are written into data memory for the store. Note that the data come from the EX/MEM pipeline register and that nothing is changed in the MEM/WB pipeline register. Once the data are written in memory, there is nothing left for the store instruction to do, so nothing happens in stage 5.

which instruction supplies the write register number? The instruction in the IF/ID pipeline register supplies the write register number, yet this instruction occurs considerably *after* the load instruction!

Hence, we need to preserve the destination register number in the load instruction. Just as store passed the register *value* from the ID/EX to the EX/MEM pipeline registers for use in the MEM stage, load must pass the register *number* from the ID/EX through EX/MEM to the MEM/WB pipeline register for use in the WB stage. Another way to think about the passing of the register number is that to share the pipelined datapath, we need to preserve the instruction read during the IF stage, so each pipeline register contains a portion of the instruction needed for that stage and later stages.

Figure 4.39 shows the correct version of the datapath, passing the write register number first to the ID/EX register, then to the EX/MEM register, and finally to the MEM/WB register. The register number is used during the WB stage to specify the register to be written. Figure 4.40 is a single drawing of the corrected datapath, highlighting the hardware used in all five stages of the load register instruction in Figures 4.34 through 4.36. See Section 4.8 for an explanation of how to make the branch instruction work as expected.

Graphically Representing Pipelines

Pipelining can be difficult to master, since many instructions are simultaneously executing in a single datapath in every clock cycle. To aid understanding, there are

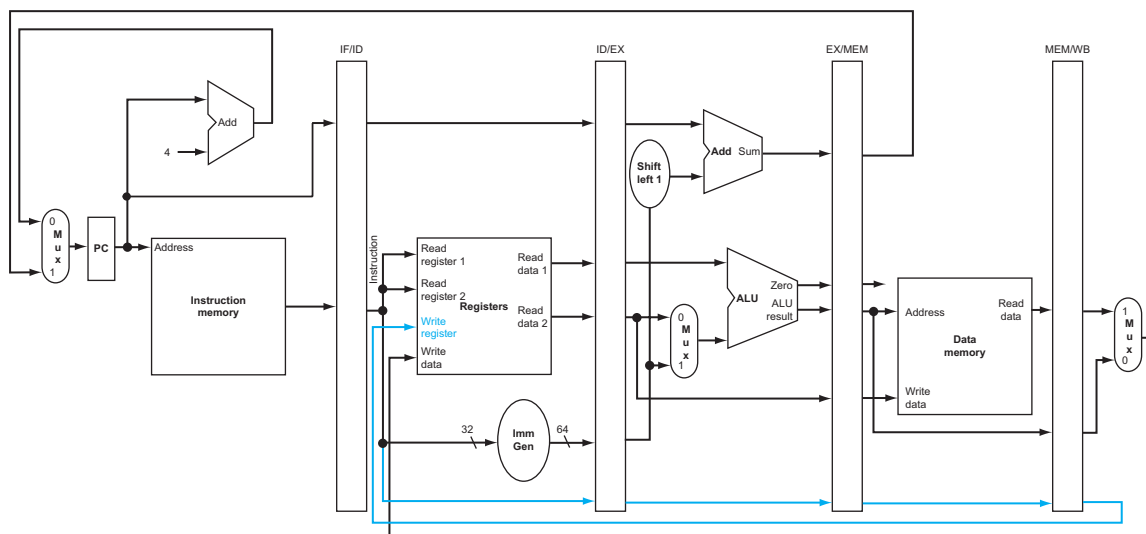


FIGURE 4.39 The corrected pipelined datapath to handle the load instruction properly. The write register number now comes from the MEM/WB pipeline register along with the data. The register number is passed from the ID pipe stage until it reaches the MEM/WB pipeline register, adding five more bits to the last three pipeline registers. This new path is shown in color.

two basic styles of pipeline figures: *multiple-clock-cycle pipeline diagrams*, such as Figure 4.32 on page 278, and *single-clock-cycle pipeline diagrams*, such as Figures 4.34 through 4.38. The multiple-clock-cycle diagrams are simpler but do not contain all the details. For example, consider the following five-instruction sequence:

```
ld      x10, 40(x1)
sub     x11, x2, x3
add     x12, x3, x4
ld      x13, 48(x1)
add     x14, x5, x6
```

Figure 4.41 shows the multiple-clock-cycle pipeline diagram for these instructions. Time advances from left to right across the page in these diagrams, and instructions advance from the top to the bottom of the page, similar to the laundry pipeline in Figure 4.23. A representation of the pipeline stages is placed in each portion along the instruction axis, occupying the proper clock cycles. These stylized datapaths represent the five stages of our pipeline graphically, but a rectangle naming each pipe stage works just as well. Figure 4.42 shows the more traditional version of the multiple-clock-cycle pipeline diagram. Note that Figure 4.41 shows the physical resources used at each stage, while Figure 4.42 uses the *name* of each stage.

Single-clock-cycle pipeline diagrams show the state of the entire datapath during a single clock cycle, and usually all five instructions in the pipeline are identified by labels above their respective pipeline stages. We use this type of figure to show the details of what is happening within the pipeline during each clock

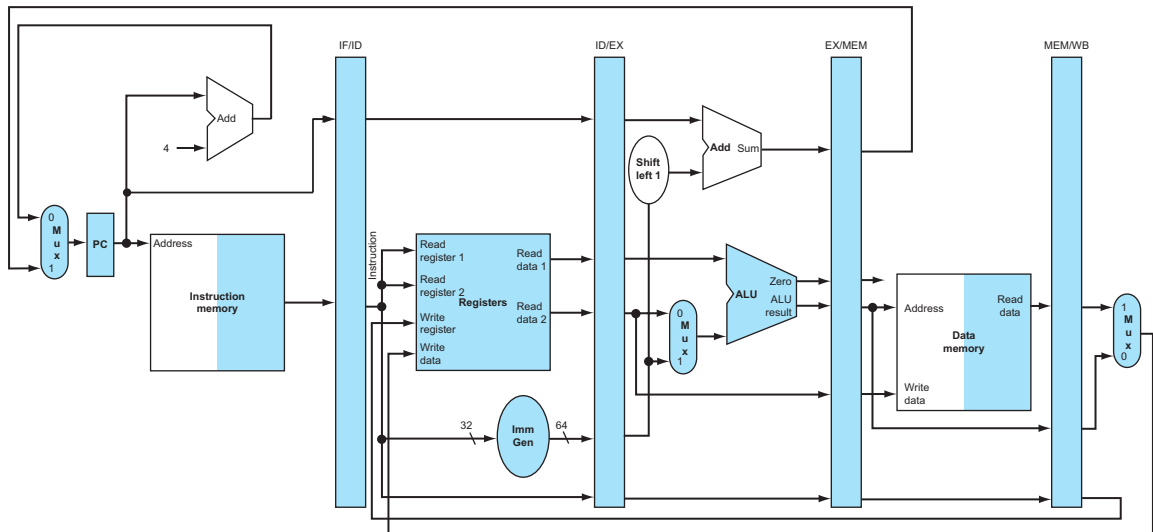


FIGURE 4.40 The portion of the datapath in Figure 4.39 that is used in all five stages of a load instruction.

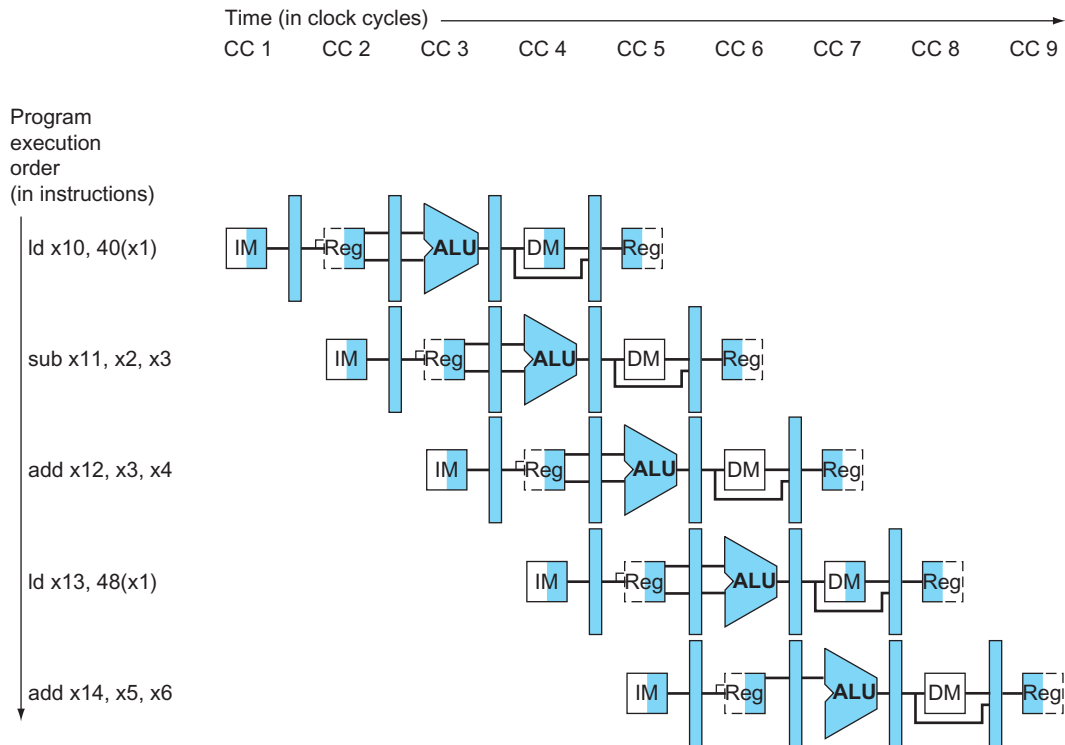


FIGURE 4.41 Multiple-clock-cycle pipeline diagram of five instructions. This style of pipeline representation shows the complete execution of instructions in a single figure. Instructions are listed in instruction execution order from top to bottom, and clock cycles move from left to right. Unlike Figure 4.26, here we show the pipeline registers between each stage. Figure 4.42 shows the traditional way to draw this diagram.

cycle; typically, the drawings appear in groups to show pipeline operation over a sequence of clock cycles. We use multiple-clock-cycle diagrams to give overviews of pipelining situations. (Section 4.13 gives more illustrations of single-clock diagrams if you would like to see more details about Figure 4.41.) A single-clock-cycle diagram represents a vertical slice of one clock cycle through a set of multiple-clock-cycle diagrams, showing the usage of the datapath by each of the instructions in the pipeline at the designated clock cycle. For example, Figure 4.43 shows the single-clock-cycle diagram corresponding to clock cycle 5 of Figures 4.41 and 4.42. Obviously, the single-clock-cycle diagrams have more detail and take significantly more space to show the same number of clock cycles. The exercises ask you to create such diagrams for other code sequences.

Check Yourself

A group of students were debating the efficiency of the five-stage pipeline when one student pointed out that not all instructions are active in every stage of the pipeline. After deciding to ignore the effects of hazards, they made the following four statements. Which ones are correct?

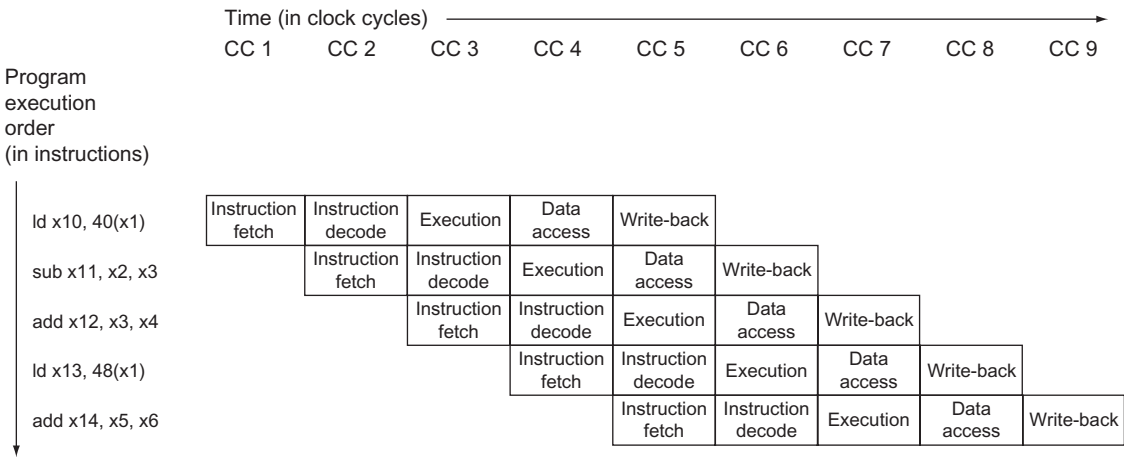


FIGURE 4.42 Traditional multiple-clock-cycle pipeline diagram of five instructions in [Figure 4.41](#).

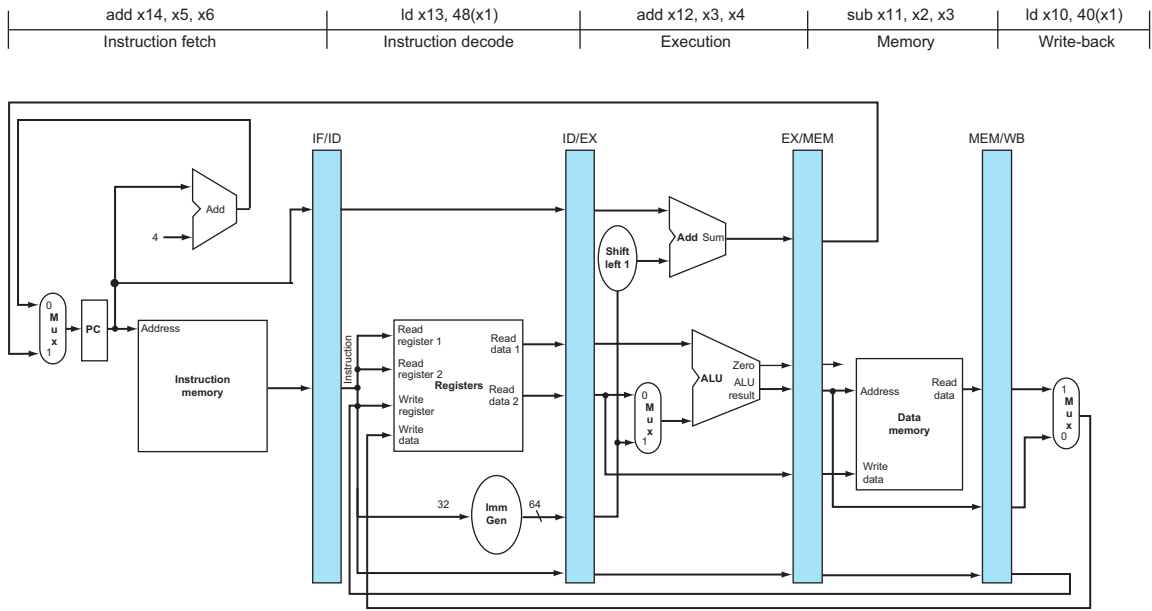


FIGURE 4.43 The single-clock-cycle diagram corresponding to clock cycle 5 of the pipeline in [Figures 4.41](#) and [4.42](#). As you can see, a single-clock-cycle figure is a vertical slice through a multiple-clock-cycle diagram.

1. Allowing branches and ALU instructions to take fewer stages than the five required by the load instruction will increase pipeline performance under all circumstances.

2. Trying to allow some instructions to take fewer cycles does not help, since the throughput is determined by the clock cycle; the number of pipe stages per instruction affects latency, not throughput.
3. You cannot make ALU instructions take fewer cycles because of the write-back of the result, but branches can take fewer cycles, so there is some opportunity for improvement.
4. Instead of trying to make instructions take fewer cycles, we should explore making the pipeline longer, so that instructions take more cycles, but the cycles are shorter. This could improve performance.

In the 6600 Computer, perhaps even more than in any previous computer, the control system is the difference.

James Thornton, *Design of a Computer: The Control Data 6600*, 1970

Pipelined Control

Just as we added control to the single-cycle datapath in [Section 4.4](#), we now add control to the pipelined datapath. We start with a simple design that views the problem through rose-colored glasses.

The first step is to label the control lines on the existing datapath. [Figure 4.44](#) shows those lines. We borrow as much as we can from the control for the simple

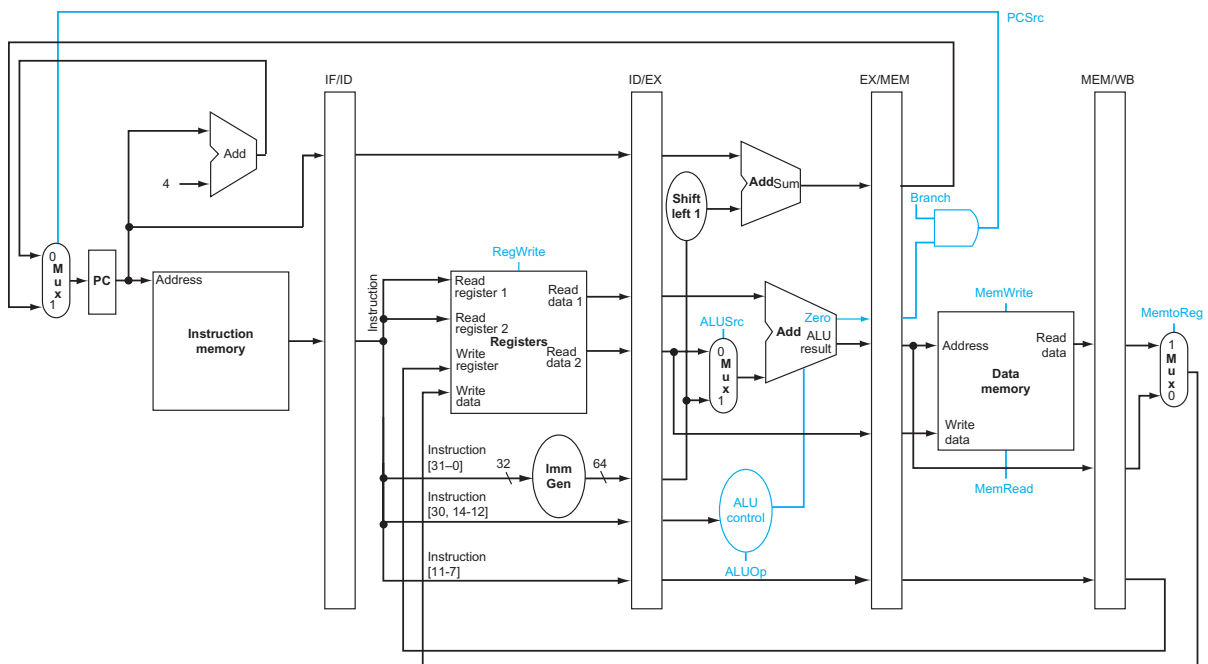


FIGURE 4.44 The pipelined datapath of [Figure 4.39](#) with the control signals identified. This datapath borrows the control logic for PC source, register destination number, and ALU control from [Section 4.4](#). Note that we now need funct fields of the instruction in the EX stage as input to ALU control, so these bits must also be included in the ID/EX pipeline register.

datapath in [Figure 4.17](#). In particular, we use the same ALU control logic, branch logic, and control lines. These functions are defined in [Figures 4.12, 4.16, and 4.18](#). We reproduce the key information in [Figures 4.45 through 4.47](#) on a single page to make the following discussion easier to absorb.

As was the case for the single-cycle implementation, we assume that the PC is written on each clock cycle, so there is no separate write signal for the PC. By the same argument, there are no separate write signals for the pipeline registers (IF/ID, ID/EX, EX/MEM, and MEM/WB), since the pipeline registers are also written during each clock cycle.

To specify control for the pipeline, we need only set the control values during each pipeline stage. Because each control line is associated with a component active in only a single pipeline stage, we can divide the control lines into five groups according to the pipeline stage.

1. *Instruction fetch*: The control signals to read instruction memory and to write the PC are always asserted, so there is nothing special to control in this pipeline stage.
2. *Instruction decode/register file read*: The two source registers are always in the same location in the RISC-V instruction formats, so there is nothing special to control in this pipeline stage.
3. *Execution/address calculation*: The signals to be set are ALUOp and ALUSrc (see [Figures 4.45 and 4.46](#)). The signals select the ALU operation and either Read data 2 or a sign-extended immediate as inputs to the ALU.
4. *Memory access*: The control lines set in this stage are Branch, MemRead, and MemWrite. The branch if equal, load, and store instructions set these signals, respectively. Recall that PCSrc in [Figure 4.46](#) selects the next sequential address unless control asserts Branch and the ALU result was 0.
5. *Write-back*: The two control lines are MemtoReg, which decides between sending the ALU result or the memory value to the register file, and RegWrite, which writes the chosen value.

Since pipelining the datapath leaves the meaning of the control lines unchanged, we can use the same control values. [Figure 4.47](#) has the same values as in [Section 4.4](#), but now the seven control lines are grouped by pipeline stage.

Instruction	ALUOp	operation	Funct7 field	Funct3 field	Desired ALU action	ALU control input
ld	00	load doubleword	XXXXXX	XXX	add	0010
sd	00	store doubleword	XXXXXX	XXX	add	0010
beq	01	branch if equal	XXXXXX	XXX	subtract	0110
R-type	10	add	0000000	000	add	0010
R-type	10	sub	0100000	000	subtract	0110
R-type	10	and	0000000	111	AND	0000
R-type	10	or	0000000	110	OR	0001


FIGURE 4.45 A copy of **Figure 4.12**. This figure shows how the ALU control bits are set depending on the ALUOp control bits and the different opcodes for the R-type instruction.

Signal name	Effect when deasserted	Effect when asserted
RegWrite	None.	The register on the Write register input is written with the value on the Write data input.
ALUSrc	The second ALU operand comes from the second register file output (Read data 2).	The second ALU operand is the sign-extended, 12 bits of the instruction.
PCSrc	The PC is replaced by the output of the adder that computes the value of PC + 4.	The PC is replaced by the output of the adder that computes the branch target.
MemRead	None.	Data memory contents designated by the address input are put on the Read data output.
MemWrite	None.	Data memory contents designated by the address input are replaced by the value on the Write data input.
MemtoReg	The value fed to the register Write data input comes from the ALU.	The value fed to the register Write data input comes from the data memory.

FIGURE 4.46 A copy of **Figure 4.16**. The function of each of six control signals is defined. The ALU control lines (ALUOp) are defined in the second column of **Figure 4.45**. When a 1-bit control to a two-way multiplexor is asserted, the multiplexor selects the input corresponding to 1. Otherwise, if the control is deasserted, the multiplexor selects the 0 input. Note that PCSrc is controlled by an AND gate in **Figure 4.44**. If the Branch signal and the ALU Zero signal are both set, then PCSrc is 1; otherwise, it is 0. Control sets the Branch signal only during a beq instruction; otherwise, PCSrc is set to 0.

Instruction	Execution/address calculation stage control lines		Memory access stage control lines			Write-back stage control lines	
	ALUOp	ALUSrc	Branch	Mem-Read	Mem-Write	Reg-Write	Memto-Reg
R-format	10	0	0	0	0	1	0
ld	00	1	0	1	0	1	1
sd	00	1	0	0	1	0	X
beq	01	0	1	0	0	0	X

FIGURE 4.47 The values of the control lines are the same as in **Figure 4.18**, but they have been shuffled into three groups corresponding to the last three pipeline stages.

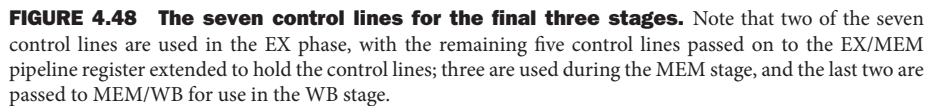

Since the rest of the control lines starts with the EX stage, we can create the control information during instruction decode for the later stages. The simplest way to pass these control signals is to extend the pipeline registers to include control information. [Figure 4.48](#) above shows that these control signals are then used in the appropriate pipeline stage as the instruction moves down the pipeline, just as the destination register number for loads moves down the pipeline in [Figure 4.39](#). [Figure 4.49](#) shows the full datapath with the extended pipeline registers and with the control lines connected to the proper stage. ([Section 4.13](#) gives more examples of RISC-V code executing on pipelined hardware using single-clock diagrams, if you would like to see more details.)

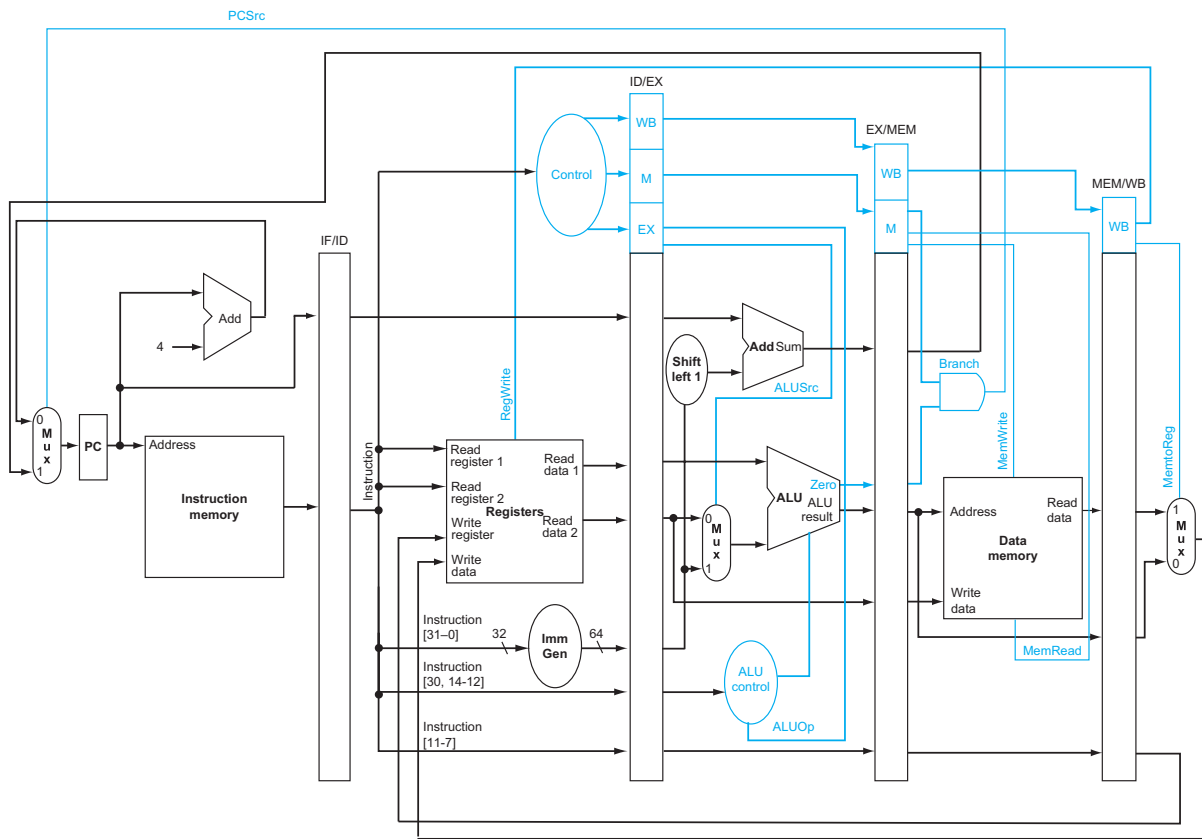


FIGURE 4.49 The pipelined datapath of Figure 4.44, with the control signals connected to the control portions of the pipeline registers. The control values for the last three stages are created during the instruction decode stage and then placed in the ID/EX pipeline register. The control lines for each pipe stage are used, and remaining control lines are then passed to the next pipeline stage.

What do you mean, why's it got to be built? It's a bypass. You've got to build bypasses.

Douglas Adams, *The Hitchhiker's Guide to the Galaxy*, 1979

4.7

Data Hazards: Forwarding versus Stalling

The examples in the previous section show the power of pipelined execution and how the hardware performs the task. It's now time to take off the rose-colored glasses and look at what happens with real programs. The RISC-V instructions in Figures 4.41 through 4.43 were independent; none of them used the results calculated by any of the others. Yet, in Section 4.5, we saw that data hazards are obstacles to pipelined execution.

Let's look at a sequence with many dependences, shown in color:

```
sub  x2, x1, x3    // Register z2 written by sub
and  x12, x2, x5   // 1st operand(x2) depends on sub
or   x13, x6, x2   // 2nd operand(x2) depends on sub
add  x14, x2, x2   // 1st(x2) & 2nd(x2) depend on sub
sd   x15, 100(x2)  // Base (x2) depends on sub
```

The last four instructions are all dependent on the result in register `x2` of the first instruction. If register `x2` had the value 10 before the subtract instruction and `-20` afterwards, the programmer intends that `-20` will be used in the following instructions that refer to register `x2`.

How would this sequence perform with our pipeline? Figure 4.50 illustrates the execution of these instructions using a multiple-clock-cycle pipeline representation. To demonstrate the execution of this instruction sequence in our current pipeline, the top of Figure 4.50 shows the value of register `x2`, which changes during the middle of clock cycle 5, when the `sub` instruction writes its result.

The last potential hazard can be resolved by the design of the register file hardware: What happens when a register is read and written in the same clock cycle? We assume that the write is in the first half of the clock cycle and the read is in the second half, so the read delivers what is written. As is the case for many implementations of register files, we have no data hazard in this case.

Figure 4.50 shows that the values read for register `x2` would *not* be the result of the `sub` instruction unless the read occurred during clock cycle 5 or later. Thus, the instructions that would get the correct value of `-20` are `add` and `sd`; the `and` and `or` instructions would get the incorrect value 10! Using this style of drawing, such problems become apparent when a dependence line goes backward in time.

As mentioned in Section 4.5, the desired result is available at the end of the EX stage of the `sub` instruction or clock cycle 3. When are the data actually needed by the `and` and `or` instructions? The answer is at the beginning of the EX stage of the `and` and `or` instructions, or clock cycles 4 and 5, respectively. Thus, we can execute this segment without stalls if we simply *forward* the data as soon as it is available to any units that need it before it is ready to read from the register file.

How does forwarding work? For simplicity in the rest of this section, we consider only the challenge of forwarding to an operation in the EX stage, which may be either an ALU operation or an effective address calculation. This means that when an instruction tries to use a register in its EX stage that an earlier instruction intends to write in its WB stage, we actually need the values as inputs to the ALU.

A notation that names the fields of the pipeline registers allows for a more precise notation of dependences. For example, “ID/EX.RegisterRs1” refers to the number of one register whose value is found in the pipeline register ID/EX; that is, the one from the first read port of the register file. The first part of the name,

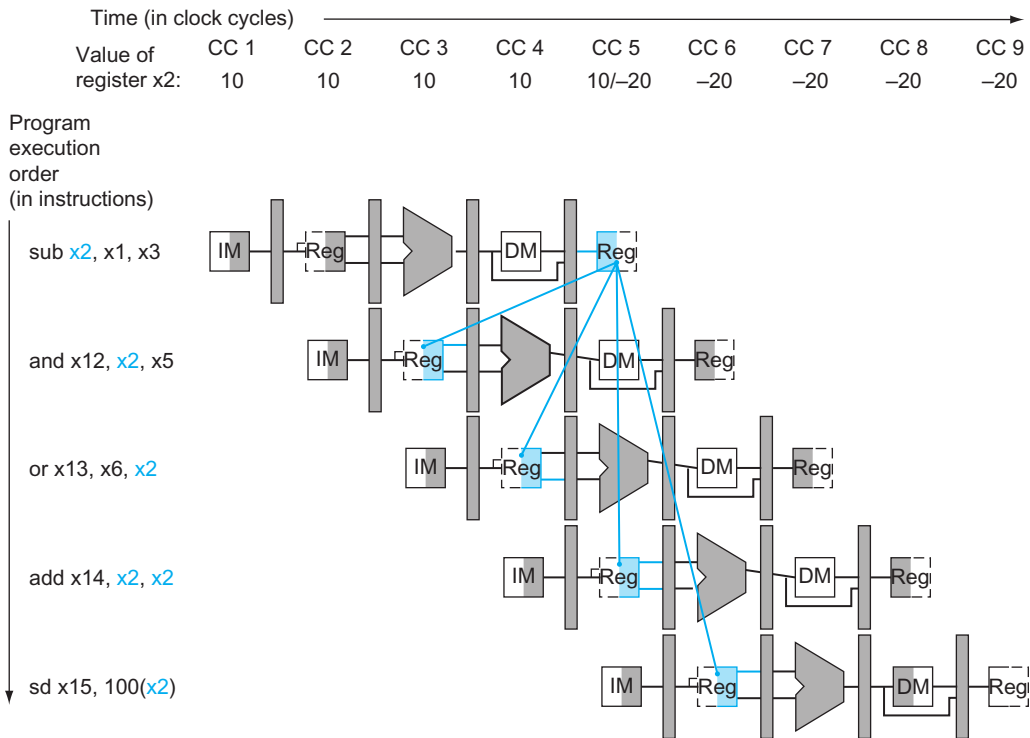


FIGURE 4.50 Pipelined dependences in a five-instruction sequence using simplified datapaths to show the dependences. All the dependent actions are shown in color, and “CC 1” at the top of the figure means clock cycle 1. The first instruction writes into x2, and all the following instructions read x2. This register is written in clock cycle 5, so the proper value is unavailable before clock cycle 5. (A read of a register during a clock cycle returns the value written at the end of the first half of the cycle, when such a write occurs.) The colored lines from the top datapath to the lower ones show the dependences. Those that must go backward in time are *pipeline data hazards*.

to the left of the period, is the name of the pipeline register; the second part is the name of the field in that register. Using this notation, the two pairs of hazard conditions are

- 1a. EX/MEM.RegisterRd = ID/EX.RegisterRs1
- 1b. EX/MEM.RegisterRd = ID/EX.RegisterRs2
- 2a. MEM/WB.RegisterRd = ID/EX.RegisterRs1
- 2b. MEM/WB.RegisterRd = ID/EX.RegisterRs2

The first hazard in the sequence on page 295 is on register x2, between the result of `sub x2, x1, x3` and the first read operand of `and x12, x2, x5`. This hazard can

be detected when the `and` instruction is in the EX stage and the prior instruction is in the MEM stage, so this is hazard 1a:

$$\text{EX/MEM.RegisterRd} = \text{ID/EX.RegisterRs1} = x2$$

Dependence Detection

Classify the dependences in this sequence from page 295:

```
sub x2, x1, x3      // Register x2 set by sub
and x12, x2, x5     // 1st operand(x2) set by sub
or x13, x6, x2      // 2nd operand(x2) set by sub
add x14, x2, x2      // 1st(x2) & 2nd(x2) set by sub
sd x15, 100(x2)     // Index(x2) set by sub
```

As mentioned above, the `sub-and` is a type 1a hazard. The remaining hazards are as follows:

- The `sub-or` is a type 2b hazard:

$$\text{MEM/WB.RegisterRd} = \text{ID/EX.RegisterRs2} = x2$$

- The two dependences on `sub-add` are not hazards because the register file supplies the proper data during the ID stage of `add`.
- There is no data hazard between `sub` and `sd` because `sd` reads `x2` the clock cycle *after* `sub` writes `x2`.

Because some instructions do not write registers, this policy is inaccurate; sometimes it would forward when it shouldn't. One solution is simply to check to see if the `RegWrite` signal will be active: examining the WB control field of the pipeline register during the EX and MEM stages determines whether `RegWrite` is asserted. Recall that RISC-V requires that every use of `x0` as an operand must yield an operand value of 0. If an instruction in the pipeline has `x0` as its destination (for example, `addi x0, x1, 2`), we want to avoid forwarding its possibly nonzero result value. Not forwarding results destined for `x0` frees the assembly programmer and the compiler of any requirement to avoid using `x0` as a destination. The conditions above thus work properly as long as we add `EX/MEM.RegisterRd ≠ 0` to the first hazard condition and `MEM/WB.RegisterRd ≠ 0` to the second.

Now that we can detect hazards, half of the problem is resolved—but we must still forward the proper data.

Figure 4.51 shows the dependences between the pipeline registers and the inputs to the ALU for the same code sequence as in Figure 4.50. The change is that the

EXAMPLE

ANSWER

dependence begins from a *pipeline* register, rather than waiting for the WB stage to write the register file. Thus, the required data exist in time for later instructions, with the pipeline registers holding the data to be forwarded.

If we can take the inputs to the ALU from *any* pipeline register rather than just ID/EX, then we can forward the correct data. By adding multiplexors to the input of the ALU, and with the proper controls, we can run the pipeline at full speed in the presence of these data hazards.

For now, we will assume the only instructions we need to forward are the four R-format instructions: add, sub, and, and or. Figure 4.52 shows a close-up of the ALU and pipeline register before and after adding forwarding. Figure 4.53



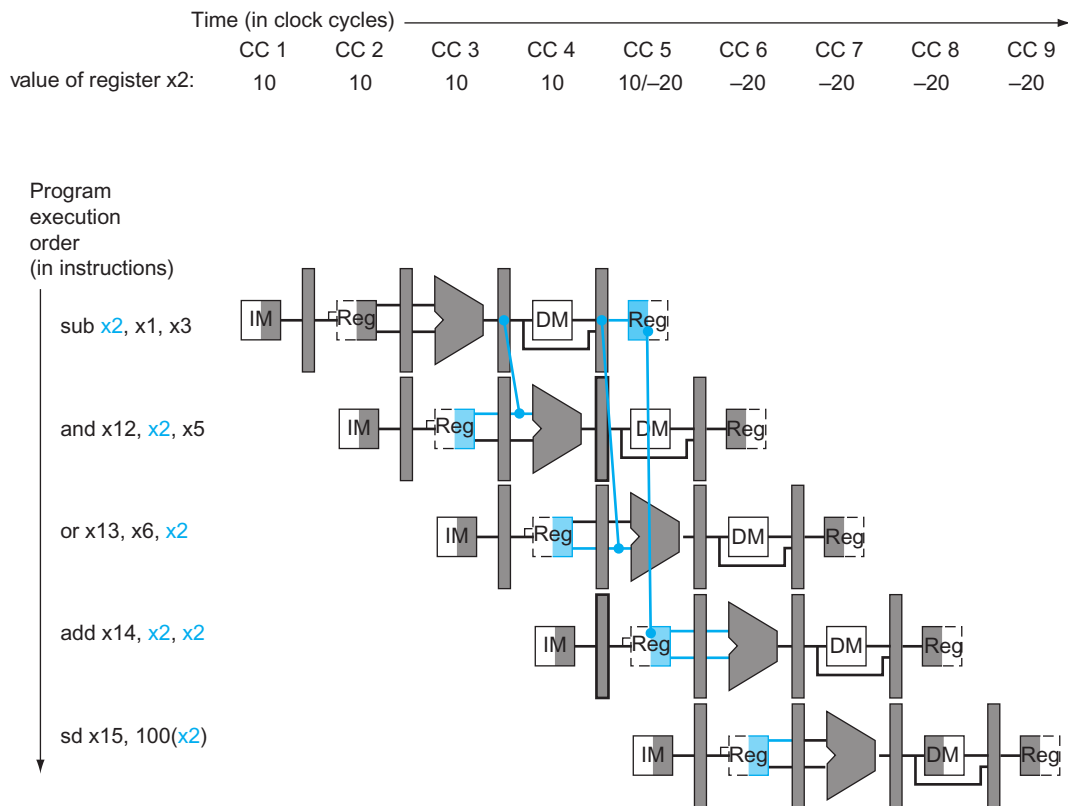


FIGURE 4.51 The dependences between the pipeline registers move forward in time, so it is possible to supply the inputs to the ALU needed by the `and` instruction and `or` instruction by forwarding the results found in the pipeline registers. The values in the pipeline registers show that the desired value is available before it is written into the register file. We assume that the register file forwards values that are read and written during the same clock cycle, so the `add` does not stall, but the values come from the register file instead of a pipeline register. Register file “forwarding”—that is, the read gets the value of the write in that clock cycle—is why clock cycle 5 shows register x2 having the value 10 at the beginning and -20 at the end of the clock cycle.

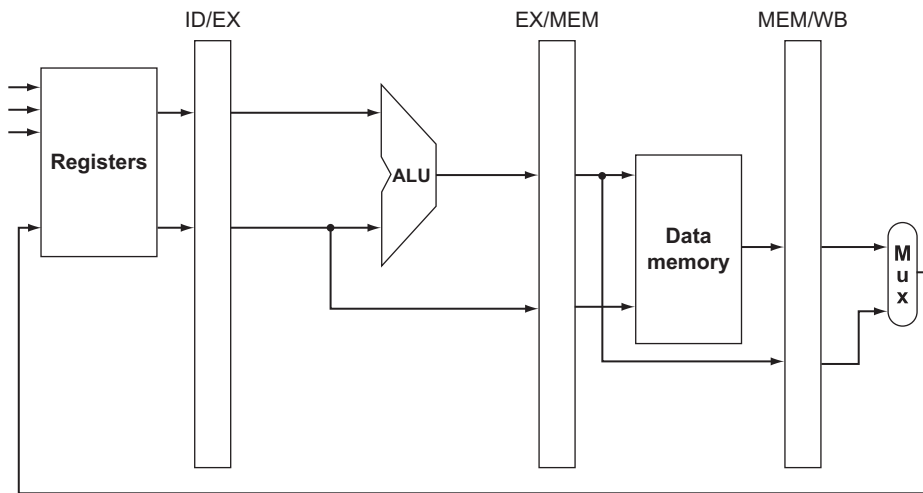

a. No forwarding

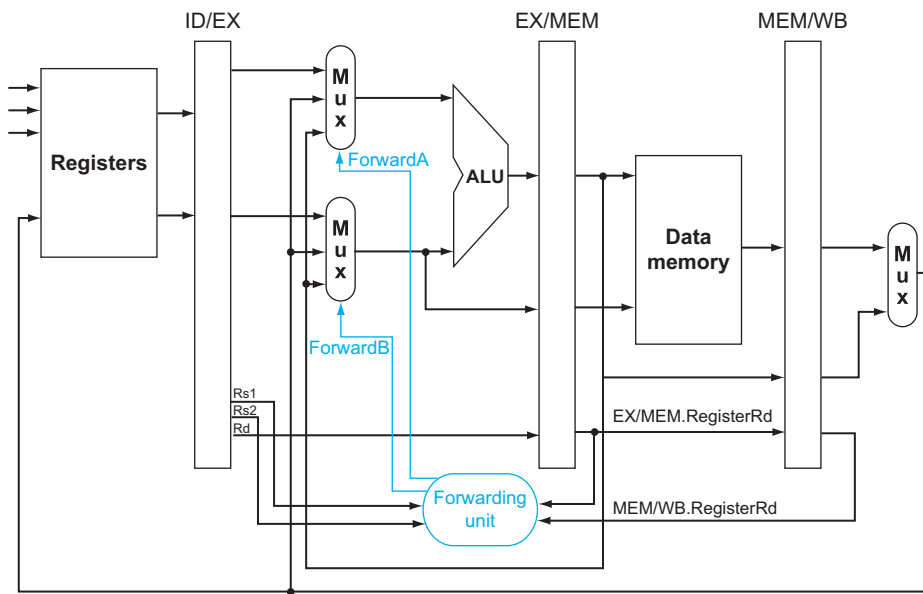

b. With forwarding

FIGURE 4.52 On the top are the ALU and pipeline registers before adding forwarding. On the bottom, the multiplexors have been expanded to add the forwarding paths, and we show the forwarding unit. The new hardware is shown in color. This figure is a stylized drawing, however, leaving out details from the full datapath such as the sign extension hardware.

Mux control	Source	Explanation
ForwardA = 00	ID/EX	The first ALU operand comes from the register file.
ForwardA = 10	EX/MEM	The first ALU operand is forwarded from the prior ALU result.
ForwardA = 01	MEM/WB	The first ALU operand is forwarded from data memory or an earlier ALU result.
ForwardB = 00	ID/EX	The second ALU operand comes from the register file.
ForwardB = 10	EX/MEM	The second ALU operand is forwarded from the prior ALU result.
ForwardB = 01	MEM/WB	The second ALU operand is forwarded from data memory or an earlier ALU result.

FIGURE 4.53 The control values for the forwarding multiplexors in Figure 4.52. The signed immediate that is another input to the ALU is described in the *Elaboration* at the end of this section.

shows the values of the control lines for the ALU multiplexors that select either the register file values or one of the forwarded values.

This forwarding control will be in the EX stage, because the ALU forwarding multiplexors are found in that stage. Thus, we must pass the operand register numbers from the ID stage via the ID/EX pipeline register to determine whether to forward values. Before forwarding, the ID/EX register had no need to include space to hold the rs1 and rs2 fields. Hence, they were added to ID/EX.

Let's now write both the conditions for detecting hazards, and the control signals to resolve them:

1. *EX hazard:*

```

if (EX/MEM.RegWrite
and (EX/MEM.RegisterRd ≠ 0)
and (EX/MEM.RegisterRd = ID/EX.RegisterRs1)) ForwardA = 10
if (EX/MEM.RegWrite
and (EX/MEM.RegisterRd ≠ 0)
and (EX/MEM.RegisterRd = ID/EX.RegisterRs2)) ForwardB = 10

```

This case forwards the result from the previous instruction to either input of the ALU. If the previous instruction is going to write to the register file, and the write register number matches the read register number of ALU inputs A or B, provided it is not register 0, then steer the multiplexor to pick the value instead from the pipeline register EX/MEM.

2. *MEM hazard:*

```

if (MEM/WB.RegWrite
and (MEM/WB.RegisterRd ≠ 0)
and (MEM/WB.RegisterRd = ID/EX.RegisterRs1)) ForwardA = 01

```

```

if (MEM/WB.RegWrite
and (MEM/WB.RegisterRd ≠ 0)
and (MEM/WB.RegisterRd = ID/EX.RegisterRs2)) ForwardB = 01

```

As mentioned above, there is no hazard in the WB stage, because we assume that the register file supplies the correct result if the instruction in the ID stage reads the same register written by the instruction in the WB stage. Such a register file performs another form of forwarding, but it occurs within the register file.

One complication is potential data hazards between the result of the instruction in the WB stage, the result of the instruction in the MEM stage, and the source operand of the instruction in the ALU stage. For example, when summing a vector of numbers in a single register, a sequence of instructions will all read and write to the same register:

```

add x1, x1, x2
add x1, x1, x3
add x1, x1, x4
. . .

```

In this case, the result should be forwarded from the MEM stage because the result in the MEM stage is the more recent result. Thus, the control for the MEM hazard would be (with the additions highlighted):


```

if (MEM/WB.RegWrite
and (MEM/WB.RegisterRd ≠ 0)
and not(EX/MEM.RegWrite and (EX/MEM.RegisterRd ≠ 0)
        and (EX/MEM.RegisterRd = ID/EX.RegisterRs1))
and (MEM/WB.RegisterRd = ID/EX.RegisterRs1)) ForwardA = 01

if (MEM/WB.RegWrite
and (MEM/WB.RegisterRd ≠ 0)
and not(EX/MEM.RegWrite and (EX/MEM.RegisterRd ≠ 0)
        and (EX/MEM.RegisterRd = ID/EX.RegisterRs2))
and (MEM/WB.RegisterRd = ID/EX.RegisterRs2)) ForwardB = 01

```

Figure 4.54 shows the hardware necessary to support forwarding for operations that use results during the EX stage. Note that the EX/MEM.RegisterRd field is the register destination for either an ALU instruction or a load.

If you would like to see more illustrated examples using single-cycle pipeline drawings,  [Section 4.13](#) has figures that show two pieces of RISC-V code with hazards that cause forwarding.

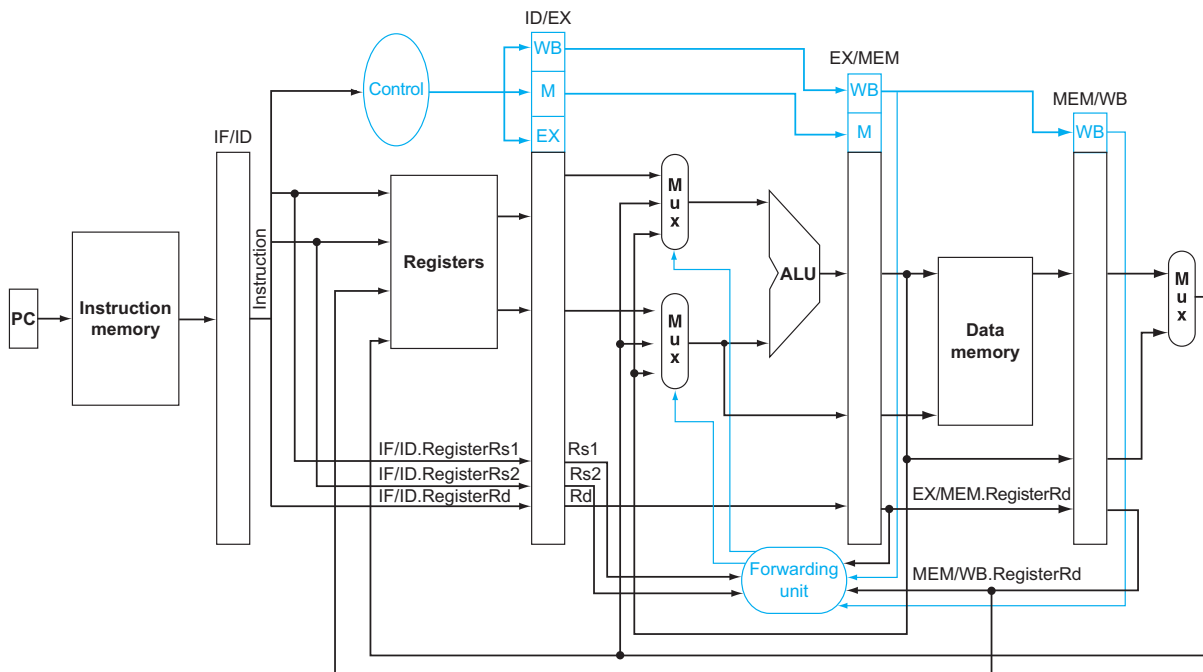


FIGURE 4.54 The datapath modified to resolve hazards via forwarding. Compared with the datapath in Figure 4.49, the additions are the multiplexors to the inputs to the ALU. This figure is a more stylized drawing, however, leaving out details from the full datapath, such as the branch hardware and the sign extension hardware.

Elaboration: Forwarding can also help with hazards when store instructions are dependent on other instructions. Since they use just one data value during the MEM stage, forwarding is easy. However, consider loads immediately followed by stores, useful when performing memory-to-memory copies in the RISC-V architecture. Since copies are frequent, we need to add more forwarding hardware to make them run faster. If we were to redraw Figure 4.51, replacing the `sub` and `and` instructions with `ld` and `sd`, we would see that it is possible to avoid a stall, since the data exist in the MEM/WB register of a load instruction in time for its use in the MEM stage of a store instruction. We would need to add forwarding into the memory access stage for this option. We leave this modification as an exercise to the reader.

In addition, the signed-immediate input to the ALU, needed by loads and stores, is missing from the datapath in Figure 4.54. Since central control decides between register and immediate, and since the forwarding unit chooses the pipeline register for a register input to the ALU, the easiest solution is to add a 2:1 multiplexor that chooses between the ForwardB multiplexor output and the signed immediate. Figure 4.55 shows this addition.

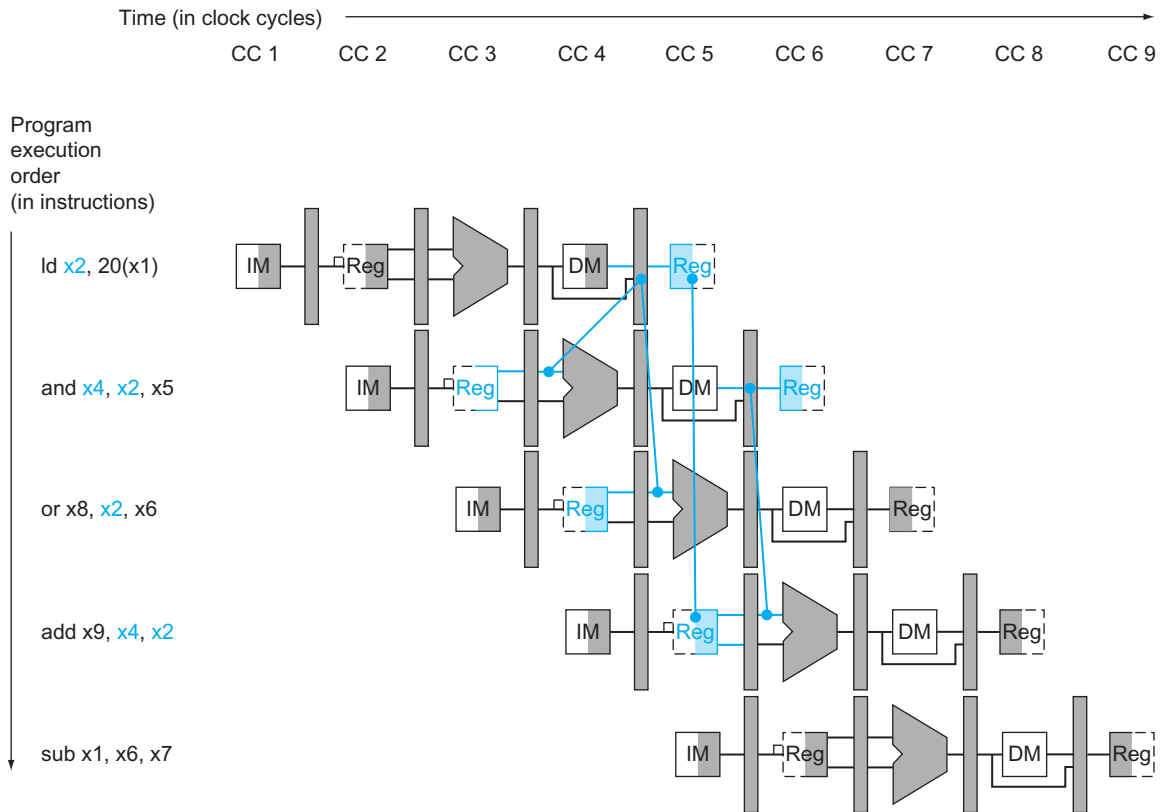


FIGURE 4.56 A pipelined sequence of instructions. Since the dependence between the load and the following instruction (*and*) goes backward in time, this hazard cannot be solved by forwarding. Hence, this combination must result in a stall by the hazard detection unit.

Recall that we are using the RegisterRd to refer the register specified in instruction bits 11:7 for both load and R-type instructions. The first line tests to see if the instruction is a load: the only instruction that reads data memory is a load. The next two lines check to see if the destination register field of the load in the EX stage matches either source register of the instruction in the ID stage. If the condition holds, the instruction stalls one clock cycle. After this one-cycle stall, the forwarding logic can handle the dependence and execution proceeds. (If there were no forwarding, then the instructions in [Figure 4.56](#) would need another stall cycle.)

If the instruction in the ID stage is stalled, then the instruction in the IF stage must also be stalled; otherwise, we would lose the fetched instruction. Preventing these two instructions from making progress is accomplished simply by preventing the PC register and the IF/ID pipeline register from changing. Provided these registers are preserved, the instruction in the IF stage will continue to be read using the same PC, and the registers in the ID stage will continue to be read using

a water pipe, a stall bubble delays everything behind it and proceeds down the instruction pipe one stage each clock cycle until it exits at the end. In this example, the hazard forces the and and or instructions to repeat in clock cycle 4 what they did in clock cycle 3: and reads registers and decodes, and or is refetched from instruction memory. Such repeated work is what a stall looks like, but its effect is to stretch the time of the and and or instructions and delay the fetch of the add instruction.

Figure 4.58 highlights the pipeline connections for both the hazard detection unit and the forwarding unit. As before, the forwarding unit controls the ALU multiplexors to replace the value from a general-purpose register with the value from the proper pipeline register. The hazard detection unit controls the writing of the PC and IF/ID registers plus the multiplexor that chooses between the real control values and all 0s. The hazard detection unit stalls and deasserts the control fields if the load-use hazard test above is true. If you would like to see more details, [Section 4.13](#) gives an example illustrated using single-clock pipeline diagrams of RISC-V code with hazards that cause stalling.

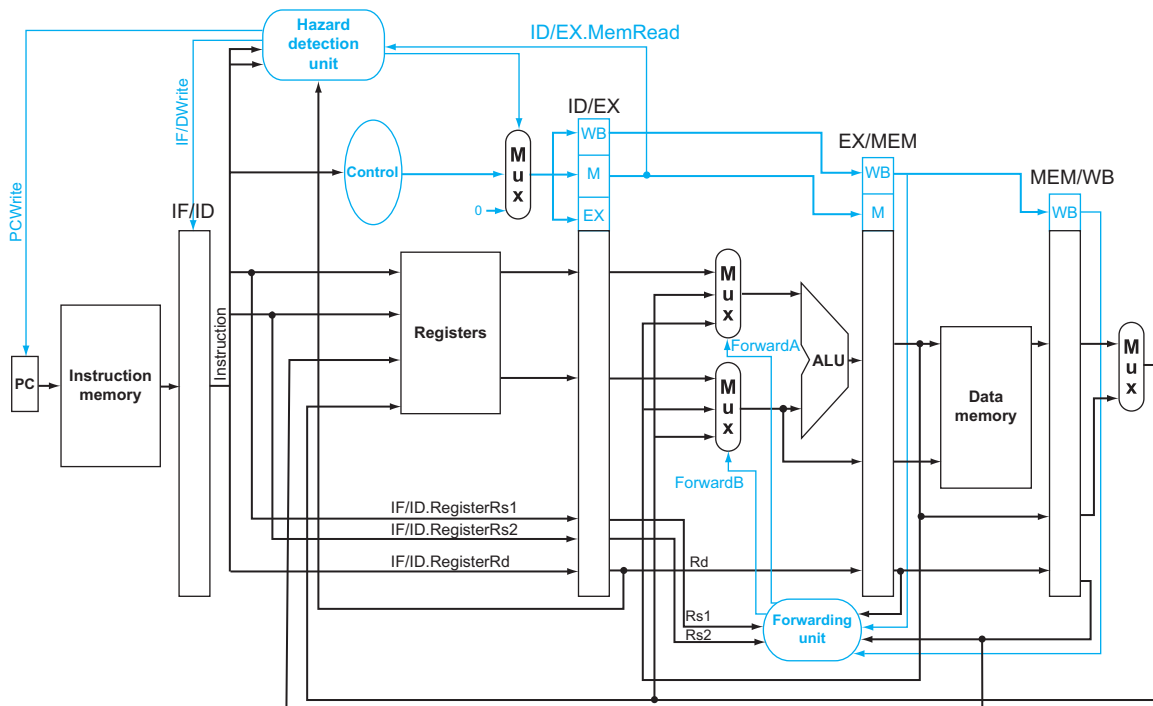


FIGURE 4.58 Pipelined control overview, showing the two multiplexers for forwarding, the hazard detection unit, and the forwarding unit. Although the ID and EX stages have been simplified—the sign-extended immediate and branch logic are missing—this drawing gives the essence of the forwarding hardware requirements.

Although the compiler generally relies upon the hardware to resolve hazards and thereby ensure correct execution, the compiler must understand the pipeline to achieve the best performance. Otherwise, unexpected stalls will reduce the performance of the compiled code.

The BIG Picture

Elaboration: Regarding the remark earlier about setting control lines to 0 to avoid writing registers or memory: only the signals RegWrite and MemWrite need be 0, while the other control signals can be don't cares.

4.8 Control Hazards

Thus far, we have limited our concern to hazards involving arithmetic operations and data transfers. However, as we saw in [Section 4.5](#), there are also pipeline hazards involving conditional branches. [Figure 4.59](#) shows a sequence of instructions and indicates when the branch would occur in this pipeline. An instruction must be fetched at every clock cycle to sustain the pipeline, yet in our design the decision about whether to branch doesn't occur until the MEM pipeline stage. As mentioned in [Section 4.5](#), this delay in determining the proper instruction to fetch is called a *control hazard* or *branch hazard*, in contrast to the *data hazards* we have just examined.


This section on control hazards is shorter than the previous sections on data hazards. The reasons are that control hazards are relatively simple to understand, they occur less frequently than data hazards, and there is nothing as effective against control hazards as forwarding is against data hazards. Hence, we use simpler schemes. We look at two schemes for resolving control hazards and one optimization to improve these schemes.

Assume Branch Not Taken

As we saw in [Section 4.5](#), stalling until the branch is complete is too slow. One improvement over branch stalling is to **predict** that the conditional branch will not be taken and thus continue execution down the sequential instruction stream. If the conditional branch is taken, the instructions that are being fetched and decoded must be discarded. Execution continues at the branch target. If conditional branches are untaken half the time, and if it costs little to discard the instructions, this optimization halves the cost of control hazards.

*There are a thousand
hacking at the
branches of evil to one
who is striking at the
root.*

Henry David Thoreau,
Walden, 1854

 

PREDICTION

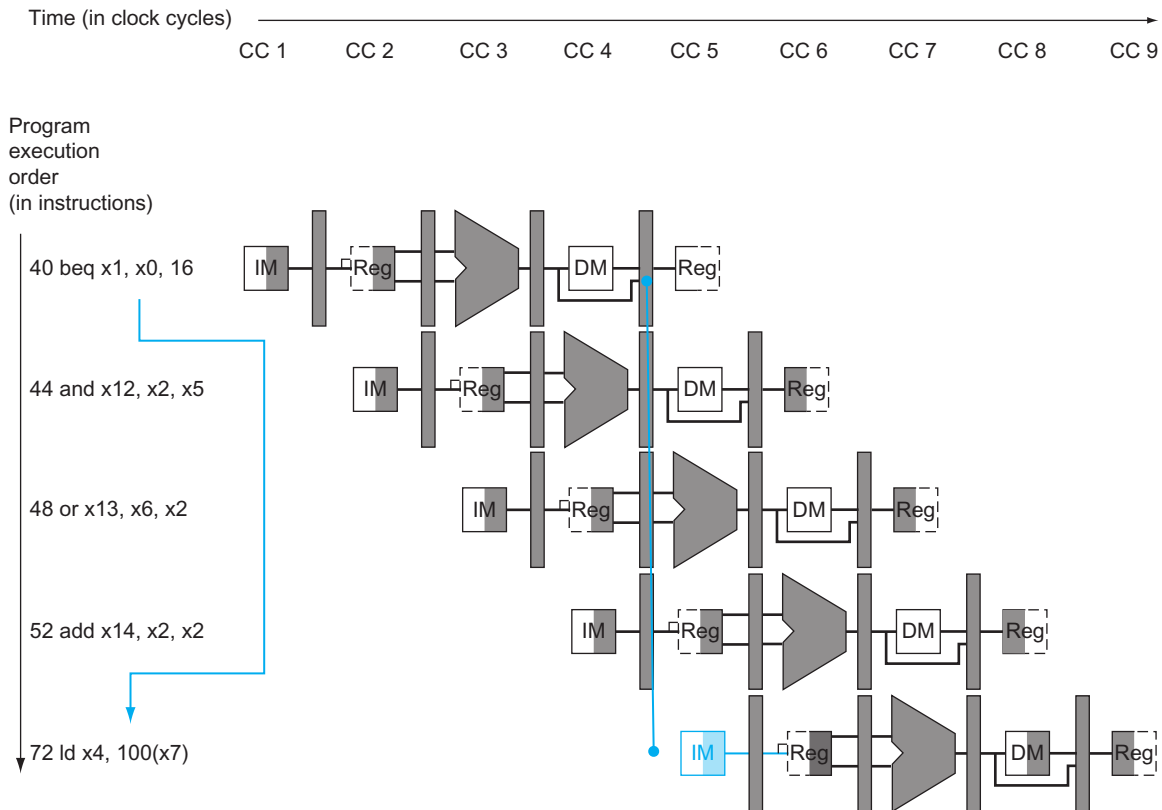


FIGURE 4.59 The impact of the pipeline on the branch instruction. The numbers to the left of the instruction (40, 44, ...) are the addresses of the instructions. Since the branch instruction decides whether to branch in the MEM stage—clock cycle 4 for the `beq` instruction above—the three sequential instructions that follow the branch will be fetched and begin execution. Without intervention, those three following instructions will begin execution before `beq` branches to `ld` at location 72. (Figure 4.29 assumed extra hardware to reduce the control hazard to one clock cycle; this figure uses the nonoptimized datapath.)

flush To discard instructions in a pipeline, usually due to an unexpected event.

To discard instructions, we merely change the original control values to 0s, much as we did to stall for a load-use data hazard. The difference is that we must also change the three instructions in the IF, ID, and EX stages when the branch reaches the MEM stage; for load-use stalls, we just change control to 0 in the ID stage and let them percolate through the pipeline. Discarding instructions, then, means we must be able to **flush** instructions in the IF, ID, and EX stages of the pipeline.

Reducing the Delay of Branches

One way to improve conditional branch performance is to reduce the cost of the taken branch. Thus far, we have assumed the next PC for a branch is selected in the

MEM stage, but if we move the conditional branch execution earlier in the pipeline, then fewer instructions need be flushed. Moving the branch decision up requires two actions to occur earlier: computing the branch target address and evaluating the branch decision. The easy part of this change is to move up the branch address calculation. We already have the PC value and the immediate field in the IF/ID pipeline register, so we just move the branch adder from the EX stage to the ID stage; of course, the address calculation for branch targets will be performed for all instructions, but only used when needed.

The harder part is the branch decision itself. For branch if equal, we would compare two register reads during the ID stage to see if they are equal. Equality can be tested by XORing individual bit positions of two registers and ORing the XORed result. Moving the branch test to the ID stage implies additional forwarding and hazard detection hardware, since a branch dependent on a result still in the pipeline must still work properly with this optimization. For example, to implement branch if equal (and its inverse), we will need to forward results to the equality test logic that operates during ID. There are two complicating factors:

1. During ID, we must decode the instruction, decide whether a bypass to the equality test unit is needed, and complete the equality test so that if the instruction is a branch, we can set the PC to the branch target address. Forwarding for the operand of branches was formerly handled by the ALU forwarding logic, but the introduction of the equality test unit in ID will require new forwarding logic. Note that the bypassed source operands of a branch can come from either the EX/MEM or MEM/WB pipeline registers.
2. Because the value in a branch comparison is needed during ID but may be produced later in time, it is possible that a data hazard can occur and a stall will be needed. For example, if an ALU instruction immediately preceding a branch produces the operand for the test in the conditional branch, a stall will be required, since the EX stage for the ALU instruction will occur after the ID cycle of the branch. By extension, if a load is immediately followed by a conditional branch that depends on the load result, two stall cycles will be needed, as the result from the load appears at the end of the MEM cycle but is needed at the beginning of ID for the branch.

Despite these difficulties, moving the conditional branch execution to the ID stage is an improvement, because it reduces the penalty of a branch to only one instruction if the branch is taken, namely, the one currently being fetched. The exercises explore the details of implementing the forwarding path and detecting the hazard.

To flush instructions in the IF stage, we add a control line, called IF.Flush, that zeros the instruction field of the IF/ID pipeline register. Clearing the register transforms the fetched instruction into a `nop`, an instruction that has no action and changes no state.

EXAMPLE**Pipelined Branch**

Show what happens when the branch is taken in this instruction sequence, assuming the pipeline is optimized for branches that are not taken, and that we moved the branch execution to the ID stage:

```

36  sub  x10, x4, x8
40  beq  x1,  x3, 16 // PC-relative branch to 40+16*2=72
44  and  x12, x2, x5
48  or   x13, x2, x6
52  add  x14, x4, x2
56  sub  x15, x6, x7
   . . .
72  ld   x4, 50(x7)

```

ANSWER

Figure 4.60 shows what happens when a conditional branch is taken. Unlike Figure 4.59, there is only one pipeline bubble on a taken branch.



PREDICTION

dynamic branch

prediction Prediction of branches at runtime using runtime information.

branch prediction

buffer Also called **branch history** table. A small memory that is indexed by the lower portion of the address of the branch instruction and that contains one or more bits indicating whether the branch was recently taken or not.

Dynamic Branch Prediction

Assuming a conditional branch is not taken is one simple form of *branch prediction*. In that case, we predict that conditional branches are untaken, flushing the pipeline when we are wrong. For the simple five-stage pipeline, such an approach, possibly coupled with compiler-based prediction, is probably adequate. With deeper pipelines, the branch penalty increases when measured in clock cycles. Similarly, with multiple issue (see Section 4.10), the branch penalty increases in terms of instructions lost. This combination means that in an aggressive pipeline, a simple static prediction scheme will probably waste too much performance. As we mentioned in Section 4.5, with more hardware it is possible to try to **predict** branch behavior during program execution.

One approach is to look up the address of the instruction to see if the conditional branch was taken the last time this instruction was executed, and, if so, to begin fetching new instructions from the same place as the last time. This technique is called **dynamic branch prediction**.

One implementation of that approach is a **branch prediction buffer** or **branch history** table. A branch prediction buffer is a small memory indexed by the lower portion of the address of the branch instruction. The memory contains a bit that says whether the branch was recently taken or not.

This prediction uses the simplest sort of buffer; we don't know, in fact, if the prediction is the right one—it may have been put there by another conditional branch that has the same low-order address bits. However, this doesn't affect correctness. Prediction is just a hint that we hope is correct, so fetching begins in the predicted direction. If the hint turns out to be wrong, the incorrectly predicted

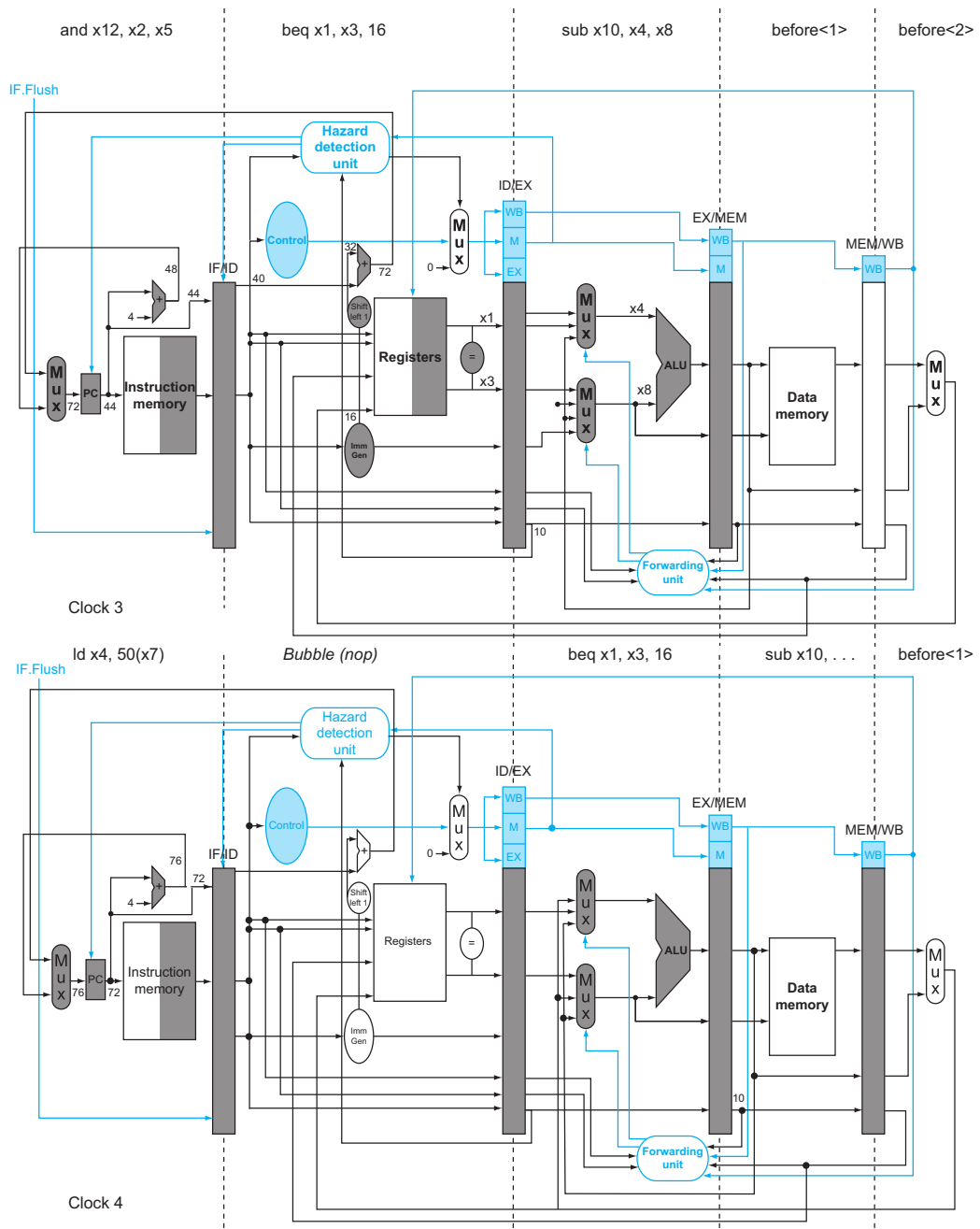


FIGURE 4.60 The ID stage of clock cycle 3 determines that a branch must be taken, so it selects 72 as the next PC address and zeros the instruction fetched for the next clock cycle. Clock cycle 4 shows the instruction at location 72 being fetched and the single bubble or *nop* instruction in the pipeline because of the taken branch.

instructions are deleted, the prediction bit is inverted and stored back, and the proper sequence is fetched and executed.

This simple 1-bit prediction scheme has a performance shortcoming: even if a conditional branch is almost always taken, we can predict incorrectly twice, rather than once, when it is not taken. The following example shows this dilemma.

EXAMPLE

Loops and Prediction

Consider a loop branch that branches nine times in a row, and then is not taken once. What is the prediction accuracy for this branch, assuming the prediction bit for this branch remains in the prediction buffer?

ANSWER

The steady-state prediction behavior will mispredict on the first and last loop iterations. Mispredicting the last iteration is inevitable since the prediction bit will indicate taken, as the branch has been taken nine times in a row at that point. The misprediction on the first iteration happens because the bit is flipped on prior execution of the last iteration of the loop, since the branch was not taken on that exiting iteration. Thus, the prediction accuracy for this branch that is taken 90% of the time is only 80% (two incorrect predictions and eight correct ones).

Ideally, the accuracy of the predictor would match the taken branch frequency for these highly regular branches. To remedy this weakness, 2-bit prediction schemes are often used. In a 2-bit scheme, a prediction must be wrong twice before it is changed. [Figure 4.61](#) shows the finite-state machine for a 2-bit prediction scheme.

A branch prediction buffer can be implemented as a small, special buffer accessed with the instruction address during the IF pipe stage. If the instruction is predicted as taken, fetching begins from the target as soon as the PC is known; as mentioned on page 308, it can be as early as the ID stage. Otherwise, sequential fetching and executing continue. If the prediction turns out to be wrong, the prediction bits are changed as shown in [Figure 4.61](#).

Elaboration: A branch predictor tells us whether a conditional branch is taken, but still requires the calculation of the branch target. In the five-stage pipeline, this calculation takes one cycle, meaning that taken branches will have a one-cycle penalty. One approach is to use a cache to hold the destination program counter or destination instruction using a [branch target buffer](#).

The 2-bit dynamic prediction scheme uses only information about a particular branch. Researchers noticed that using information about both a local branch and the global behavior of recently executed branches together yields greater prediction accuracy for the same number of prediction bits. Such predictors are called [correlating predictors](#). A typical correlating predictor might have two 2-bit

branch target buffer

A structure that caches the destination PC or destination instruction for a branch. It is usually organized as a cache with tags, making it more costly than a simple prediction buffer.

correlating predictor

A branch predictor that combines local behavior of a particular branch and global information about the behavior of some recent number of executed branches.

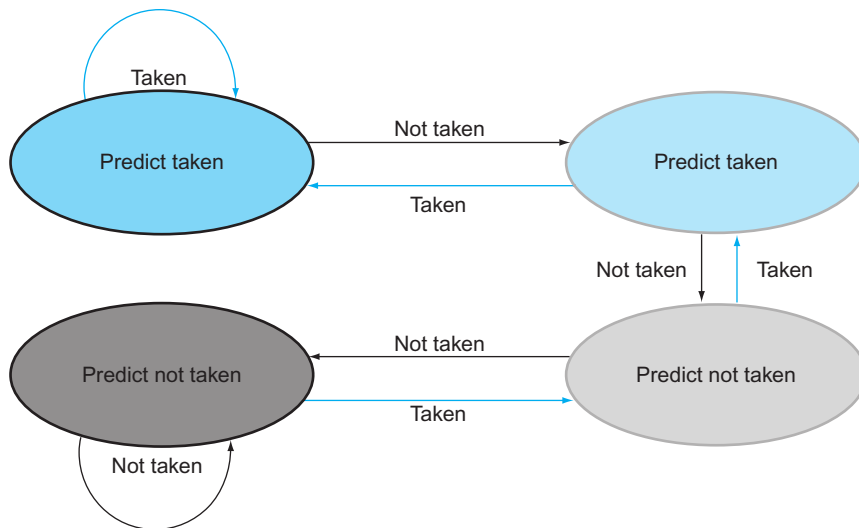


FIGURE 4.61 The states in a 2-bit prediction scheme. By using 2 bits rather than 1, a branch that strongly favors taken or not taken—as many branches do—will be mispredicted only once. The 2 bits are used to encode the four states in the system. The 2-bit scheme is a general instance of a counter-based predictor, which is incremented when the prediction is accurate and decremented otherwise, and uses the mid-point of its range as the division between taken and not taken.

predictors for each branch, with the choice between predictors made based on whether the last executed branch was taken or not taken. Thus, the global branch behavior can be thought of as adding additional index bits for the prediction lookup.

Another approach to branch prediction is the use of tournament predictors. A **tournament branch predictor** uses multiple predictors, tracking, for each branch, which predictor yields the best results. A typical tournament predictor might contain two predictions for each branch index: one based on local information and one based on global branch behavior. A selector would choose which predictor to use for any given prediction. The selector can operate similarly to a 1- or 2-bit predictor, favoring whichever of the two predictors has been more accurate. Some recent microprocessors use such ensemble predictors.

tournament branch predictor A branch predictor with multiple predictions for each branch and a selection mechanism that chooses which predictor to enable for a given branch.

Elaboration: One way to reduce the number of conditional branches is to add *conditional move* instructions. Instead of changing the PC with a conditional branch, the instruction conditionally changes the destination register of the move. For example, the ARMv8 instruction set architecture has a conditional select instruction called `CSEL`. It specifies a destination register, two source registers, and a condition. The destination register gets a value of the first operand if the condition is true and the second operand otherwise. Thus, `CSEL X8, X11, X4, NE` copies the contents of register 11 into register 8 if the condition codes say the result of the operation was not equal zero or a copy of register 4 into register 11 if it was zero. Hence, programs using the ARMv8 instruction set could have fewer conditional branches than programs written in RISC-V.

Pipeline Summary

We started in the laundry room, showing principles of pipelining in an everyday setting. Using that analogy as a guide, we explained instruction pipelining step-by-step, starting with the single-cycle datapath and then adding pipeline registers, forwarding paths, data hazard detection, branch prediction, and flushing instructions on mispredicted branches or load-use data hazards. [Figure 4.62](#) shows the final evolved datapath and control. We now are ready for yet another control hazard: the sticky issue of exceptions.

Check Yourself

Consider three branch prediction schemes: predict not taken, predict taken, and dynamic prediction. Assume that they all have zero penalty when they predict correctly and two cycles when they are wrong. Assume that the average predict accuracy of the dynamic predictor is 90%. Which predictor is the best choice for the following branches?

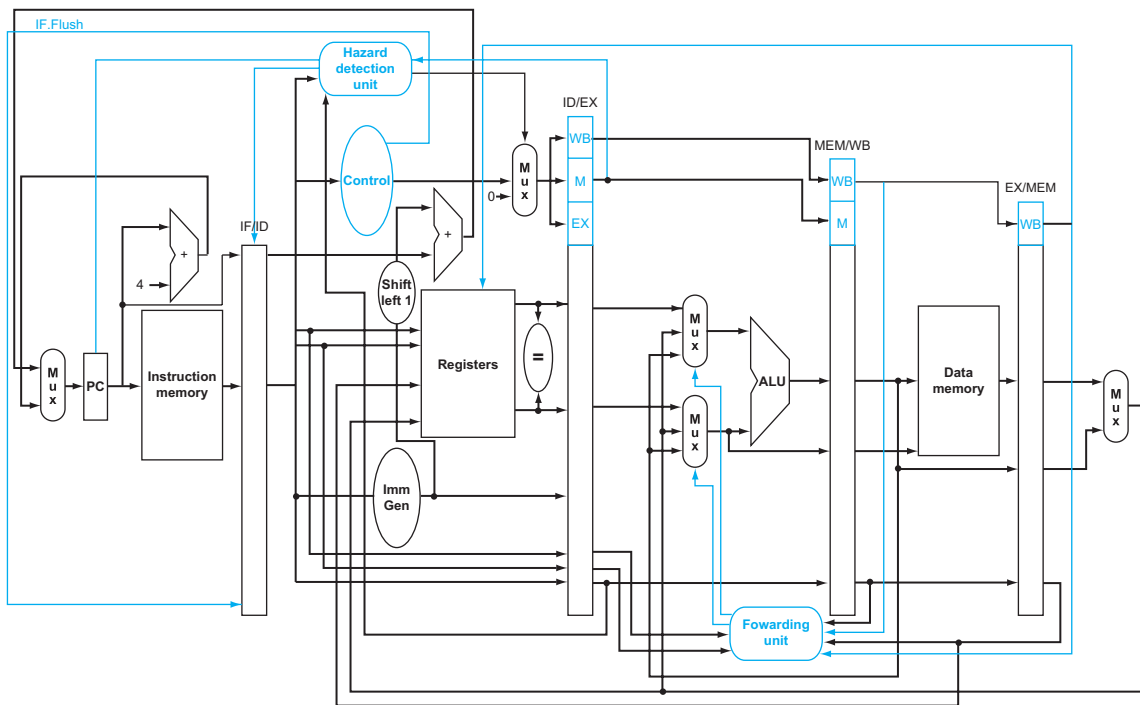


FIGURE 4.62 The final datapath and control for this chapter. Note that this is a stylized figure rather than a detailed datapath, so it's missing the ALUSrc Mux from [Figure 4.55](#) and the multiplexor controls from [Figure 4.49](#).

1. A conditional branch that is taken with 5% frequency
2. A conditional branch that is taken with 95% frequency
3. A conditional branch that is taken with 70% frequency

4.9 Exceptions

Control is the most challenging aspect of processor design: it is both the hardest part to get right and the toughest part to make fast. One of the demanding tasks of control is implementing **exceptions** and **interrupts**—events other than branches that change the normal flow of instruction execution. They were initially created to handle unexpected events from within the processor, like an undefined instruction. The same basic mechanism was extended for I/O devices to communicate with the processor, as we will see in [Chapter 5](#).

Many architectures and authors do not distinguish between interrupts and exceptions, often using either name to refer to both types of events. For example, the Intel x86 uses interrupt. We use the term *exception* to refer to *any* unexpected change in control flow without distinguishing whether the cause is internal or external; we use the term *interrupt* only when the event is externally caused. Here are examples showing whether the situation is internally generated by the processor or externally generated and the name that RISC-V uses:

Type of event	From where?	RISC-V terminology
System reset	External	Exception
I/O device request	External	Interrupt
Invoke the operating system from user program	Internal	Exception
Using an undefined instruction	Internal	Exception
Hardware malfunctions	Either	Either

Many of the requirements to support exceptions come from the specific situation that causes an exception to occur. Accordingly, we will return to this topic in [Chapter 5](#), when we will better understand the motivation for additional capabilities in the exception mechanism. In this section, we deal with the control implementation for detecting types of exceptions that arise from the portions of the instruction set and implementation that we have already discussed.

Detecting exceptional conditions and taking the appropriate action is often on the critical timing path of a processor, which determines the clock cycle time and thus performance. Without proper attention to exceptions during design of the control unit, attempts to add exceptions to an intricate implementation can significantly reduce performance, as well as complicate the task of getting the design correct.

To make a computer with automatic program-interruption facilities behave [sequentially] was not an easy matter, because the number of instructions in various stages of processing when an interrupt signal occurs may be large.

Fred Brooks, Jr.,
Planning a Computer System: Project Stretch,
1962

exception Also called **interrupt**. An unscheduled event that disrupts program execution; used to detect undefined instructions.

interrupt An exception that comes from outside of the processor. (Some architectures use the term *interrupt* for all exceptions.)

How Exceptions are Handled in the RISC-V Architecture

The only types of exceptions that our current implementation can generate are execution of an undefined instruction or a hardware malfunction. We'll assume a hardware malfunction occurs during the instruction `add x11, x12, x11` as the example exception in the next few pages. The basic action that the processor must perform when an exception occurs is to save the address of the unfortunate instruction in the *supervisor exception cause register* (SEPC) and then transfer control to the operating system at some specified address.

The operating system can then take the appropriate action, which may involve providing some service to the user program, taking some predefined action in response to a malfunction, or stopping the execution of the program and reporting an error. After performing whatever action is required because of the exception, the operating system can terminate the program or may continue its execution, using the SEPC to determine where to restart the execution of the program. In [Chapter 5](#), we will look more closely at the issue of restarting the execution.

For the operating system to handle the exception, it must know the reason for the exception, in addition to the instruction that caused it. There are two main methods used to communicate the reason for an exception. The method used in the RISC-V architecture is to include a register (called the *Supervisor Exception Cause Register* or *SCAUSE*), which holds a field that indicates the reason for the exception.

vectored interrupt An interrupt for which the address to which control is transferred is determined by the cause of the exception.

A second method is to use **vectored interrupts**. In a vectored interrupt, the address to which control is transferred is determined by the cause of the exception, possibly added to a base register that points to memory range for vectored interrupts. For example, we might define the following exception vector addresses to accommodate these exception types:

Exception type	Exception vector address to be added to a Vector Table Base Register
Undefined instruction	00 0100 0000 _{two}
System Error (hardware malfunction)	01 1000 0000 _{two}

The operating system knows the reason for the exception by the address at which it is initiated. When the exception is not vectored, as in RISC-V, a single entry point for all exceptions can be used, and the operating system decodes the status register to find the cause. For architectures with vectored exceptions, the addresses might be separated by, say, 32 bytes or eight instructions, and the operating system must record the reason for the exception and may perform some limited processing in this sequence.

We can perform the processing required for exceptions by adding a few extra registers and control signals to our basic implementation and by slightly extending control. Let's assume that we are implementing the exception system with the single interrupt entry point being the address `0000 0000 1C09 0000hex`. (Implementing

vectored exceptions is no more difficult.) We will need to add two additional registers to our current RISC-V implementation:

- **SEPC**: A 64-bit register used to hold the address of the affected instruction. (Such a register is needed even when exceptions are vectored.)
- **SCAUSE**: A register used to record the cause of the exception. In the RISC-V architecture, this register is 64 bits, although most bits are currently unused. Assume there is a field that encodes the two possible exception sources mentioned above, with 2 representing an undefined instruction and 12 representing hardware malfunction.

Exceptions in a Pipelined Implementation

A pipelined implementation treats exceptions as another form of control hazard. For example, suppose there is a hardware malfunction in an add instruction. Just as we did for the taken branch in the previous section, we must flush the instructions that follow the add instruction from the pipeline and begin fetching instructions from the new address. We will use the same mechanism we used for taken branches, but this time the exception causes the deasserting of control lines.

When we dealt with branch misprediction, we saw how to flush the instruction in the IF stage by turning it into a nop. To flush instructions in the ID stage, we use the multiplexor already in the ID stage that zeros control signals for stalls. A new control signal, called ID.Flush, is ORed with the stall signal from the hazard detection unit to flush during ID. To flush the instruction in the EX phase, we use a new signal called EX.Flush to cause new multiplexors to zero the control lines. To start fetching instructions from location 0000 0000 1C09 0000_{hex}, which we are using as the RISC-V exception address, we simply add an additional input to the PC multiplexor that sends 0000 0000 1C09 0000_{hex} to the PC. [Figure 4.63](#) shows these changes.

This example points out a problem with exceptions: if we do not stop execution in the middle of the instruction, the programmer will not be able to see the original value of register x1 because it will be clobbered as the destination register of the add instruction. If we assume the exception is detected during the EX stage, we can use the EX.Flush signal to prevent the instruction in the EX stage from writing its result in the WB stage. Many exceptions require that we eventually complete the instruction that caused the exception as if it executed normally. The easiest way to do this is to flush the instruction and restart it from the beginning after the exception is handled.

The final step is to save the address of the offending instruction in the *supervisor exception program counter* (SEPC). [Figure 4.63](#) shows a stylized version of the datapath, including the branch hardware and necessary accommodations to handle exceptions.

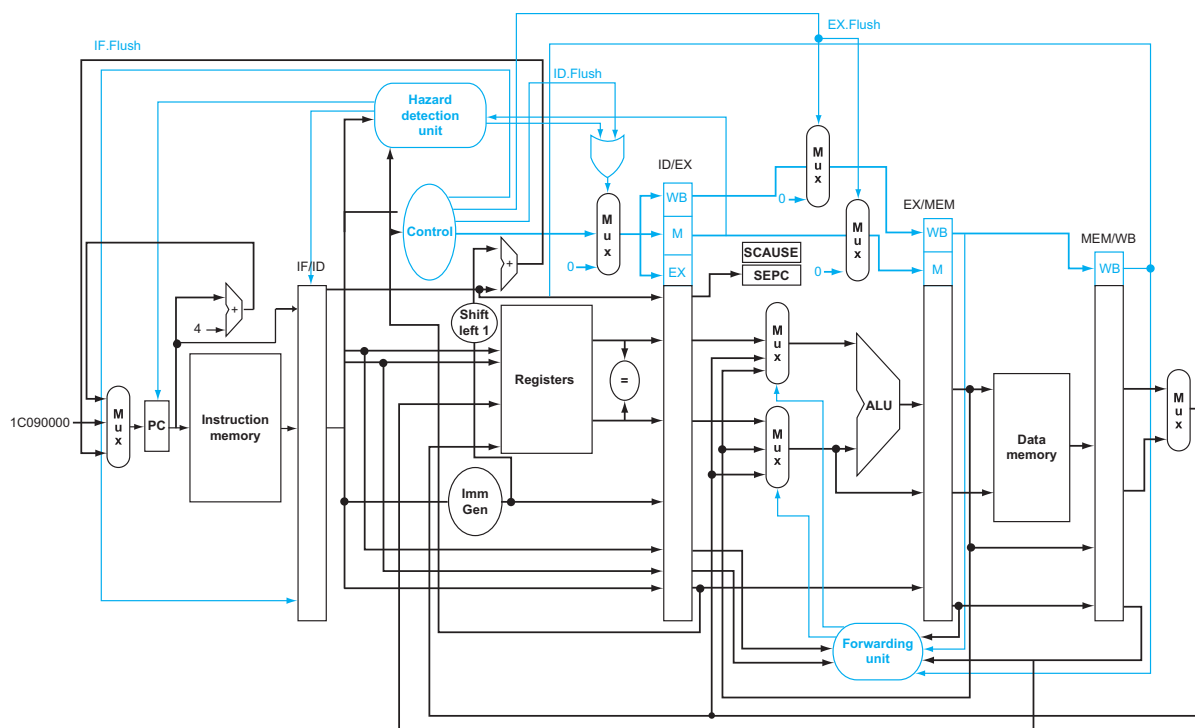


FIGURE 4.63 The datapath with controls to handle exceptions. The key additions include a new input with the value 0000 0000 1C09 0000_{hex} in the multiplexor that supplies the new PC value; an SCAUSE register to record the cause of the exception; and an SEPC register to save the address of the instruction that caused the exception. The 0000 0000 1C09 0000_{hex} input to the multiplexor is the initial address to begin fetching instructions in the event of an exception.

EXAMPLE

Exception in a Pipelined Computer

Given this instruction sequence,

```

40hex sub    x11, x2, x4
44hex and    x12, x2, x5
48hex or     x13, x2, x6
4Chex add    x1,  x2, x1
50hex sub    x15, x6, x7
54hex ld     x16, 100(x7)
. . .

```

assume the instructions to be invoked on an exception begin like this:

```

1C090000hex sd    x26, 1000(x10)
1C090004hex sd    x27, 1008(x10)
. . .

```

Show what happens in the pipeline if a hardware malfunction exception occurs in the `add` instruction.

Figure 4.64 shows the events, starting with the `add` instruction in the EX stage. Assume the hardware malfunction is detected during that phase, and `0000 0000 1C09 0000`_{hex} is forced into the PC. Clock cycle 7 shows that the `add` and following instructions are flushed, and the first instruction of the exception-handling code is fetched. Note that the address of the `add` instruction is saved: `4C`_{hex}.

ANSWER

We mentioned several examples of exceptions on page 315, and we will see others in Chapter 5. With five instructions active in any clock cycle, the challenge is to associate an exception with the appropriate instruction. Moreover, multiple exceptions can occur simultaneously in a single clock cycle. The solution is to prioritize the exceptions so that it is easy to determine which is serviced first. In RISC-V implementations, the hardware sorts exceptions so that the earliest instruction is interrupted.

I/O device requests and hardware malfunctions are not associated with a specific instruction, so the implementation has some flexibility as to when to interrupt the pipeline. Hence, the mechanism used for other exceptions works just fine.

The SEPC register captures the address of the interrupted instructions, and the SCAUSE register records the highest priority exception in a clock cycle if more than one exception occurs.

The hardware and the operating system must work in conjunction so that exceptions behave as you would expect. The hardware contract is normally to stop the offending instruction in midstream, let all prior instructions complete, flush all following instructions, set a register to show the cause of the exception, save the address of the offending instruction, and then branch to a prearranged address. The operating system contract is to look at the cause of the exception and act appropriately. For an undefined instruction or hardware failure, the operating system normally kills the program and returns an indicator of the reason. For an I/O device request or an operating system service call, the operating system saves the state of the program, performs the desired task, and, at some point in the future, restores the program to continue execution. In the case of I/O device requests, we may often choose to run another task before resuming the task that requested the I/O, since that task may often not be able to proceed until the I/O is complete. Exceptions are why the ability to save and restore the state of any task is critical. One of the most important and frequent uses of exceptions is handling page faults; Chapter 5 describes these exceptions and their handling in more detail.

**Hardware/
Software
Interface**

 


FIGURE 4.64 The result of an exception due to hardware malfunction in the `add` instruction. The exception is detected during the EX stage of clock 6, saving the address of the `add` instruction in the SEPC register (`4C_hex`). It causes all the Flush signals to be set near the end of this clock cycle, deasserting control values (setting them to 0) for the `add`. Clock cycle 7 shows the instructions converted to bubbles in the pipeline plus the fetching of the first instruction of the exception routine—`sd x26, 1000(x0)`—from instruction location `0000 0000 1C09 0000_hex`. Note that the `and` and `or` instructions, which are prior to the `add`, still complete.

Elaboration: The difficulty of always associating the proper exception with the correct instruction in pipelined computers has led some computer designers to relax this requirement in noncritical cases. Such processors are said to have **imprecise interrupts** or **imprecise exceptions**. In the example above, PC would normally have 58_{hex} at the start of the clock cycle after the exception is detected, even though the offending instruction is at address $4C_{\text{hex}}$. A processor with imprecise exceptions might put 58_{hex} into SEPC and leave it up to the operating system to determine which instruction caused the problem. RISC-V and the vast majority of computers today support **precise interrupts** or **precise exceptions**. One reason is designers of a deeper pipeline processor might be tempted to record a different value in SEPC, which would create headaches for the OS. To prevent them, the deeper pipeline would likely be required to record the same PC that would have been recorded in the five-stage pipeline. It is simpler for everyone to just record the PC of the faulting instruction instead. (Another reason is to support virtual memory, which we shall see in [Chapter 5](#).)

Elaboration: We show that RISC-V uses the exception entry address $0000\ 0000\ 1C09\ 0000_{\text{hex}}$, which is chosen somewhat arbitrarily. Many RISC-V computers store the exception entry address in a special register named *Supervisor Trap Vector* (STVEC), which the OS can load with a value of its choosing.

imprecise interrupt Also called **imprecise exception**. Interrupts or exceptions in pipelined computers that are not associated with the exact instruction that was the cause of the interrupt or exception.

precise interrupt Also called **precise exception**. An interrupt or exception that is always associated with the correct instruction in pipelined computers.

Which exception should be recognized first in this sequence?


1. `xxx x11, x12, x11` // undefined instruction
2. `sub x11, x12, x11` // hardware error

Check Yourself

 4.10 Parallelism via Instructions

Be forewarned: this section is a brief overview of fascinating but complex topics. If you want to learn more details, you should consult our more advanced book, *Computer Architecture: A Quantitative Approach*, fifth edition, where the material covered in these 13 pages is expanded to almost 200 pages (including appendices)!

Pipelining exploits the potential **parallelism** among instructions. This parallelism is called, naturally enough, **instruction-level parallelism (ILP)**. There are two primary methods for increasing the potential amount of instruction-level parallelism. The first is increasing the depth of the pipeline to overlap more instructions. Using our laundry analogy and assuming that the washer cycle was longer than the others were, we could divide our washer into three machines that perform the wash, rinse, and spin steps of a traditional washer. We would then



PIPELINING



PARALLELISM

instruction-level parallelism

The parallelism among instructions.

multiple issue

A scheme whereby multiple instructions are launched in one clock cycle.

static multiple issue An approach to implementing a multiple-issue processor where many decisions are made by the compiler before execution.

dynamic multiple issue

An approach to implementing a multiple-issue processor where many decisions are made during execution by the processor.

issue slots The positions from which instructions could issue in a given clock cycle; by analogy, these correspond to positions at the starting blocks for a sprint.

move from a four-stage to a six-stage pipeline. To get the full speed-up, we need to rebalance the remaining steps so they are the same length, in processors or in laundry. The amount of parallelism being exploited is higher, since there are more operations being overlapped. Performance is potentially greater since the clock cycle can be shorter.

Another approach is to replicate the internal components of the computer so that it can launch multiple instructions in every pipeline stage. The general name for this technique is **multiple issue**. A multiple-issue laundry would replace our household washer and dryer with, say, three washers and three dryers. You would also have to recruit more assistants to fold and put away three times as much laundry in the same amount of time. The downside is the extra work to keep all the machines busy and transferring the loads to the next pipeline stage.

Launching multiple instructions per stage allows the instruction execution rate to exceed the clock rate or, stated alternatively, the CPI to be less than 1. As mentioned in [Chapter 1](#), it is sometimes useful to flip the metric and use *IPC*, or *instructions per clock cycle*. Hence, a 3-GHz four-way multiple-issue microprocessor can execute a peak rate of 12 billion instructions per second and have a best-case CPI of 0.33, or an IPC of 3. Assuming a five-stage pipeline, such a processor would have up to 20 instructions in execution at any given time. Today's high-end microprocessors attempt to issue from three to six instructions in every clock cycle. Even moderate designs will aim at a peak IPC of 2. There are typically, however, many constraints on what types of instructions may be executed simultaneously, and what happens when dependences arise.

There are two main ways to implement a multiple-issue processor, with the major difference being the division of work between the compiler and the hardware. Because the division of work dictates whether decisions are being made statically (that is, at compile time) or dynamically (that is, during execution), the approaches are sometimes called **static multiple issue** and **dynamic multiple issue**. As we will see, both approaches have other, more commonly used names, which may be less precise or more restrictive.

Two primary and distinct responsibilities must be dealt with in a multiple-issue pipeline:

1. Packaging instructions into **issue slots**: how does the processor determine how many instructions and which instructions can be issued in a given clock cycle? In most static issue processors, this process is at least partially handled by the compiler; in dynamic issue designs, it is normally dealt with at runtime by the processor, although the compiler will often have already tried to help improve the issue rate by placing the instructions in a beneficial order.
2. Dealing with data and control hazards: in static issue processors, the compiler handles some or all the consequences of data and control hazards statically. In contrast, most dynamic issue processors attempt to alleviate at least some classes of hazards using hardware techniques operating at execution time.

Although we describe these as distinct approaches, in reality, one approach often borrows techniques from the other, and neither approach can claim to be perfectly pure.


The Concept of Speculation

One of the most important methods for finding and exploiting more ILP is speculation. Based on the great idea of **prediction**, **speculation** is an approach that allows the compiler or the processor to “guess” about the properties of an instruction, to enable execution to begin for other instructions that may depend on the speculated instruction. For example, we might speculate on the outcome of a branch, so that instructions after the branch could be executed earlier. Another example is that we might speculate that a store that precedes a load does not refer to the same address, which would allow the load to be executed before the store. The difficulty with speculation is that it may be wrong. So, any speculation mechanism must include both a method to check if the guess was right and a method to unroll or back out the effects of the instructions that were executed speculatively. The implementation of this back-out capability adds complexity.

Speculation may be done in the compiler or by the hardware. For example, the compiler can use speculation to reorder instructions, moving an instruction across a branch or a load across a store. The processor hardware can perform the same transformation at runtime using techniques we discuss later in this section.

The recovery mechanisms used for incorrect speculation are rather different. In the case of speculation in software, the compiler usually inserts additional instructions that check the accuracy of the speculation and provide a fix-up routine to use when the speculation is wrong. In hardware speculation, the processor usually buffers the speculative results until it knows they are no longer speculative. If the speculation is correct, the instructions are completed by allowing the contents of the buffers to be written to the registers or memory. If the speculation is incorrect, the hardware flushes the buffers and re-executes the correct instruction sequence. Misspeculation typically requires the pipeline to be flushed, or at least stalled, and thus further reduces performance.

Speculation introduces one other possible problem: speculating on certain instructions may introduce exceptions that were formerly not present. For example, suppose a load instruction is moved in a speculative manner, but the address it uses is not within bounds when the speculation is incorrect. The result would be that an exception that should not have occurred would occur. The problem is complicated by the fact that if the load instruction were not speculative, then the exception must occur! In compiler-based speculation, such problems are avoided by adding special speculation support that allows such exceptions to be ignored until it is clear that they really should occur. In hardware-based speculation, exceptions are simply buffered until it is clear that the instruction causing them is no longer speculative and is ready to complete; at that point, the exception is raised, and normal exception handling proceeds.

 

PREDICTION

speculation An approach whereby the compiler or processor guesses the outcome of an instruction to remove it as a dependence in executing other instructions.

Since speculation can improve performance when done properly and decrease performance when done carelessly, significant effort goes into deciding when it is appropriate to speculate. Later in this section, we will examine both static and dynamic techniques for speculation.

Static Multiple Issue

issue packet The set of instructions that issues together in one clock cycle; the packet may be determined statically by the compiler or dynamically by the processor.

Very Long Instruction Word (VLIW) A style of instruction set architecture that launches many operations that are defined to be independent in a single-wide instruction, typically with many separate opcode fields.

Static multiple-issue processors all use the compiler to assist with packaging instructions and handling hazards. In a static issue processor, you can think of the set of instructions issued in a given clock cycle, which is called an **issue packet**, as one large instruction with multiple operations. This view is more than an analogy. Since a static multiple-issue processor usually restricts what mix of instructions can be initiated in a given clock cycle, it is useful to think of the issue packet as a single instruction allowing several operations in certain predefined fields. This view led to the original name for this approach: **Very Long Instruction Word (VLIW)**.

Most static issue processors also rely on the compiler to take on some responsibility for handling data and control hazards. The compiler's responsibilities may include static branch prediction and code scheduling to reduce or prevent all hazards. Let's look at a simple static issue version of an RISC-V processor, before we describe the use of these techniques in more aggressive processors.

An Example: Static Multiple Issue with the RISC-V ISA

To give a flavor of static multiple issue, we consider a simple two-issue RISC-V processor, where one of the instructions can be an integer ALU operation or branch and the other can be a load or store. Such a design is like that used in some embedded processors. Issuing two instructions per cycle will require fetching and decoding 64 bits of instructions. In many static multiple-issue processors, and essentially all VLIW processors, the layout of simultaneously issuing instructions is restricted to simplify the decoding and instruction issue. Hence, we will require that the instructions be paired and aligned on a 64-bit boundary, with the ALU or branch portion appearing first. Furthermore, if one instruction of the pair cannot be used, we require that it be replaced with a `nop`. Thus, the instructions always issue in pairs, possibly with a `nop` in one slot. [Figure 4.65](#) shows how the instructions look as they go into the pipeline in pairs.

Static multiple-issue processors vary in how they deal with potential data and control hazards. In some designs, the compiler takes full responsibility for removing *all* hazards, scheduling the code, and inserting no-ops so that the code executes without any need for hazard detection or hardware-generated stalls. In others, the hardware detects data hazards and generates stalls between two issue packets, while requiring that the compiler avoid all dependences within an instruction packet. Even so, a hazard generally forces the entire issue packet containing the dependent instruction to stall. Whether the software must handle all hazards or only try to reduce the fraction of hazards between separate issue packets, the appearance of

Instruction type	Pipe stages							
ALU or branch instruction	IF	ID	EX	MEM	WB			
Load or store instruction	IF	ID	EX	MEM	WB			
ALU or branch instruction		IF	ID	EX	MEM	WB		
Load or store instruction		IF	ID	EX	MEM	WB		
ALU or branch instruction			IF	ID	EX	MEM	WB	
Load or store instruction			IF	ID	EX	MEM	WB	
ALU or branch instruction				IF	ID	EX	MEM	WB
Load or store instruction				IF	ID	EX	MEM	WB

FIGURE 4.65 Static two-issue pipeline in operation. The ALU and data transfer instructions are issued at the same time. Here we have assumed the same five-stage structure as used for the single-issue pipeline. Although this is not strictly necessary, it does have some advantages. In particular, keeping the register writes at the end of the pipeline simplifies the handling of exceptions and the maintenance of a precise exception model, which become more difficult in multiple-issue processors.

having a large single instruction with multiple operations is reinforced. We will assume the second approach for this example.

To issue an ALU and a data transfer operation in parallel, the first need for additional hardware—beyond the usual hazard detection and stall logic—is extra ports in the register file (see Figure 4.66). In one clock cycle, we may need to read two registers for the ALU operation and two more for a store, and also one write port for an ALU operation and one write port for a load. Since the ALU is tied up for the ALU operation, we also need a separate adder to calculate the effective address for data transfers. Without these extra resources, our two-issue pipeline would be hindered by structural hazards.

Clearly, this two-issue processor can improve performance by up to a factor of two! Doing so, however, requires that twice as many instructions be overlapped in execution, and this additional overlap increases the relative performance loss from data and control hazards. For example, in our simple five-stage pipeline, loads have a **use latency** of one clock cycle, which prevents one instruction from using the result without stalling. In the two-issue, five-stage pipeline the result of a load instruction cannot be used on the next *clock cycle*. This means that the next *two* instructions cannot use the load result without stalling. Furthermore, ALU instructions that had no use latency in the simple five-stage pipeline now have a one-instruction use latency, since the results cannot be used in the paired load or store. To effectively exploit the parallelism available in a multiple-issue processor, more ambitious compiler or hardware scheduling techniques are needed, and static multiple issue requires that the compiler take on this role.

use latency Number of clock cycles between a load instruction and an instruction that can use the result of the load without stalling the pipeline.

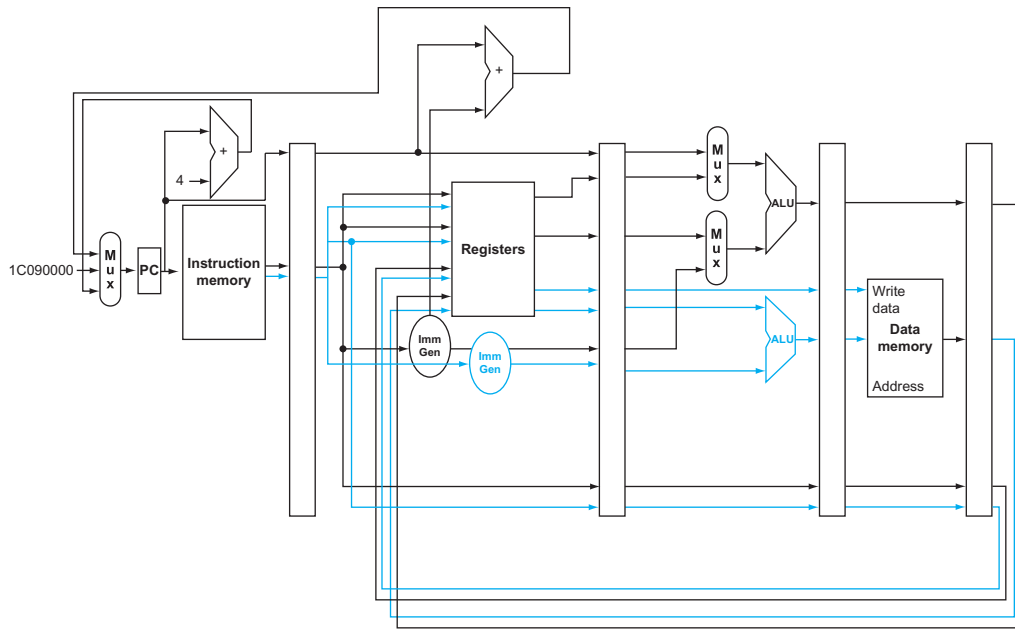


FIGURE 4.66 A static two-issue datapath. The additions needed for double issue are highlighted: another 32 bits from instruction memory, two more read ports and one more write port on the register file, and another ALU. Assume the bottom ALU handles address calculations for data transfers and the top ALU handles everything else.

EXAMPLE

Simple Multiple-Issue Code Scheduling

How would this loop be scheduled on a static two-issue pipeline for RISC-V?

```

Loop: ld    x31, 0(x20)    // x31=array element
      add   x31, x31, x21  // add scalar in x21
      sd    x31, 0(x20)    // store result
      addi  x20, x20, -8   // decrement pointer
      blt   x22, x20, Loop // compare to loop limit,
                          // branch if x20 > x22
  
```

Reorder the instructions to avoid as many pipeline stalls as possible. Assume branches are predicted, so that control hazards are handled by the hardware.

ANSWER

The first three instructions have data dependences, as do the next two. [Figure 4.67](#) shows the best schedule for these instructions. Notice that just one pair of instructions has both issue slots used. It takes five clocks per loop iteration; at four clocks to execute five instructions, we get the disappointing CPI of 0.8 versus the best case of 0.5, or an IPC of 1.25 versus 2.0. Notice that in computing CPI or IPC, we do not count any nops executed as useful instructions. Doing so would improve CPI, but not performance!

	ALU or branch instruction	Data transfer instruction	Clock cycle
Loop:		ld x31, 0(x20)	1
	addi x20, x20, -8		2
	add x31, x31, x21		3
	blt x22, x20, Loop	sd x31, 8(x20)	4

FIGURE 4.67 The scheduled code as it would look on a two-issue RISC-V pipeline. The empty slots are no-ops. Note that since we moved the `addi` before the `sd`, we had to adjust `sd`'s offset by 8.

An important compiler technique to get more performance from loops is **loop unrolling**, where multiple copies of the loop body are made. After unrolling, there is more ILP available by overlapping instructions from different iterations.

loop unrolling A technique to get more performance from loops that access arrays, in which multiple copies of the loop body are made and instructions from different iterations are scheduled together.

Loop Unrolling for Multiple-Issue Pipelines

See how well loop unrolling and scheduling work in the example above. For simplicity, assume that the loop index is a multiple of four.

To schedule the loop without any delays, it turns out that we need to make four copies of the loop body. After unrolling and eliminating the unnecessary loop overhead instructions, the loop will contain four copies each of `ld`, `add`, and `sd`, plus one `addi`, and one `blt`. Figure 4.68 shows the unrolled and scheduled code.

During the unrolling process, the compiler introduced additional registers (`x28`, `x29`, `x30`). The goal of this process, called **register renaming**, is to eliminate dependences that are not true data dependences, but could either lead to potential hazards or prevent the compiler from flexibly scheduling the code. Consider how the unrolled code would look using only `x31`. There would be repeated instances of `ld x31, 0(x20)`, `add x31, x31, x21` followed by `sd x31, 8(x20)`, but these sequences, despite using `x31`, are actually completely independent—no data values flow between one set of these instructions and the next set. This case is what is called an **antidependence** or **name dependence**, which is an ordering forced purely by the reuse of a name, rather than a real data dependence that is also called a true dependence.

Renaming the registers during the unrolling process allows the compiler to move these independent instructions subsequently to better schedule the code. The renaming process eliminates the name dependences, while preserving the true dependences.

EXAMPLE

ANSWER

register renaming The renaming of registers by the compiler or hardware to remove antidependences.

antidependence Also called **name dependence** An ordering forced by the reuse of a name, typically a register, rather than by a true dependence that carries a value between two instructions.

	ALU or branch instruction	Data transfer instruction	Clock cycle
Loop:	addi x20, x20, -32	ld x28, 0(x20)	1
		ld x29, 24(x20)	2
	add x28, x28, x21	ld x30, 16(x20)	3
	add x29, x29, x21	ld x31, 8(x20)	4
	add x30, x30, x21	sd x28, 32(x20)	5
	add x31, x31, x21	sd x29, 24(x20)	6
		sd x30, 16(x20)	7
	blt x22, x20, Loop	sd x31, 8(x20)	8

FIGURE 4.68 The unrolled and scheduled code of Figure 4.67 as it would look on a static two-issue RISC-V pipeline. The empty slots are no-ops. Since the first instruction in the loop decrements x20 by 32, the addresses loaded are the original value of x20, then that address minus 8, minus 16, and minus 24.

Notice now that 12 of the 14 instructions in the loop execute as pairs. It takes eight clocks for four loop iterations, which yields an IPC of $14/8 = 1.75$. Loop unrolling and scheduling more than doubled performance—8 versus 20 clock cycles for 4 iterations—partly from reducing the loop control instructions and partly from dual issue execution. The cost of this performance improvement is using four temporary registers rather than one, as well as more than doubling the code size.

Dynamic Multiple-Issue Processors

superscalar An advanced pipelining technique that enables the processor to execute more than one instruction per clock cycle by selecting them during execution.

Dynamic multiple-issue processors are also known as **superscalar** processors, or simply superscalars. In the simplest superscalar processors, instructions issue in order, and the processor decides whether zero, one, or more instructions can issue in a given clock cycle. Obviously, achieving good performance on such a processor still requires the compiler to try to schedule instructions to move dependences apart and thereby improve the instruction issue rate. Even with such compiler scheduling, there is an important difference between this simple superscalar and a VLIW processor: the code, whether scheduled or not, is guaranteed by the hardware to execute correctly. Furthermore, compiled code will always run correctly independent of the issue rate or pipeline structure of the processor. In some VLIW designs, this has not been the case, and recompilation was required when moving across different processor models; in other static issue processors, code would run correctly across different implementations, but often so poorly as to make compilation effectively required.

dynamic pipeline scheduling Hardware support for reordering the order of instruction execution to avoid stalls.

Many superscalars extend the basic framework of dynamic issue decisions to include **dynamic pipeline scheduling**. Dynamic pipeline scheduling chooses which instructions to execute in a given clock cycle while trying to avoid hazards

and stalls. Let's start with a simple example of avoiding a data hazard. Consider the following code sequence:

```
ld    x31, 0(x21)
add   x1,  x31, x2
sub   x23, x23, x3
andi  x5,  x23, 20
```


Even though the `sub` instruction is ready to execute, it must wait for the `ld` and `add` to complete first, which might take many clock cycles if memory is slow. (Chapter 5 explains cache misses, the reason that memory accesses are sometimes very slow.) Dynamic **pipeline** scheduling allows such hazards to be avoided either fully or partially.

Dynamic Pipeline Scheduling

Dynamic pipeline scheduling chooses which instructions to execute next, possibly reordering them to avoid stalls. In such processors, the pipeline is divided into three major units: an instruction fetch and issue unit, multiple functional units (a dozen or more in high-end designs in 2015), and a **commit unit**. Figure 4.69 shows the model. The first unit fetches instructions, decodes them, and sends each instruction to a corresponding functional unit for execution. Each functional unit has buffers, called **reservation stations**, which hold the operands and the operation. (In the next section, we will discuss an alternative to reservation stations used by many recent processors.) As soon as the buffer contains all its operands and the functional unit is ready to execute, the result is calculated. When the result is completed, it is sent to any reservation stations waiting for this particular result as well as to the commit unit, which buffers the result until it is safe to put the result into the register file or, for a store, into memory. The buffer in the commit unit, often called the **reorder buffer**, is also used to supply operands, in much the same way as forwarding logic does in a statically scheduled pipeline. Once a result is committed to the register file, it can be fetched directly from there, just as in a normal pipeline.

The combination of buffering operands in the reservation stations and results in the reorder buffer provides a form of register renaming, just like that used by the compiler in our earlier loop-unrolling example on page 327. To see how this conceptually works, consider the following steps:

 1. When an instruction issues, it is copied to a reservation station for the appropriate functional unit. Any operands that are available in the register file or reorder buffer are also immediately copied into the reservation station. The instruction is buffered in the reservation station until all the operands and the functional unit are available. For the issuing instruction, the register copy of the operand is no longer required, and if a write to that register occurred, the value could be overwritten.



PIPELINING

commit unit The unit in a dynamic or out-of-order execution pipeline that decides when it is safe to release the result of an operation to programmer-visible registers and memory.

reservation station A buffer within a functional unit that holds the operands and the operation.

reorder buffer The buffer that holds results in a dynamically scheduled processor until it is safe to store the results to memory or a register.

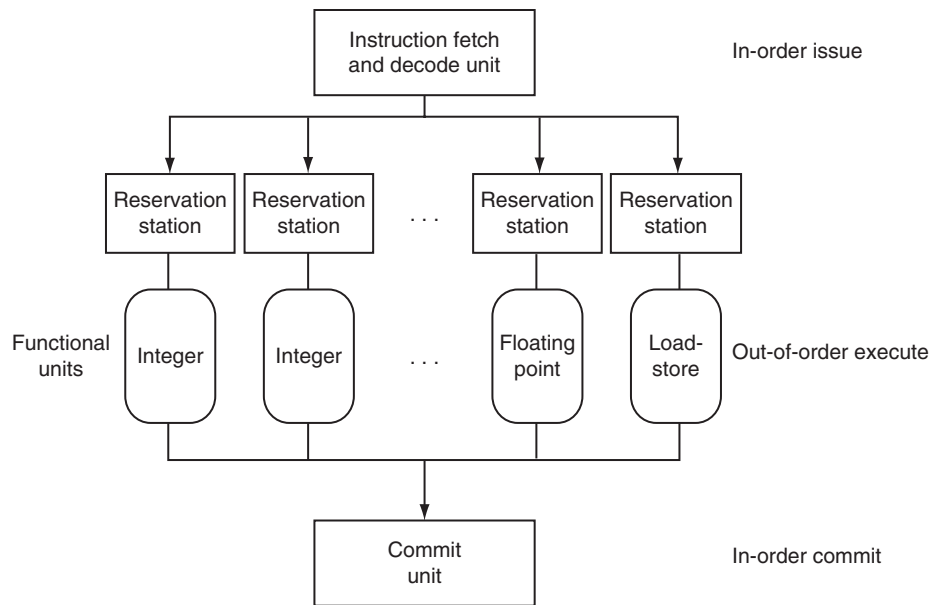


FIGURE 4.69 The three primary units of a dynamically scheduled pipeline. The final step of updating the state is also called retirement or graduation.

2. If an operand is not in the register file or reorder buffer, it must be waiting to be produced by a functional unit. The name of the functional unit that will produce the result is tracked. When that unit eventually produces the result, it is copied directly into the waiting reservation station from the functional unit bypassing the registers.

out-of-order

execution A situation in pipelined execution when an instruction blocked from executing does not cause the following instructions to wait.

in-order commit A commit in which the results of pipelined execution are written to the programmer visible state in the same order that instructions are fetched.

These steps effectively use the reorder buffer and the reservation stations to implement register renaming.

Conceptually, you can think of a dynamically scheduled pipeline as analyzing the data flow structure of a program. The processor then executes the instructions in some order that preserves the data flow order of the program. This style of execution is called an **out-of-order execution**, since the instructions can be executed in a different order than they were fetched.

To make programs behave as if they were running on a simple in-order pipeline, the instruction fetch and decode unit is required to issue instructions in order, which allows dependences to be tracked, and the commit unit is required to write results to registers and memory in program fetch order. This conservative mode is called **in-order commit**. Hence, if an exception occurs, the computer can point to the last instruction executed, and the only registers updated will be those written

by instructions before the instruction causing the exception. Although the front end (fetch and issue) and the back end (commit) of the pipeline run in order, the functional units are free to initiate execution whenever the data they need are available. Today, all dynamically scheduled pipelines use in-order commit.


Dynamic scheduling is often extended by including hardware-based speculation, especially for branch outcomes. By predicting the direction of a branch, a dynamically scheduled processor can continue to fetch and execute instructions along the predicted path. Because the instructions are committed in order, we know whether the branch was correctly predicted before any instructions from the predicted path are committed. A speculative, dynamically scheduled pipeline can also support speculation on load addresses, allowing load-store reordering, and using the commit unit to avoid incorrect speculation. In the next section, we will look at the use of dynamic scheduling with speculation in the Intel Core i7 design.

Given that compilers can also schedule code around data dependences, you might ask why a superscalar processor would use dynamic scheduling. There are three major reasons. First, not all stalls are predictable. In particular, cache misses (see [Chapter 5](#)) in the **memory hierarchy** cause unpredictable stalls. Dynamic scheduling allows the processor to hide some of those stalls by continuing to execute instructions while waiting for the stall to end.


Second, if the processor speculates on branch outcomes using dynamic branch **prediction**, it cannot know the exact order of instructions at compile time, since it depends on the predicted and actual behavior of branches. Incorporating dynamic speculation to exploit more *instruction-level parallelism* (ILP) without incorporating dynamic scheduling would significantly restrict the benefits of speculation.

Third, as the pipeline latency and issue width change from one implementation to another, the best way to compile a code sequence also changes. For example, how to schedule a sequence of dependent instructions is affected by both issue width and latency. The pipeline structure affects both the number of times a loop must be unrolled to avoid stalls as well as the process of compiler-based register renaming. Dynamic scheduling allows the hardware to hide most of these details. Thus, users and software distributors do not need to worry about having multiple versions of a program for different implementations of the same instruction set. Similarly, old legacy code will get much of the benefit of a new implementation without the need for recompilation.

Understanding Program Performance

 


H I E R A R C H Y

 

P R E D I C T I O N

The BIG Picture

 

PIPELINING



PARALLELISM



PREDICTION

Both **pipelining** and multiple-issue execution increase peak instruction throughput and attempt to exploit instruction-level **parallelism** (ILP). Data and control dependences in programs, however, offer an upper limit on sustained performance because the processor must sometimes wait for a dependence to be resolved. Software-centric approaches to exploiting ILP rely on the ability of the compiler to find and reduce the effects of such dependences, while hardware-centric approaches rely on extensions to the pipeline and issue mechanisms. Speculation, performed by the compiler or the hardware, can increase the amount of ILP that can be exploited via **prediction**, although care must be taken since speculating incorrectly is likely to reduce performance.

Hardware/ Software Interface

Modern, high-performance microprocessors are capable of issuing several instructions per clock; unfortunately, sustaining that issue rate is very difficult. For example, despite the existence of processors with four to six issues per clock, very few applications can sustain more than two instructions per clock. There are two primary reasons for this.

First, within the pipeline, the major performance bottlenecks arise from dependences that cannot be alleviated, thus reducing the parallelism among instructions and the sustained issue rate. Although little can be done about true data dependences, often the compiler or hardware does not know precisely whether a dependence exists or not, and so must conservatively assume the dependence exists. For example, code that makes use of pointers, particularly in ways that may lead to aliasing, will lead to more implied potential dependences. In contrast, the greater regularity of array accesses often allows a compiler to deduce that no

dependences exist. Similarly, branches that cannot be accurately predicted whether at runtime or compile time will limit the ability to exploit ILP. Often, additional ILP is available, but the ability of the compiler or the hardware to find ILP that may be widely separated (sometimes by the execution of thousands of instructions) is limited.

Second, losses in the **memory hierarchy** (the topic of [Chapter 5](#)) also limit the ability to keep the pipeline full. Some memory system stalls can be hidden, but limited amounts of ILP also limit the extent to which such stalls can be hidden.



Energy Efficiency and Advanced Pipelining

The downside to the increasing exploitation of instruction-level parallelism via dynamic multiple issue and speculation is potential energy inefficiency. Each innovation was able to turn more transistors into performance, but they often did so very inefficiently. Now that we have collided with the power wall, we are seeing designs with multiple processors per chip where the processors are not as deeply pipelined or as aggressively speculative as its predecessors.

The belief is that while the simpler processors are not as fast as their sophisticated brethren, they deliver better performance per Joule, so that they can deliver more performance per chip when designs are constrained more by energy than they are by the number of transistors.

[Figure 4.70](#) shows the number of pipeline stages, the issue width, speculation level, clock rate, cores per chip, and power of several past and recent Intel microprocessors. Note the drop in pipeline stages and power as companies switch to multicore designs.

Microprocessor	Year	Clock Rate	Pipeline Stages	Issue Width	Out-of-Order/Speculation	Cores/Chip	Power
Intel 486	1989	25 MHz	5	1	No	1	5 W
Intel Pentium	1993	66 MHz	5	2	No	1	10 W
Intel Pentium Pro	1997	200 MHz	10	3	Yes	1	29 W
Intel Pentium 4 Willamette	2001	2000 MHz	22	3	Yes	1	75 W
Intel Pentium 4 Prescott	2004	3600 MHz	31	3	Yes	1	103 W
Intel Core	2006	2930 MHz	14	4	Yes	2	75 W
Intel Core i5 Nehalem	2010	3300 MHz	14	4	Yes	2–4	87 W
Intel Core i5 Ivy Bridge	2012	3400 MHz	14	4	Yes	8	77 W

FIGURE 4.70 Record of Intel Microprocessors in terms of pipeline complexity, number of cores, and power. The Pentium 4 pipeline stages do not include the commit stages. If we included them, the Pentium 4 pipelines would be even deeper.

Elaboration: A commit unit controls updates to the register file *and* memory. Some dynamically scheduled processors update the register file immediately during execution, using extra registers to implement the renaming function and preserving the older copy of a register until the instruction updating the register is no longer speculative. Other processors buffer the result, which, as mentioned above, is typically in a structure called a reorder buffer, and the actual update to the register file occurs later as part of the commit. Stores to memory must be buffered until commit time either in a *store buffer* (see [Chapter 5](#)) or in the reorder buffer. The commit unit allows the store to write to memory from the buffer when the buffer has a valid address and valid data, and when the store is no longer dependent on predicted branches.

Elaboration: Memory accesses benefit from *nonblocking caches*, which continue servicing cache accesses during a cache miss (see [Chapter 5](#)). Out-of-order execution processors need the cache to allow instructions to execute during a miss.

Check Yourself

State whether the following techniques or components are associated primarily with a software- or hardware-based approach to exploiting ILP. In some cases, the answer may be both.

1. Branch prediction
2. Multiple issue
3. VLIW
4. Superscalar
5. Dynamic scheduling
6. Out-of-order execution
7. Speculation
8. Reorder buffer
9. Register renaming

4.11

Real Stuff: The ARM Cortex-A53 and Intel Core i7 Pipelines

[Figure 4.71](#) describes the two microprocessors we examine in this section, whose targets are the two endpoints of the post-PC era.

The ARM Cortex-A53

The ARM Cortex-A53 runs at 1.5 GHz with an eight-stage pipeline and executes the ARMv8 instruction set. It uses dynamic multiple issue, with two instructions per clock cycle. It is a static in-order pipeline, in that instructions issue, execute, and commit in order. The pipeline consists of three sections for instruction fetch, instruction decode, and execute. [Figure 4.72](#) shows the overall pipeline.

Processor	ARM A53	Intel Core i7 920
Market	Personal Mobile Device	Server, Cloud
Thermal design power	100 milliWatts (1 core @ 1 GHz)	130 Watts
Clock rate	1.5 GHz	2.66 GHz
Cores/Chip	4 (configurable)	4
Floating point?	Yes	Yes
Multiple Issue?	Dynamic	Dynamic
Peak instructions/clock cycle	2	4
Pipeline Stages	8	14
Pipeline schedule	Static In-order	Dynamic Out-of-order with Speculation
Branch prediction	Hybrid	2-level
1st level caches/core	16-64 KiB I, 16-64 KiB D	32 KiB I, 32 KiB D
2nd level cache/core	128-2048 KiB (shared)	256 KiB (per core)
3rd level cache (shared)	(platform dependent)	2-8 MiB

FIGURE 4.71 Specification of the ARM Cortex-A53 and the Intel Core i7 920.

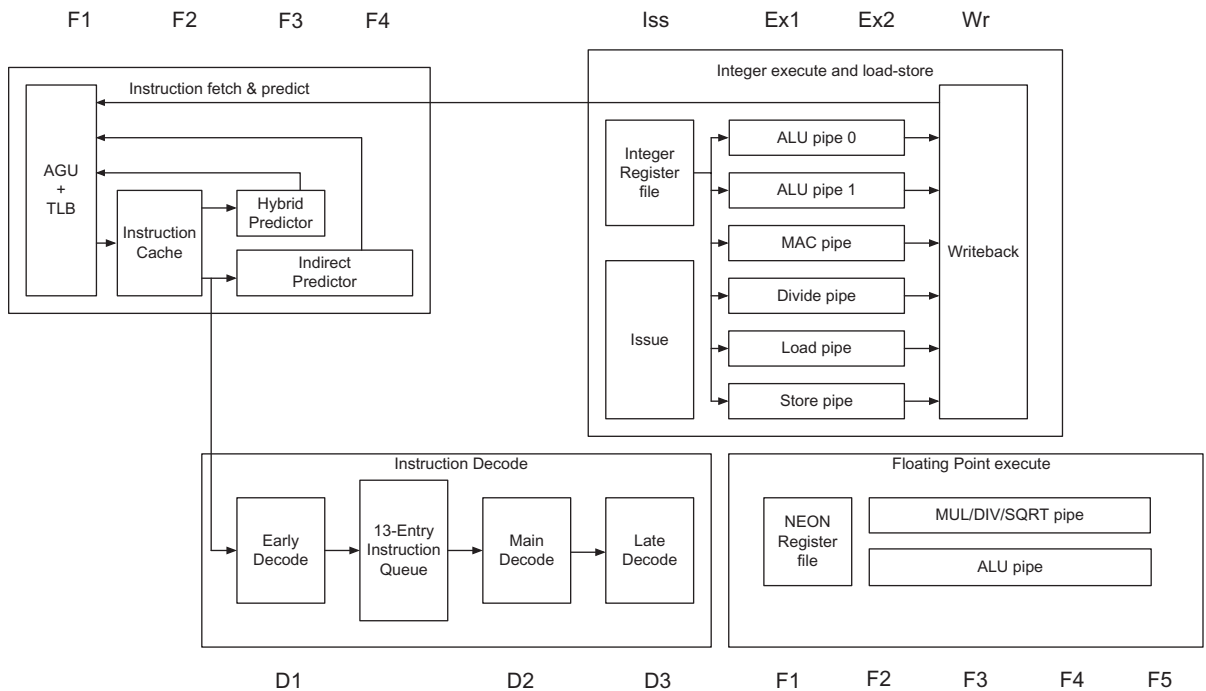


FIGURE 4.72 The Cortex-A53 pipeline. The first three stages fetch instructions into a 13-entry instruction queue. The *Address Generation Unit* (AGU) uses a *Hybrid Predictor*, *Indirect Predictor*, and a *Return Stack* to predict branches to try to keep the instruction queue full. Instruction decode is three stages and instruction execution is three stages. With two additional stages for floating point and SIMD operations.

The first three stages fetch two instructions at a time and try to keep a 13-entry instruction queue full. It uses a 6k-bit hybrid conditional branch predictor, a 256-entry indirect branch predictor, and an 8-entry return address stack to predict future function returns. The prediction of indirect branches takes an additional pipeline stage. This design choice will incur extra latency if the instruction queue cannot decouple the decode and execute stages from the fetch stage, primarily in the case of a branch misprediction or an instruction cache miss. When the branch prediction is wrong, it empties the pipeline, resulting in an eight-clock cycle misprediction penalty.

The decode stages of the pipeline determine if there are dependences between a pair of instructions, which would force sequential execution, and in which pipeline of the execution stages to send the instructions.

The instruction execution section primarily occupies three pipeline stages and provides one pipeline for load instructions, one pipeline for store instructions, two pipelines for integer arithmetic operations, and separate pipelines for integer multiply and divide operations. Either instruction from the pair can be issued to the load or store pipelines. The execution stages have full forwarding between the pipelines.

Floating-point and SIMD operations add a two more pipeline stages to the instruction execution section and feature one pipeline for multiply/divide/square root operations and one pipeline for other arithmetic operations.

Figure 4.73 shows the CPI of the Cortex-A53 using the SPEC2006 benchmarks. While the ideal CPI is 0.5, the best case achieved is 1.0, the median case is 1.3, and

 


FIGURE 4.73 CPI on ARM Cortex-A53 for the SPEC2006 integer benchmarks.

the worst case is 8.6. For the median case, 60% of the stalls are due to the pipelining hazards and 40% are stalls due to the memory hierarchy. Pipeline stalls are caused by branch mispredictions, structural hazards, and data dependencies between pairs of instructions. Given the static pipeline of the Cortex-A53, it is up to the compiler to try to avoid structural hazards and data dependencies.

Elaboration: The Cortex-A53 is a configurable core that supports the ARMv8 instruction set architecture. It is delivered as an IP (*Intellectual Property*) core. IP cores are the dominant form of technology delivery in the embedded, personal mobile device, and related markets; billions of ARM and MIPS processors have been created from these IP cores.

Note that IP cores are different than the cores in the Intel i7 multicore computers. An IP core (which may itself be a multicore) is designed to be incorporated with other logic (hence it is the “core” of a chip), including application-specific processors (such as an encoder or decoder for video), I/O interfaces, and memory interfaces, and then fabricated to yield a processor optimized for a particular application. Although the processor core is almost identical logically, the resultant chips have many differences. One parameter is the size of the L2 cache, which can vary by a factor of 16.

The Intel Core i7 920

x86 microprocessors employ sophisticated pipelining approaches, using both dynamic multiple issue and dynamic pipeline scheduling with out-of-order execution and speculation for their pipelines. These processors, however, are still faced with the challenge of implementing the complex x86 instruction set, described in [Chapter 2](#). Intel fetches x86 instructions and translates them into internal RISC-V-like instructions, which Intel calls *micro-operations*. The micro-operations are then executed by a sophisticated, dynamically scheduled, speculative pipeline capable of sustaining an execution rate of up to six micro-operations per clock cycle. This section focuses on that micro-operation pipeline.

When we consider the design of such processors, the design of the functional units, the cache and register file, instruction issue, and overall pipeline control become intermingled, making it difficult to separate the datapath from the pipeline. Because of this, many engineers and researchers have adopted the term **microarchitecture** to refer to the detailed internal architecture of a processor.

The Intel Core i7 uses a scheme for resolving antidependences and incorrect speculation that uses a reorder buffer together with register renaming. Register renaming explicitly renames the **architectural registers** in a processor (16 in the case of the 64-bit version of the x86 architecture) to a larger set of physical registers. The Core i7 uses register renaming to remove antidependences. Register renaming requires the processor to maintain a map between the architectural registers and the physical registers, indicating which physical register is the most current copy of an architectural register. By keeping track of the renamings that have occurred, register renaming offers another approach to recovery in the event of incorrect speculation: simply undo the mappings that have occurred since the first incorrectly

microarchitecture The organization of the processor, including the major functional units, their interconnection, and control.

architectural registers The instruction set of visible registers of a processor; for example, in RISC-V, these are the 32 integer and 32 floating-point registers.

speculated instruction. This undo will cause the state of the processor to return to the last correctly executed instruction, keeping the correct mapping between the architectural and physical registers.

Figure 4.74 shows the overall organization and pipeline of the Core i7. Below are the eight steps an x86 instruction goes through for execution.

1. Instruction fetch—The processor uses a multilevel branch target buffer to achieve a balance between speed and prediction accuracy. There is also a return address stack to speed up function return. Mispredictions cause a penalty of about 15 cycles. Using the predicted address, the instruction fetch unit fetches 16 bytes from the instruction cache.
2. The 16 bytes are placed in the predecode instruction buffer—The predecode stage transforms the 16 bytes into individual x86 instructions. This predecode is nontrivial since the length of an x86 instruction can be from 1 to 15 bytes

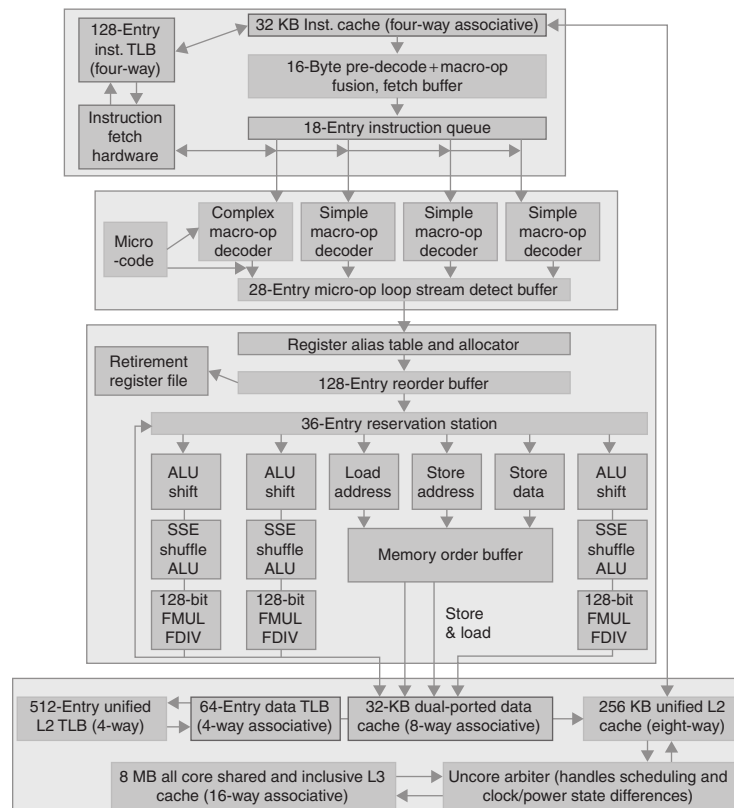


FIGURE 4.74 The Core i7 pipeline with memory components. The total pipeline depth is 14 stages, with branch mispredictions costing 17 clock cycles. This design can buffer 48 loads and 32 stores. The six independent units can begin execution of a ready micro-operation each clock cycle.

and the predecoder must look through a number of bytes before it knows the instruction length. Individual x86 instructions are placed into the 18-entry instruction queue.

3. Micro-op decode—Individual x86 instructions are translated into micro-operations (micro-ops). Three of the decoders handle x86 instructions that translate directly into one micro-op. For x86 instructions that have more complex semantics, there is a microcode engine that is used to produce the micro-op sequence; it can produce up to four micro-ops every cycle and continues until the necessary micro-op sequence has been generated. The micro-ops are placed according to the order of the x86 instructions in the 28-entry micro-op buffer.
4. The micro-op buffer performs *loop stream detection*—If there is a small sequence of instructions (less than 28 instructions or 256 bytes in length) that comprises a loop, the loop stream detector will find the loop and directly issue the micro-ops from the buffer, eliminating the need for the instruction fetch and instruction decode stages to be activated.
5. Perform the basic instruction issue—Looking up the register location in the register tables, renaming the registers, allocating a reorder buffer entry, and fetching any results from the registers or reorder buffer before sending the micro-ops to the reservation stations.
6. The i7 uses a 36-entry centralized reservation station shared by six functional units. Up to six micro-ops may be dispatched to the functional units every clock cycle.
7. The individual function units execute micro-ops and then results are sent back to any waiting reservation station as well as to the register retirement unit, where they will update the register state, once it is known that the instruction is no longer speculative. The entry corresponding to the instruction in the reorder buffer is marked as complete.
8. When one or more instructions at the head of the reorder buffer have been marked as complete, the pending writes in the register retirement unit are executed, and the instructions are removed from the reorder buffer.

Elaboration: Hardware in the second and fourth steps can combine or *fuse* operations together to reduce the number of operations that must be performed. *Macro-op fusion* in the second step takes x86 instruction combinations, such as compare followed by a branch, and fuses them into a single operation. *Microfusion* in the fourth step combines micro-operation pairs such as load/ALU operation and ALU operation/store and issues them to a single reservation station (where they can still issue independently), thus increasing the usage of the buffer. In a study of the Intel Core architecture, which also incorporated microfusion and macrofusion, Bird et al. [2007] discovered that microfusion had little impact on performance, while macrofusion appears to have a modest positive impact on integer performance and little impact on floating-point performance.

Performance of the Intel Core i7 920

Figure 4.75 shows the CPI of the Intel Core i7 for each of the SPEC2006 benchmarks. While the ideal CPI is 0.25, the best case achieved is 0.44, the median case is 0.79, and the worst case is 2.67.

Although it is difficult to differentiate between pipeline stalls and memory stalls in a dynamic out-of-order execution pipeline, we can show the effectiveness of branch prediction and speculation. Figure 4.76 shows the percentage of branches mispredicted and the percentage of the work (measured by the numbers of micro-ops dispatched into the pipeline) that does not retire (that is, their results are annulled) relative to all micro-op dispatches. The min, median, and max of branch mispredictions are 0%, 2%, and 10%. For wasted work, they are 1%, 18%, and 39%.

The wasted work in some cases closely matches the branch misprediction rates, such as for gobmk and astar. In several instances, such as mcf, the wasted work seems relatively larger than the misprediction rate. This divergence is likely due to the memory behavior. With very high data cache miss rates, mcf will dispatch many instructions during an incorrect speculation as long as sufficient reservation stations are available for the stalled memory references. When a branch among the many speculated instructions is finally mispredicted, the micro-ops corresponding to all these instructions will be flushed.

 


FIGURE 4.75 CPI of Intel Core i7 920 running SPEC2006 integer benchmarks.

 


FIGURE 4.76 Percentage of branch mispredictions and wasted work due to unfruitful speculation of Intel Core i7 920 running SPEC2006 integer benchmarks.

The Intel Core i7 combines a 14-stage pipeline and aggressive multiple issue to achieve high performance. By keeping the latencies for back-to-back operations low, the impact of data dependences is reduced. What are the most serious potential performance bottlenecks for programs running on this processor? The following list includes some possible performance problems, the last three of which can apply in some form to any high-performance pipelined processor.

- The use of x86 instructions that do not map to a few simple micro-operations
- Branches that are difficult to predict, causing misprediction stalls and restarts when speculation fails
- Long dependences—typically caused by long-running instructions or the **memory hierarchy**—that lead to stalls
- Performance delays arising in accessing memory (see [Chapter 5](#)) that cause the processor to stall

Understanding Program Performance



4.12

Going Faster: Instruction-Level Parallelism and Matrix Multiply

Returning to the DGEMM example from [Chapter 3](#), we can see the impact of instruction-level parallelism by unrolling the loop so that the multiple-issue, out-of-order execution processor has more instructions to work with. [Figure 4.77](#) shows the unrolled version of [Figure 3.22](#), which contains the C intrinsics to produce the AVX instructions.

Like the unrolling example in [Figure 4.68](#) above, we are going to unroll the loop four times. Rather than manually unrolling the loop in C by making four copies of each of the intrinsics in [Figure 3.22](#), we can rely on the gcc compiler to do the unrolling at `-O3` optimization. (We use the constant `UNROLL` in the C code to control the amount of unrolling in case we want to try other values.) We surround each intrinsic with a simple *for* loop with four iterations (lines 9, 15, and 20) and replace the scalar `C0` in [Figure 3.22](#) with a four-element array `c[]` (lines 8, 10, 16, and 21).

```

1 //include <x86intrin.h>
2 //define UNROLL (4)
3
4 void dgemm (int n, double* A, double* B, double* C)
5 {
6     for ( int i = 0; i < n; i+=UNROLL*4 )
7         for ( int j = 0; j < n; j++ ) {
8             __m256d c[4];
9             for ( int x = 0; x < UNROLL; x++ )
10                 c[x] = _mm256_load_pd(C+i*x*4+j*n);
11
12             for( int k = 0; k < n; k++ )
13             {
14                 __m256d b = _mm256_broadcast_sd(B+k*j*n);
15                 for (int x = 0; x < UNROLL; x++)
16                     c[x] = _mm256_add_pd(c[x],
17                                     _mm256_mul_pd(_mm256_load_pd(A+n*k+x*4+i), b));
18             }
19
20             for ( int x = 0; x < UNROLL; x++ )
21                 _mm256_store_pd(C+i*x*4+j*n, c[x]);
22         }
23     }

```

FIGURE 4.77 Optimized C version of DGEMM using C intrinsics to generate the AVX subword-parallel instructions for the x86 ([Figure 3.22](#)) and loop unrolling to create more opportunities for instruction-level parallelism. [Figure 4.78](#) shows the assembly language produced by the compiler for the inner loop, which unrolls the three for-loop bodies to expose instruction-level parallelism.

Figure 4.78 shows the assembly language output of the unrolled code. As expected, in Figure 4.78 there are four versions of each of the AVX instructions in Figure 3.23, with one exception. We only need one copy of the `vbroadcastsd` instruction, since we can use the four copies of the B element in register `%ymm0` repeatedly throughout the loop. Thus, the five AVX instructions in Figure 3.23 become 17 in Figure 4.78, and the seven integer instructions appear in both, although the constants and addressing changes to account for the unrolling. Hence, despite unrolling four times, the number of instructions in the body of the loop only doubles: from 12 to 24.

```

1  vmovapd (%r11),%ymm4           // Load 4 elements of C into %ymm4
2  mov     %rbx,%rax              // register %rax = %rbx
3  xor     %ecx,%ecx              // register %ecx = 0
4  vmovapd 0x20(%r11),%ymm3       // Load 4 elements of C into %ymm3
5  vmovapd 0x40(%r11),%ymm2       // Load 4 elements of C into %ymm2
6  vmovapd 0x60(%r11),%ymm1       // Load 4 elements of C into %ymm1
7  vbroadcastsd (%rcx,%r9,1),%ymm0 // Make 4 copies of B element
8  add     $0x8,%rcx              // register %rcx = %rcx + 8
9  vmulpd  (%rax),%ymm0,%ymm5      // Parallel mul %ymm1,4 A
10 vaddpd  %ymm5,%ymm4,%ymm4       // Parallel add %ymm5, %ymm4
11 vmulpd  0x20(%rax),%ymm0,%ymm5 // Parallel mul %ymm1,4 A
12 vaddpd  %ymm5,%ymm3,%ymm3       // Parallel add %ymm5, %ymm3
13 vmulpd  0x40(%rax),%ymm0,%ymm5 // Parallel mul %ymm1,4 A
14 vmulpd  0x60(%rax),%ymm0,%ymm0 // Parallel mul %ymm1,4 A
15 add     %r8,%rax               // register %rax = %rax + %r8
16 cmp     %r10,%rcx              // compare %r8 to %rax
17 vaddpd  %ymm5,%ymm2,%ymm2       // Parallel add %ymm5, %ymm2
18 vaddpd  %ymm0,%ymm1,%ymm1       // Parallel add %ymm0, %ymm1
19 jne     68 <dgemm+0x68>         // branch if %r8 != %rax
20 add     $0x1,%esi              // register %esi = %esi + 1
21 vmovapd %ymm4,(%r11)           // Store %ymm4 into 4 C elements
22 vmovapd %ymm3,0x20(%r11)       // Store %ymm3 into 4 C elements
23 vmovapd %ymm2,0x40(%r11)       // Store %ymm2 into 4 C elements
24 vmovapd %ymm1,0x60(%r11)       // Store %ymm1 into 4 C elements

```

FIGURE 4.78 The x86 assembly language for the body of the nested loops generated by compiling the unrolled C code in Figure 4.77.

 


FIGURE 4.79 Performance of three versions of DGEMM for 32×32 matrices. Subword parallelism and instruction-level parallelism have led to speedup of almost a factor of 9 over the unoptimized code in Figure 3.21.



Figure 4.79 shows the performance increase DGEMM for 32×32 matrices in going from unoptimized to AVX and then to AVX with unrolling. Unrolling more than doubles performance, going from 6.4 GFLOPS to 14.6 GFLOPS. Optimizations for **subword parallelism** and **instruction-level parallelism** result in an overall speedup of 8.59 versus the unoptimized DGEMM in Figure 3.21.

Elaboration: As mentioned in the Elaboration in Section 3.8, these results are with Turbo mode turned off. If we turn it on, like in Chapter 3, we improve all the results by the temporary increase in the clock rate of $3.3/2.6 = 1.27$ to 2.1 GFLOPS for unoptimized DGEMM, 8.1 GFLOPS with AVX, and 18.6 GFLOPS with unrolling and AVX. As mentioned in Section 3.8, Turbo mode works particularly well in this case because it is using only a single core of an eight-core chip.

Elaboration: There are no pipeline stalls despite the reuse of register `%ymm5` in lines 9 to 17 of Figure 4.78 because the Intel Core i7 pipeline renames the registers.

Check Yourself

Are the following statements true or false?

1. The Intel Core i7 uses a multiple-issue pipeline to directly execute x86 instructions.
2. Both the Cortex-A53 and the Core i7 use dynamic multiple issue.
3. The Core i7 microarchitecture has many more registers than x86 requires.
4. The Intel Core i7 uses less than half the pipeline stages of the earlier Intel Pentium 4 Prescott (see Figure 4.70).



Advanced Topic: An Introduction to Digital Design Using a Hardware Design Language to Describe and Model a Pipeline and More Pipelining Illustrations

Modern digital design is done using hardware description languages and modern computer-aided synthesis tools that can create detailed hardware designs from the descriptions using both libraries and logic synthesis. Entire books are written on such languages and their use in digital design. This section, which appears online, gives a brief introduction and shows how a hardware design language, Verilog in this case, can be used to describe the processor control both behaviorally and in a form suitable for hardware synthesis. It then provides a series of behavioral models in Verilog of the five-stage pipeline. The initial model ignores hazards, and additions to the model highlight the changes for forwarding, data hazards, and branch hazards.

We then provide about a dozen illustrations using the single-cycle graphical pipeline representation for readers who want to see more detail on how pipelines work for a few sequences of RISC-V instructions.

4.14 Fallacies and Pitfalls

Fallacy: Pipelining is easy.

Our books testify to the subtlety of correct pipeline execution. Our advanced book had a pipeline bug in its first edition, despite its being reviewed by more than 100 people and being class-tested at 18 universities. The bug was uncovered only when someone tried to build the computer in that book. The fact that the Verilog to describe a pipeline like that in the Intel Core i7 will be hundreds of thousands of lines is an indication of the complexity. Beware!

Fallacy: Pipelining ideas can be implemented independent of technology.

When the number of transistors on-chip and the speed of transistors made a five-stage pipeline the best solution, then the delayed branch (see the *Elaboration* on page 274) was a simple solution to control hazards. With longer pipelines, superscalar execution, and dynamic branch prediction, it is now redundant. In the early 1990s, dynamic pipeline scheduling took too many resources and was not required for high performance, but as transistor budgets continued to double due to **Moore's Law** and logic became much faster than memory, then multiple functional units and dynamic pipelining made more sense. Today, concerns about power are leading to less aggressive and more efficient designs.

Pitfall: Failure to consider instruction set design can adversely impact pipelining.





Advanced Topic: An Introduction to Digital Design Using a Hardware Design Language to Describe and Model a Pipeline and More Pipelining Illustrations

This online section covers hardware description languages and then gives a dozen examples of pipeline diagrams, starting on page 366.e18.

As mentioned in [Appendix A](#), Verilog can describe processors for simulation or with the intention that the Verilog specification be synthesized. To achieve acceptable synthesis results in size and speed, and a behavioral specification intended for synthesis must carefully delineate the highly combinational portions of the design, such as a datapath, from the control. The datapath can then be synthesized using available libraries. A Verilog specification intended for synthesis is usually longer and more complex.

We start with a behavioral model of the five-stage pipeline. To illustrate the dichotomy between behavioral and synthesizable designs, we then give two Verilog descriptions of a multiple-cycle-per-instruction RISC-V processor: one intended solely for simulations and one suitable for synthesis.

Using Verilog for Behavioral Specification with Simulation for the Five-Stage Pipeline

[Figure e4.13.1](#) shows a Verilog behavioral description of the pipeline that handles ALU instructions as well as loads and stores. It does not accommodate branches (even incorrectly!), which we postpone including until later in the chapter.

Because Verilog lacks the ability to define registers with named fields such as structures in C, we use several independent registers for each pipeline register. We name these registers with a prefix using the same convention; hence, IFIDIR is the IR portion of the IFID pipeline register.

This version is a behavioral description not intended for synthesis. Instructions take the same number of clock cycles as our hardware design, but the control is done in a simpler fashion by repeatedly decoding fields of the instruction in each pipe stage. Because of this difference, the instruction register (IR) is needed throughout the pipeline, and the entire IR is passed from pipe stage to pipe stage. As you read the Verilog descriptions in this chapter, remember that the actions in the `always` block all occur in parallel on every clock cycle. Since there are no blocking assignments, the order of the events within the `always` block is arbitrary.

```

module RISCVCPU (clock);
    // Instruction opcodes
    parameter LD = 7'b000_0011, SD = 7'b010_0011, BEQ = 7'b110_0011, NOP =
    32'h0000_0013, ALUop = 7'b001_0011;
    input clock;

    reg [63:0] PC, Regs[0:31], IDEXA, IDEXB, EXMEMB, EXMEMALUOut,
    MEMWBValue;
    reg [31:0] IMemory[0:1023], DMemory[0:1023], // separate memories
    IFIDIR, IDEXIR, EXMEMIR, MEMWBIR; // pipeline registers
    wire [4:0] IFIDrs1, IFIDrs2, MEMWBrd; // Access register fields
    wire [6:0] IDEXop, EXMEMop, MEMWBop; // Access opcodes
    wire [63:0] Ain, Bin; // the ALU inputs

    // These assignments define fields from the pipeline registers
    assign IFIDrs1 = IFIDIR[19:15]; // rs1 field
    assign IFIDrs2 = IFIDIR[24:20]; // rs2 field
    assign IDEXop = IDEXIR[6:0]; // the opcode
    assign EXMEMop = EXMEMIR[6:0]; // the opcode
    assign MEMWBop = MEMWBIR[6:0]; // the opcode
    assign MEMWBrd = MEMWBIR[11:7]; // rd field
    // Inputs to the ALU come directly from the ID/EX pipeline registers
    assign Ain = IDEXA;
    assign Bin = IDEXB;

    integer i; // used to initialize registers
    initial
    begin
        PC = 0;
        IFIDIR = NOP; IDEXIR = NOP; EXMEMIR = NOP; MEMWBIR = NOP; // put NOPs
        in pipeline registers
        for (i=0;i<=31;i=i+1) Regs[i] = i; // initialize registers--just so
        they aren't cares
    end

    // Remember that ALL these actions happen every pipe stage and with the
    use of <= they happen in parallel!
    always @(posedge clock)
    begin
        // first instruction in the pipeline is being fetched
        // Fetch & increment PC
        IFIDIR <= IMemory[PC >> 2];
        PC <= PC + 4;

        // second instruction in pipeline is fetching registers
        IDEXA <= Regs[IFIDrs1]; IDEXB <= Regs[IFIDrs2]; // get two registers
        IDEXIR <= IFIDIR; // pass along IR--can happen anywhere, since this
        affects next stage only!

        // third instruction is doing address calculation or ALU operation
        if (IDEXop == LD)
            EXMEMALUOut <= IDEXA + {{53{IDEXIR[31]}}, IDEXIR[30:20]};
        else if (IDEXop == SD)
            EXMEMALUOut <= IDEXA + {{53{IDEXIR[31]}}, IDEXIR [30:25],
        IDEXIR[11:7]};
        else if (IDEXop == ALUop)
            case (IDEXIR[31:25]) // case for the various R-type instructions
            0: EXMEMALUOut <= Ain + Bin; // add operation

```

FIGURE e4.13.1 A Verilog behavioral model for the RISC-V five-stage pipeline, ignoring branch and data hazards. As in the design earlier in [Chapter 4](#), we use separate instruction and data memories, which would be implemented using separate caches as we describe in [Chapter 5](#).

```

default: ; // other R-type operations: subtract, SLT, etc.
    endcase
    EXMEMIR <= IDEXIR; EXMEMB <= IDEXB; // pass along the IR & B register

    // Mem stage of pipeline
    if (EXMEMop == ALUop) MEMWBValue <= EXMEMALUOut; // pass along ALU
result
    else if (EXMEMop == LD) MEMWBValue <= DMemory[EXMEMALUOut >> 2];
    else if (EXMEMop == SD) DMemory[EXMEMALUOut >> 2] <= EXMEMB; //store
    MEMWBIR <= EXMEMIR; // pass along IR

    // WB stage
    if (((MEMWBop == LD) || (MEMWBop == ALUop)) && (MEMWBrd != 0)) //
update registers if load/ALU operation and destination not 0
    Regs[MEMWBrd] <= MEMWBValue;
    end
endmodule

```

FIGURE e4.13.1 A Verilog behavioral model for the RISC-V five-stage pipeline, ignoring branch and data hazards. (Continued)

Implementing Forwarding in Verilog

To extend the Verilog model further, [Figure e4.13.2](#) shows the addition of forwarding logic for the case when the source and destination are ALU instructions. Neither load stalls nor branches are handled; we will add these shortly. The changes from the earlier Verilog description are highlighted.

Someone has proposed moving the write for a result from an ALU instruction from the WB to the MEM stage, pointing out that this would reduce the maximum length of forwards from an ALU instruction by one cycle. Which of the following is accurate reasons *not* to consider such a change?

**Check
Yourself**

1. It would not actually change the forwarding logic, so it has no advantage.
2. It is impossible to implement this change under any circumstance since the write for the ALU result must stay in the same pipe stage as the write for a load result.
3. Moving the write for ALU instructions would create the possibility of writes occurring from two different instructions during the same clock cycle. Either an extra write port would be required on the register file or a structural hazard would be created.
4. The result of an ALU instruction is not available in time to do the write during MEM.

The Behavioral Verilog with Stall Detection

If we ignore branches, stalls for data hazards in the RISC-V pipeline are confined to one simple case: loads whose results are currently in the WB clock stage. Thus, extending the Verilog to handle a load with a destination that is either an ALU instruction or an effective address calculation is reasonably straightforward, and [Figure e4.13.3](#) shows the few additions needed.

```

module RISCVCPU (clock);
    // Instruction opcodes
    parameter LD = 7'b000_0011, SD = 7'b010_0011, BEQ = 7'b110_0011, NOP =
32'h0000_0013, ALUop = 7'b001_0011;
    input clock;

    reg [63:0] PC, Regs[0:31], IDEXA, IDEXB, EXMEMB, EXMEMALUOut,
MEMWBValue;
    reg [31:0] IMemory[0:1023], DMemory[0:1023], // separate memories
        IFIDIR, IDEXIR, EXMEMIR, MEMWBIR; // pipeline registers
    wire [4:0] IFIDrs1, IFIDrs2, IDEXrs1, IDEXrs2, EXMEMrd, MEMWBrd; //
Access register fields
    wire [6:0] IDEXop, EXMEMop, MEMWBop; // Access opcodes
    wire [63:0] Ain, Bin; // the ALU inputs
    // declare the bypass signals
    wire bypassAfromMEM, bypassAfromALUinWB,
        bypassBfromMEM, bypassBfromALUinWB,
        bypassAfromLDinWB, bypassBfromLDinWB;

    assign IFIDrs1 = IFIDIR[19:15];
    assign IFIDrs2 = IFIDIR[24:20];
    assign IDEXop = IDEXIR[6:0];
    assign IDEXrs1 = IDEXIR[19:15];
    assign IDEXrs2 = IDEXIR[24:20];
    assign EXMEMop = EXMEMIR[6:0];
    assign EXMEMrd = EXMEMIR[11:7];
    assign MEMWBop = MEMWBIR[6:0];
    assign MEMWBrd = MEMWBIR[11:7];

    // The bypass to input A from the MEM stage for an ALU operation
    assign bypassAfromMEM = (IDEXrs1 == EXMEMrd) && (IDEXrs1 != 0) &&
(EXMEMop == ALUop);
    // The bypass to input B from the MEM stage for an ALU operation
    assign bypassBfromMEM = (IDEXrs2 == EXMEMrd) && (IDEXrs2 != 0) &&
(EXMEMop == ALUop);
    // The bypass to input A from the WB stage for an ALU operation
    assign bypassAfromALUinWB = (IDEXrs1 == MEMWBrd) && (IDEXrs1 != 0) &&
(MEMWBop == ALUop);
    // The bypass to input B from the WB stage for an ALU operation
    assign bypassBfromALUinWB = (IDEXrs2 == MEMWBrd) && (IDEXrs2 != 0) &&
(MEMWBop == ALUop);
    // The bypass to input A from the WB stage for an LD operation
    assign bypassAfromLDinWB = (IDEXrs1 == MEMWBrd) && (IDEXrs1 != 0) &&
(MEMWBop == LD);
    // The bypass to input B from the WB stage for an LD operation
    assign bypassBfromLDinWB = (IDEXrs2 == MEMWBrd) && (IDEXrs2 != 0) &&
(MEMWBop == LD);
    // The A input to the ALU is bypassed from MEM if there is a bypass
there,
    // Otherwise from WB if there is a bypass there, and otherwise comes
from the IDEX register
    assign Ain = bypassAfromMEM ? EXMEMALUOut :
        (bypassAfromALUinWB || bypassAfromLDinWB) ? MEMWBValue :
IDEXA;
    // The B input to the ALU is bypassed from MEM if there is a bypass
there,
    // Otherwise from WB if there is a bypass there, and otherwise comes
from the IDEX register

```

FIGURE e4.13.2 A behavioral definition of the five-stage RISC-V pipeline with bypassing to ALU operations and address calculations. The code added to [Figure e4.13.1](#) to handle bypassing is highlighted. Because these bypasses only require changing where the ALU inputs come from, the only changes required are in the combinational logic responsible for selecting the ALU inputs. (*continues on next page*)

```

    assign Bin = bypassBfromMEM ? EXMEMALUOut :
              (bypassBfromALUinWB || bypassBfromLDinWB) ? MEMWBValue;
IDEXB;

integer i; // used to initialize registers
initial
begin
    PC = 0;
    IFIDIR = NOP; IDEXIR = NOP; EXMEMIR = NOP; MEMWBIR = NOP; // put NOPs
in pipeline registers
    for (i=0;i<=31;i=i+1) Regs[i] = i; // initialize registers--just so
they aren't cares
end

// Remember that ALL these actions happen every pipe stage and with the
use of <= they happen in parallel!
always @(posedge clock)
begin
    // first instruction in the pipeline is being fetched
    // Fetch & increment PC
    IFIDIR <= IMemory[PC >> 2];
    PC <= PC + 4;

    // second instruction in pipeline is fetching registers
    IDEXA <= Regs[IFIDrs1]; IDEXB <= Regs[IFIDrs2]; // get two registers
    IDEXIR <= IFIDIR; // pass along IR--can happen anywhere, since this
affects next stage only!

    // third instruction is doing address calculation or ALU operation
    if (IDEXop == LD)
        EXMEMALUOut <= IDEXA + {{53{IDEXIR[31]}}, IDEXIR[30:20]};
    else if (IDEXop == SD)
        EXMEMALUOut <= IDEXA + {{53{IDEXIR[31]}}, IDEXIR[30:25],
IDEXIR[11:7]};
    else if (IDEXop == ALUop)
        case (IDEXIR[31:25]) // case for the various R-type instructions
            0: EXMEMALUOut <= Ain + Bin; // add operation
            default: ; // other R-type operations: subtract, SLT, etc.
        endcase
    EXMEMIR <= IDEXIR; EXMEMB <= IDEXB; // pass along the IR & B register

    // Mem stage of pipeline
    if (EXMEMop == ALUop) MEMWBValue <= EXMEMALUOut; // pass along ALU
result
    else if (EXMEMop == LD) MEMWBValue <= DMemory[EXMEMALUOut >> 2];
    else if (EXMEMop == SD) DMemory[EXMEMALUOut >> 2] <= EXMEMB; //store
    MEMWBIR <= EXMEMIR; // pass along IR

    // WB stage
    if ((MEMWBop == LD) || (MEMWBop == ALUop)) && (MEMWBrd != 0) //
update registers if load/ALU operation and destination not 0
        Regs[MEMWBrd] <= MEMWBValue;
end
endmodule

```

FIGURE e4.13.2 A behavioral definition of the five-stage RISC-V pipeline with bypassing to ALU operations and address calculations. (Continued)

```

module RISCVCPU (clock);
    // Instruction opcodes
    parameter LD = 7'b000_0011, SD = 7'b010_0011, BEQ = 7'b110_0011, NOP =
32'h0000_0013, ALUop = 7'b001_0011;
    input clock;

    reg [63:0] PC, Regs[0:31], IDEXA, IDEXB, EXMEMB, EXMEMALUOut,
MEMWBValue;
    reg [31:0] IMemory[0:1023], DMemory[0:1023], // separate memories
        IFIDIR, IDEXIR, EXMEMIR, MEMWBIR; // pipeline registers
    wire [4:0] IFIDrs1, IFIDrs2, IDEXrs1, IDEXrs2, EXMEMrd, MEMWBrd; //
Access register fields
    wire [6:0] IDEXop, EXMEMop, MEMWBop; // Access opcodes
    wire [63:0] Ain, Bin; // the ALU inputs
    // declare the bypass signals
    wire bypassAfromMEM, bypassAfromALUinWB,
        bypassBfromMEM, bypassBfromALUinWB,
        bypassAfromLDinWB, bypassBfromLDinWB;
    wire stall; // stall signal

    assign IFIDrs1 = IFIDIR[19:15];
    assign IFIDrs2 = IFIDIR[24:20];
    assign IDEXop = IDEXIR[6:0];
    assign IDEXrs1 = IDEXIR[19:15];
    assign IDEXrs2 = IDEXIR[24:20];
    assign EXMEMop = EXMEMIR[6:0];
    assign EXMEMrd = EXMEMIR[11:7];
    assign MEMWBop = MEMWBIR[6:0];
    assign MEMWBrd = MEMWBIR[11:7];

    // The bypass to input A from the MEM stage for an ALU operation
    assign bypassAfromMEM = (IDEXrs1 == EXMEMrd) && (IDEXrs1 != 0) &&
(EXMEMop == ALUop);
    // The bypass to input B from the MEM stage for an ALU operation
    assign bypassBfromMEM = (IDEXrs2 == EXMEMrd) && (IDEXrs2 != 0) &&
(EXMEMop == ALUop);
    // The bypass to input A from the WB stage for an ALU operation
    assign bypassAfromALUinWB = (IDEXrs1 == MEMWBrd) && (IDEXrs1 != 0) &&
(MEMWBop == ALUop);
    // The bypass to input B from the WB stage for an ALU operation
    assign bypassBfromALUinWB = (IDEXrs2 == MEMWBrd) && (IDEXrs2 != 0) &&
(MEMWBop == ALUop);
    // The bypass to input A from the WB stage for an LD operation
    assign bypassAfromLDinWB = (IDEXrs1 == MEMWBrd) && (IDEXrs1 != 0) &&
(MEMWBop == LD);
    // The bypass to input B from the WB stage for an LD operation
    assign bypassBfromLDinWB = (IDEXrs2 == MEMWBrd) && (IDEXrs2 != 0) &&
(MEMWBop == LD);
    // The A input to the ALU is bypassed from MEM if there is a bypass
there,
    // Otherwise from WB if there is a bypass there, and otherwise comes
from the IDEX register
    assign Ain = bypassAfromMEM ? EXMEMALUOut :
        (bypassAfromALUinWB || bypassAfromLDinWB) ? MEMWBValue :
IDEXA;
    // The B input to the ALU is bypassed from MEM if there is a bypass
there,
    // Otherwise from WB if there is a bypass there, and otherwise comes
from the IDEX register
    assign Bin = bypassBfromMEM ? EXMEMALUOut :
        (bypassBfromALUinWB || bypassBfromLDinWB) ? MEMWBValue :
IDEXB;

```

FIGURE e4.13.3 A behavioral definition of the five-stage RISC-V pipeline with stalls for loads when the destination is an ALU instruction or effective address calculation. The changes from [Figure e4.13.2](#) are highlighted. (*continues on next page*)

```

// The signal for detecting a stall based on the use of a result from
LW
assign stall = (MEMWBop == LD) && ( // source instruction is a load
    (((IDEXop == LD) || (IDEXop == SD)) && (IDEXrs1 ==
MEMWBrd)) || // stall for address calc
    ((IDEXop == ALUop) && ((IDEXrs1 == MEMWBrd) ||
(IDEXrs2 == MEMWBrd)))); // ALU use

integer i; // used to initialize registers
initial
begin
    PC = 0;
    IFIDIR = NOP; IDEXIR = NOP; EXMEMIR = NOP; MEMWBIR = NOP; // put NOPs
in pipeline registers
    for (i=0; i<=31; i=i+1) Regs[i] = i; // initialize registers-just so
they aren't cares
end

// Remember that ALL these actions happen every pipe stage and with the
use of <= they happen in parallel!
always @(posedge clock)
begin
    if (~stall)
        begin // the first three pipeline stages stall if there is a load
hazard
            // first instruction in the pipeline is being fetched
            // Fetch & increment PC
            IFIDIR <= IMemory[PC >> 2];
            PC <= PC + 4;

            // second instruction in pipeline is fetching registers
            IDEXA <= Regs[IFIDrs1]; IDEXB <= Regs[IFIDrs2]; // get two
registers
            IDEXIR <= IFIDIR; // pass along IR--can happen anywhere, since this
affects next stage only!

            // third instruction is doing address calculation or ALU operation
            if (IDEXop == LD)
                EXMEMALUOut <= IDEXA + {{53{IDEXIR[31]}}, IDEXIR[30:20]};
            else if (IDEXop == SD)
                EXMEMALUOut <= IDEXA + {{53{IDEXIR[31]}}, IDEXIR[30:25],
IDEXIR[11:7]};
            else if (IDEXop == ALUop)
                case (IDEXIR[31:25]) // case for the various R-type instructions
                    0: EXMEMALUOut <= Ain + Bin; // add operation
                    default: ; // other R-type operations: subtract, SLT, etc.
                endcase
            EXMEMIR <= IDEXIR; EXMEMB <= IDEXB; // pass along the IR & B
register
        end
        else EXMEMIR <= NOP; // Freeze first three stages of pipeline; inject
a nop into the EX output

// Mem stage of pipeline
        if (EXMEMop == ALUop) MEMWBValue <= EXMEMALUOut; // pass along ALU
result
        else if (EXMEMop == LD) MEMWBValue <= DMemory[EXMEMALUOut >> 2];
        else if (EXMEMop == SD) DMemory[EXMEMALUOut >> 2] <= EXMEMB; //store
MEMWBIR <= EXMEMIR; // pass along IR

// WB stage
        if (((MEMWBop == LD) || (MEMWBop == ALUop)) && (MEMWBrd != 0)) //
update registers if load/ALU operation and destination not 0
            Regs[MEMWBrd] <= MEMWBValue;
        end
    end
endmodule

```

FIGURE e4.13.3 A behavioral definition of the five-stage RISC-V pipeline with stalls for loads when the destination is an ALU instruction or effective address calculation.
(Continued)

Check Yourself

Someone has asked about the possibility of data hazards occurring through memory, contrary to through a register. Which of the following statements about such hazards is true?

1. Since memory accesses only occur in the MEM stage, all memory operations are done in the same order as instruction execution, making such hazards impossible in this pipeline.
2. Such hazards *are* possible in this pipeline; we just have not discussed them yet.
3. No pipeline can ever have a hazard involving memory, since it is the programmer's job to keep the order of memory references accurate.
4. Memory hazards may be possible in some pipelines, but they cannot occur in this particular pipeline.
5. Although the pipeline control would be obligated to maintain ordering among memory references to avoid hazards, it is impossible to design a pipeline where the references could be out of order.

Implementing the Branch Hazard Logic in Verilog

We can extend our Verilog behavioral model to implement the control for branches. We add the code to model branch equal using a “predict not taken” strategy. The Verilog code is shown in [Figure e4.13.4](#). It implements the branch hazard by detecting a taken branch in ID and using that signal to squash the instruction in IF (by setting the IR to 0x00000013, which is an effective NOP in RISC-V); in addition, the PC is assigned to the branch target. Note that to prevent an unexpected latch, it is important that the PC is clearly assigned on every path through the always block; hence, we assign the PC in a single *if* statement. Lastly, note that although [Figure e4.13.4](#) incorporates the basic logic for branches and control hazards, supporting branches requires additional bypassing and data hazard detection, which we have not included.

Using Verilog for Behavioral Specification with Synthesis

To demonstrate the contrasting types of Verilog, we show two descriptions of a different, nonpipelined implementation style of RISC-V that uses multiple clock cycles per instruction. (Since some instructors make a synthesizable description of the RISC-V pipeline project for a class, we chose not to include it here. It would also be long.)

[Figure e4.13.5](#) gives a behavioral specification of a multicycle implementation of the RISC-V processor. Because of the use of behavioral operations, it would be difficult to synthesize a separate datapath and control unit with any reasonable efficiency. This version demonstrates another approach to the control by using a Mealy finite-state machine (see discussion in [Section A.10 of Appendix A](#)). The use of a Mealy machine, which allows the output to depend both on inputs and the current state, allows us to decrease the total number of states.


```

module RISCVCPU (clock);
    // Instruction opcodes
    parameter LD = 7'b000_0011, SD = 7'b010_0011, BEQ = 7'b110_0011, NOP =
32'h0000_0013, ALUOp = 7'b001_0011;
    input clock;

    reg [63:0] PC, Regs[0:31], IDEXA, IDEXB, EXMEMB, EXMEMALUOut,
MEMWBValue;
    reg [31:0] IMemory[0:1023], DMemory[0:1023], // separate memories
        IFIDIR, IDEXIR, EXMEMIR, MEMWBIR; // pipeline registers
    wire [4:0] IFIDrs1, IFIDrs2, IDEXrs1, IDEXrs2, EXMEMrd, MEMWBrd; //
Access register fields
    wire [6:0] IFIDop, IDEXop, EXMEMop, MEMWBop; // Access opcodes
    wire [63:0] Ain, Bin; // the ALU inputs
    // declare the bypass signals
    wire bypassAfromMEM, bypassAfromALUinWB,
        bypassBfromMEM, bypassBfromALUinWB,
        bypassAfromLDinWB, bypassBfromLDinWB;
    wire stall; // stall signal
    wire takebranch;

    assign IFIDop = IFIDIR[6:0];
    assign IFIDrs1 = IFIDIR[19:15];
    assign IFIDrs2 = IFIDIR[24:20];
    assign IDEXop = IDEXIR[6:0];
    assign IDEXrs1 = IDEXIR[19:15];
    assign IDEXrs2 = IDEXIR[24:20];
    assign EXMEMop = EXMEMIR[6:0];
    assign EXMEMrd = EXMEMIR[11:7];
    assign MEMWBop = MEMWBIR[6:0];
    assign MEMWBrd = MEMWBIR[11:7];

    // The bypass to input A from the MEM stage for an ALU operation
    assign bypassAfromMEM = (IDEXrs1 == EXMEMrd) && (IDEXrs1 != 0) &&
(EXMEMop == ALUOp);
    // The bypass to input B from the MEM stage for an ALU operation
    assign bypassBfromMEM = (IDEXrs2 == EXMEMrd) && (IDEXrs2 != 0) &&
(EXMEMop == ALUOp);
    // The bypass to input A from the WB stage for an ALU operation
    assign bypassAfromALUinWB = (IDEXrs1 == MEMWBrd) && (IDEXrs1 != 0) &&
(MEMWBop == ALUOp);
    // The bypass to input B from the WB stage for an ALU operation
    assign bypassBfromALUinWB = (IDEXrs2 == MEMWBrd) && (IDEXrs2 != 0) &&
(MEMWBop == ALUOp);
    // The bypass to input A from the WB stage for an LD operation
    assign bypassAfromLDinWB = (IDEXrs1 == MEMWBrd) && (IDEXrs1 != 0) &&
(MEMWBop == LD);
    // The bypass to input B from the WB stage for an LD operation
    assign bypassBfromLDinWB = (IDEXrs2 == MEMWBrd) && (IDEXrs2 != 0) &&
(MEMWBop == LD);
    // The A input to the ALU is bypassed from MEM if there is a bypass
there,
    // Otherwise from WB if there is a bypass there, and otherwise comes
from the IDEX register
    assign Ain = bypassAfromMEM ? EXMEMALUOut :
        (bypassAfromALUinWB || bypassAfromLDinWB) ? MEMWBValue :
IDEXA;

    // The B input to the ALU is bypassed from MEM if there is a bypass
there,
    // Otherwise from WB if there is a bypass there, and otherwise comes
from the IDEX register
    assign Bin = bypassBfromMEM ? EXMEMALUOut :
        (bypassBfromALUinWB || bypassBfromLDinWB) ? MEMWBValue :
IDEXB;

```

FIGURE e4.13.4 A behavioral definition of the five-stage RISC-V pipeline with stalls for loads when the destination is an ALU instruction or effective address calculation. The changes from [Figure e4.13.2](#) are highlighted. (*continues on next page*)

```

IDEXB;
// The signal for detecting a stall based on the use of a result from
// LW
assign stall = (MEMWBop == LD) && ( // source instruction is a load
((IDEXop == LD) || (IDEXop == SD)) && (IDEXrs1 ==
MEMWBrd)) || // stall for address calc
((IDEXop == ALUop) && ((IDEXrs1 == MEMWBrd) ||
(IDEXrs2 == MEMWBrd)))); // ALU use
// Signal for a taken branch: instruction is BEQ and registers are
equal
assign takebranch = (IFIDop == BEQ) && (Regs[IFIDrs1] ==
Regs[IFIDrs2]);

integer i; // used to initialize registers
initial
begin
PC = 0;
IFIDIR = NOP; IDEXIR = NOP; EXMEMIR = NOP; MEMWBIR = NOP; // put NOPs
in pipeline registers
for (i=0; i<=31; i=i+1) Regs[i] = i; // initialize registers--just so
they aren't cares
end

// Remember that ALL these actions happen every pipe stage and with the
use of <= they happen in parallel!
always @(posedge clock)
begin
if (~stall)
begin // the first three pipeline stages stall if there is a load
hazard
if (~takebranch)
begin // first instruction in the pipeline is being fetched
normally
IFIDIR <= IMemory[PC >> 2];
PC <= PC + 4;
end
else
begin // a taken branch is in ID; instruction in IF is wrong;
insert a NOP and reset the PC
IFIDIR <= NOP;
PC <= PC + {{52{IFIDIR[31]}}, IFIDIR[7], IFIDIR[30:25],
IFIDIR[11:8], 1'b0};
end

// second instruction in pipeline is fetching registers
IDEXA <= Regs[IFIDrs1]; IDEXB <= Regs[IFIDrs2]; // get two
registers
IDEXIR <= IFIDIR; // pass along IR--can happen anywhere, since this
affects next stage only!

// third instruction is doing address calculation or ALU operation
if (IDEXop == LD)

EXMEMALUOut <= IDEXA + {{53{IDEXIR[31]}}, IDEXIR[30:20]};
else if (IDEXop == SD)
EXMEMALUOut <= IDEXA + {{53{IDEXIR[31]}}, IDEXIR[30:25],
IDEXIR[11:7]};
else if (IDEXop == ALUop)
case (IDEXIR[31:25]) // case for the various R-type instructions
0: EXMEMALUOut <= Ain + Bin; // add operation

```

FIGURE e4.13.4 A behavioral definition of the five-stage RISC-V pipeline with stalls for loads when the destination is an ALU instruction or effective address calculation.
(Continued)

```

default: ; // other R-type operations: subtract, SLT, etc.
    endcase
    EXMEMIR <= IDXR; EXMEMB <= IDXB; // pass along the IR & B
register
    end
    else EXMEMIR <= NOP; // Freeze first three stages of pipeline; inject
a nop into the EX output

    // Mem stage of pipeline
    if (EXMEMop == ALUop) MEMWBValue <= EXMEMALUOut; // pass along ALU
result
    else if (EXMEMop == LD) MEMWBValue <= DMemory[EXMEMALUOut >> 2];
    else if (EXMEMop == SD) DMemory[EXMEMALUOut >> 2] <= EXMEMB; //store
    MEMWBIR <= EXMEMIR; // pass along IR

    // WB stage
    if (((MEMWBop == LD) || (MEMWBop == ALUop)) && (MEM WBrd != 0)) //
update registers if load/ALU operation and destination not 0
    Regs[MEMWBrd] <= MEMWBValue;
    end
endmodule

```

FIGURE e4.13.4 A behavioral definition of the five-stage RISC-V pipeline with stalls for loads when the destination is an ALU instruction or effective address calculation. (Continued)

Since a version of the RISC-V design intended for synthesis is considerably more complex, we have relied on a number of Verilog modules that were specified in [Appendix A](#), including the following:

- The 4-to-1 multiplexor shown in Figure A.4.2, and the 2-to-1 multiplexor that can be trivially derived based on the 4-to-1 multiplexor.
- The RISC-V ALU shown in Figure A.5.15.
- The RISC-V ALU control defined in Figure A.5.16.
- The RISC-V register file defined in Figure A.8.11.

Now, let's look at a Verilog version of the RISC-V processor intended for synthesis. [Figure e4.13.6](#) shows the structural version of the RISC-V datapath. [Figure e4.13.7](#) uses the datapath module to specify the RISC-V CPU. This version also demonstrates another approach to implementing the control unit, as well as some optimizations that rely on relationships between various control signals. Observe that the state machine specification only provides the sequencing actions.

The setting of the control lines is done with a series of `assign` statements that depend on the state as well as the opcode field of the instruction register. If one were to fold the setting of the control into the state specification, this would look like a Mealy-style finite-state control unit. Because the setting of the control lines is specified using `assign` statements outside of the `always` block, most logic synthesis systems will generate a small implementation of a finite-state machine

```

module RISCVCPU (clock);
    parameter LD = 7'b000_0011, SD = 7'b010_0011, BEQ = 7'b110_0011, ALUop
= 7'b001_0011;
    input clock; //the clock is an external input

    // The architecturally visible registers and scratch registers for
implementation
    reg [63:0] PC, Regs[0:31], ALUOut, MDR, A, B;
    reg [31:0] Memory [0:1023], IR;
    reg [2:0] state; // processor state
    wire [6:0] opcode; // use to get opcode easily
    wire [63:0] ImmGen; // used to generate immediate

    assign opcode = IR[6:0]; // opcode is lower 7 bits
    assign ImmGen = (opcode == LD) ? {{53{IR[31]}}, IR[30:20]} :
        /* (opcode == SD) */ {{53{IR[31]}}, IR[30:25], IR[11:7]};
    assign PCOffset = {{52{IR[31]}}, IR[7], IR[30:25], IR[11:8], 1'b0};

    // set the PC to 0 and start the control in state 1
    initial begin PC = 0; state = 1; end

    // The state machine--triggered on a rising clock
    always @(posedge clock)
    begin
        Regs[0] <= 0; // shortcut way to make sure R0 is always 0
        case (state) //action depends on the state
            1: begin // first step: fetch the instruction, increment PC, go to
next state
                IR <= Memory[PC >> 2];
                PC <= PC + 4;
                state <= 2; // next state
            end
            2: begin // second step: Instruction decode, register fetch, also
compute branch address
                A <= Regs[IR[19:15]];
                B <= Regs[IR[24:20]];
                ALUOut <= PC + PCOffset; // compute PC-relative branch target
                state <= 3;
            end
            3: begin // third step: Load-store execution, ALU execution, Branch
completion
                if ((opcode == LD) || (opcode == SD))
                begin
                    ALUOut <= A + ImmGen; // compute effective address
                    state <= 4;
                end
                else if (opcode == ALUop)
                begin
                    case (IR[31:25]) // case for the various R-type instructions
                        0: ALUOut <= A + B; // add operation
                        default: ; // other R-type operations: subtract, SLT, etc.
                    endcase
                    state <= 4;
                end
                else if (opcode == BEQ)
                begin
                    if (A == B) begin
                        PC <= ALUOut; // branch taken--update PC
                    end
                end
            end
        end
    end
end

```

FIGURE e4.13.5 A behavioral specification of the multicycle RISC-V design. This has the same cycle behavior as the multicycle design, but is purely for simulation and specification. It cannot be used for synthesis. (*continues on next page*)

```

        state <= 1;
    end
    else ; // other opcodes or exception for undefined instruction
would go here
    end
4: begin
    if (opcode == ALUOp)
    begin // ALU Operation
        Regs[IR[11:7]] <= ALUOut; // write the result
        state <= 1;
    end // R-type finishes
    else if (opcode == LD)
    begin // load instruction
        MDR <= Memory[ALUOut >> 2]; // read the memory
        state <= 5; // next state
    end
    else if (opcode == SD)
    begin // store instruction
        Memory[ALUOut >> 2] <= B; // write the memory
        state <= 1; // return to state 1
    end
    else ; // other instructions go here
    end
5: begin // LD is the only instruction still in execution
    Regs[IR[11:7]] <= MDR; // write the MDR to the register
    state <= 1;
    end // complete an LD instruction
endcase
end
endmodule

```

FIGURE e4.13.5 A behavioral specification of the multicycle RISC-V design. (Continued)

that determines the setting of the state register and then uses external logic to derive the control inputs to the datapath.

In writing this version of the control, we have also taken advantage of a number of insights about the relationship between various control signals as well as situations where we don't care about the control signal value; some examples of these are given in the following elaboration.

More Illustrations of Instruction Execution on the Hardware

To reduce the cost of this book, starting with the third edition, we moved sections and figures that were used by a minority of instructors online. This subsection recaptures those figures for readers who would like more supplemental material to understand pipelining better. These are all single-clock-cycle pipeline diagrams, which take many figures to illustrate the execution of a sequence of instructions.

The three examples are respectively for code with no hazards, an example of forwarding on the pipelined implementation, and an example of bypassing on the pipelined implementation.

```

module Datapath (ALUOp, MemtoReg, MemRead, MemWrite, IorD, RegWrite,
IRWrite,
                PCWrite, PCWriteCond, ALUSrcA, ALUSrcB, PCSource,
opcode, clock); // the control inputs + clock
    parameter LD = 7'b000_0011, SD = 7'b010_0011;
    input [1:0] ALUOp, ALUSrcB; // 2-bit control signals
    input MemtoReg, MemRead, MemWrite, IorD, RegWrite, IRWrite, PCWrite,
PCWriteCond,
        ALUSrcA, PCSource, clock; // 1-bit control signals
    output [6:0] opcode; // opcode is needed as an output by control
    reg [63:0] PC, MDR, ALUOut; // CPU state + some temporaries
    reg [31:0] Memory[0:1023], IR; // CPU state + some temporaries
    wire [63:0] A, B, SignExtendOffset, PCOffset, ALUResultOut, PCValue,
JumpAddr, Writedata, ALUAIN,
        ALUBin, MemOut; // these are signals derived from registers
    wire [3:0] ALUCtl; // the ALU control lines
    wire Zero; // the Zero out signal from the ALU

    initial PC = 0; //start the PC at 0
    //Combinational signals used in the datapath
    // Read using word address with either ALUOut or PC as the address
source
    assign MemOut = MemRead ? Memory[(IorD ? ALUOut : PC) >> 2] : 0;
    assign opcode = IR[6:0]; // opcode shortcut
    // Get the write register data either from the ALUOut or from the MDR
    assign Writedata = MemtoReg ? MDR : ALUOut;
    // Generate immediate
    assign ImmGen = (opcode == LD) ? {{53{IR[31]}}, IR[30:20]} :
        /* (opcode == SD) */ {{53{IR[31]}}, IR[30:25], IR[11:7]};
    // Generate pc offset for branches
    assign PCOffset = {{52{IR[31]}}, IR[7], IR[30:25], IR[11:8], 1'b0};
    // The A input to the ALU is either the rs register or the PC
    assign ALUAIN = ALUSrcA ? A : PC; // ALU input is PC or A

    // Creates an instance of the ALU control unit (see the module defined
in Figure B.5.16
    // Input ALUOp is control-unit set and used to describe the
instruction class as in Chapter 4
    // Input IR[31:25] is the function code field for an ALU instruction
    // Output ALUCtl are the actual ALU control bits as in Chapter 4
    ALUControl alucontroller (ALUOp, IR[31:25], ALUCtl); // ALU control
unit

    // Creates a 2-to-1 multiplexor used to select the source of the next
PC
    // Inputs are ALUResultOut (the incremented PC), ALUOut (the branch
address)
    // PCSource is the selector input and PCValue is the multiplexor
output
    Mult2to1 PCdatasrc (ALUResultOut, ALUOut, PCSource, PCValue);

    // Creates a 4-to-1 multiplexor used to select the B input of the ALU
    // Inputs are register B, constant 4, generated immediate, PC offset
    // ALUSrcB is the select or input
    // ALUBin is the multiplexor output
    Mult4to1 ALUBinput (B, 64'd4, ImmGen, PCOffset, ALUSrcB, ALUBin);

    // Creates a RISC-V ALU
    // Inputs are ALUCtl (the ALU control), ALU value inputs (ALUAIN,
ALUBin)
    // Outputs are ALUResultOut (the 64-bit output) and Zero (zero
detection output)
    RISCVALU ALU (ALUCtl, ALUAIN, ALUBin, ALUResultOut, Zero); // the ALU

```

FIGURE e4.13.6 A Verilog version of the multicycle RISC-V datapath that is appropriate for synthesis. This datapath relies on several units from [Appendix A](#). Initial statements do not synthesize, and a version used for synthesis would have to incorporate a reset signal that had this effect. Also note that resetting R0 to 0 on every clock is not the best way to ensure that R0 stays at 0; instead, modifying the register file module to produce 0 whenever R0 is read and to ignore writes to R0 would be a more efficient solution. (*continues on next page*)

```

// Creates a RISC-V register file
// Inputs are the rs1 and rs2 fields of the IR used to specify which
registers to read,
// Writereg (the write register number), Writedata (the data to be
written),
// RegWrite (indicates a write), the clock
// Outputs are A and B, the registers read
registerfile regs (IR[19:15], IR[24:20], IR[11:7], Writedata,
RegWrite, A, B, clock); // Register file

// The clock-triggered actions of the datapath
always @(posedge clock)
begin
    if (MemWrite) Memory[ALUOut >> 2] <= B; // Write memory--must be a
store
    ALUOut <= ALUResultOut; // Save the ALU result for use on a later
clock cycle
    if (IRWrite) IR <= MemOut; // Write the IR if an instruction fetch
    MDR <= MemOut; // Always save the memory read value
    // The PC is written both conditionally (controlled by PCWrite) and
unconditionally
end
endmodule

```

FIGURE e4.13.6 A Verilog version of the multicycle RISC-V datapath that is appropriate for synthesis. (Continued)

No Hazard Illustrations

On page 285, we gave the example code sequence

```

ld      x10, 40(x1)
sub     x11, x2, x3
add     x12, x3, x4
ld      x13, 48(x1)
add     x14, x5, x6

```

Figures e4.42 and e4.43 showed the multiple-clock-cycle pipeline diagrams for this two-instruction sequence executing across six clock cycles. [Figures e4.13.8 through e4.13.10](#) show the corresponding single-clock-cycle pipeline diagrams for these two instructions. Note that the order of the instructions differs between these two types of diagrams: the newest instruction is at the *bottom and to the right* of the multiple-clock-cycle pipeline diagram, and it is on the *left* in the single-clock-cycle pipeline diagram.

More Examples

To understand how pipeline control works, let's consider these five instructions going through the pipeline:

```

ld      x10, 40(x1)
sub     x11, x2, x3
and     x12, x4, x5
or      x13, x6, x7
add     x14, x8, x9

```

```

module RISCVCPU (clock);
    parameter LD = 7'b000_0011, SD = 7'b010_0011, BEQ = 7'b110_0011, ALUOp
= 7'b001_0011;
    input clock;

    reg [2:0] state;
    wire [1:0] ALUOp, ALUSrcB;
    wire [6:0] opcode;
    wire MemtoReg, MemRead, MemWrite, IorD, RegWrite, IRWrite,
        PCWrite, PCWriteCond, ALUSrcA, PCSource, MemoryOp;

    // Create an instance of the RISC-V datapath, the inputs are the
    control signals; opcode is only output
    Datapath RISCVDP (ALUOp, MemtoReg, MemRead, MemWrite, IorD, RegWrite,
    IRWrite,
        PCWrite, PCWriteCond, ALUSrcA, ALUSrcB, PCSource,
    opcode, clock);

    initial begin state = 1; end // start the state machine in state 1
    // These are the definitions of the control signals
    assign MemoryOp = (opcode == LD) || (opcode == SD); // a memory
operation
    assign ALUOp = ((state == 1) || (state == 2) || ((state == 3) &&
MemoryOp)) ? 2'b00 : // add
        ((state == 3) && (opcode == BEQ)) ? 2'b01 : 2'b10; //
subtract or use function code
    assign MemtoReg = ((state == 4) && (opcode == ALUOp)) ? 0 : 1;
    assign MemRead = (state == 1) || ((state == 4) && (opcode == LD));
    assign MemWrite = (state == 4) && (opcode == SD);
    assign IorD = (state == 1) ? 0 : 1;
    assign RegWrite = (state == 5) || ((state == 4) && (opcode == ALUOp));
    assign IRWrite = (state == 1);
    assign PCWrite = (state == 1);
    assign PCWriteCond = (state == 3) && (opcode == BEQ);
    assign ALUSrcA = ((state == 1) || (state == 2)) ? 0 : 1;
    assign ALUSrcB = ((state == 1) || ((state == 3) && (opcode == BEQ)))?
2'b01 :
        (state == 2) ? 2'b11 :
        ((state == 3) && MemoryOp) ? 2'b10 : 2'b00; // memory
operation or other
    assign PCSource = (state == 1) ? 0 : 1;

    // Here is the state machine, which only has to sequence states
    always @(posedge clock)
    begin // all state updates on a positive clock edge
        case (state)
            1: state <= 2; // unconditional next state
            2: state <= 3; // unconditional next state
            3: state <= (opcode == BEQ) ? 1 : 4; // branch go back else next
state
            4: state <= (opcode == LD) ? 5 : 1; // R-type and SD finish
            5: state <= 1; // go back
        endcase
    end
endmodule

```

FIGURE e4.13.7 The RISC-V CPU using the datapath from [Figure e4.13.6](#).

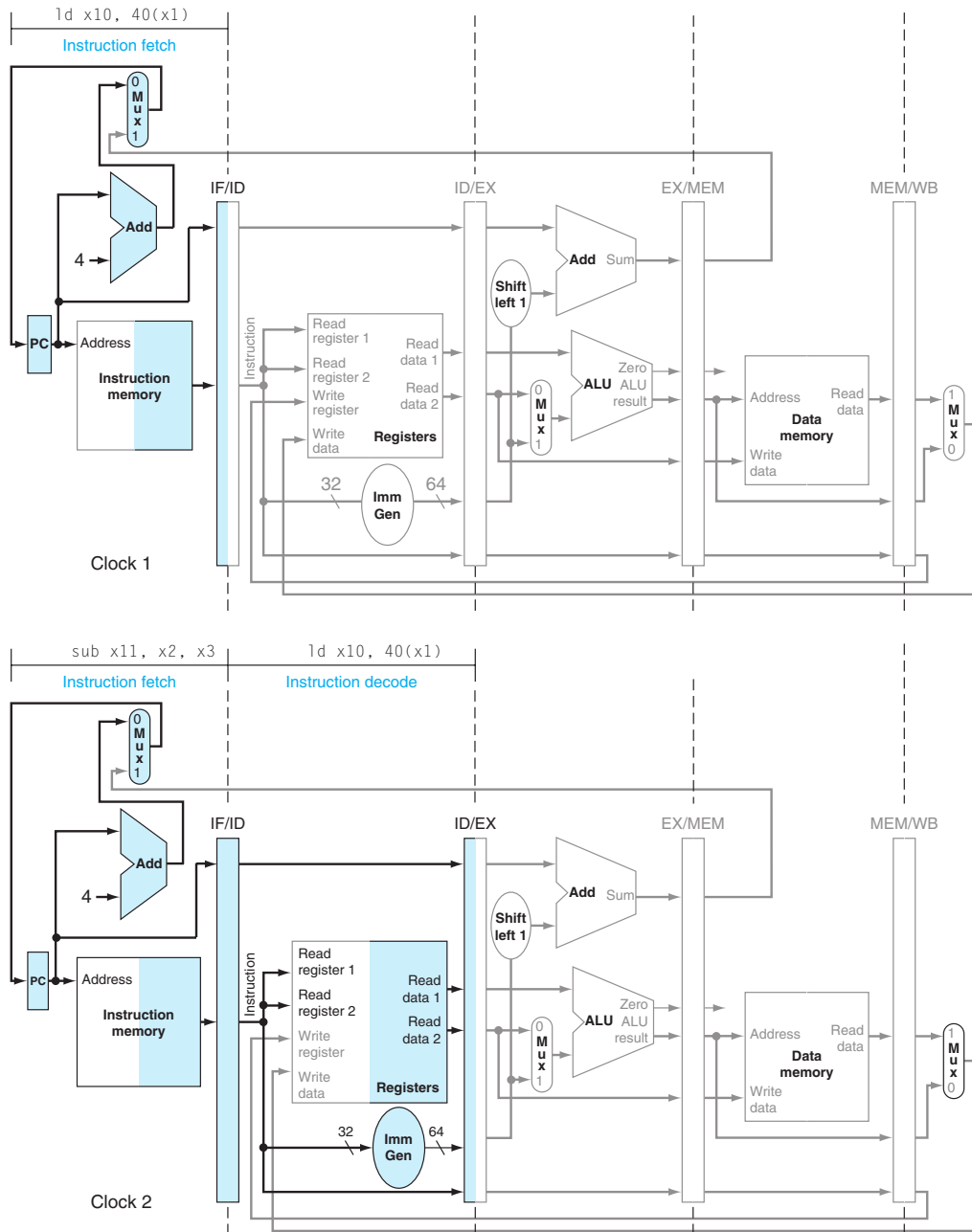


FIGURE e4.13.8 Single-cycle pipeline diagrams for clock cycles 1 (top diagram) and 2 (bottom diagram). This style of pipeline representation is a snapshot of every instruction executing during one clock cycle. Our example has but two instructions, so at most two stages are identified in each clock cycle; normally, all five stages are occupied. The highlighted portions of the datapath are active in that clock cycle. The load is fetched in clock cycle 1 and decoded in clock cycle 2, with the subtract fetched in the second clock cycle. To make the figures easier to understand, the other pipeline stages are empty, but normally there is an instruction in every pipeline stage.

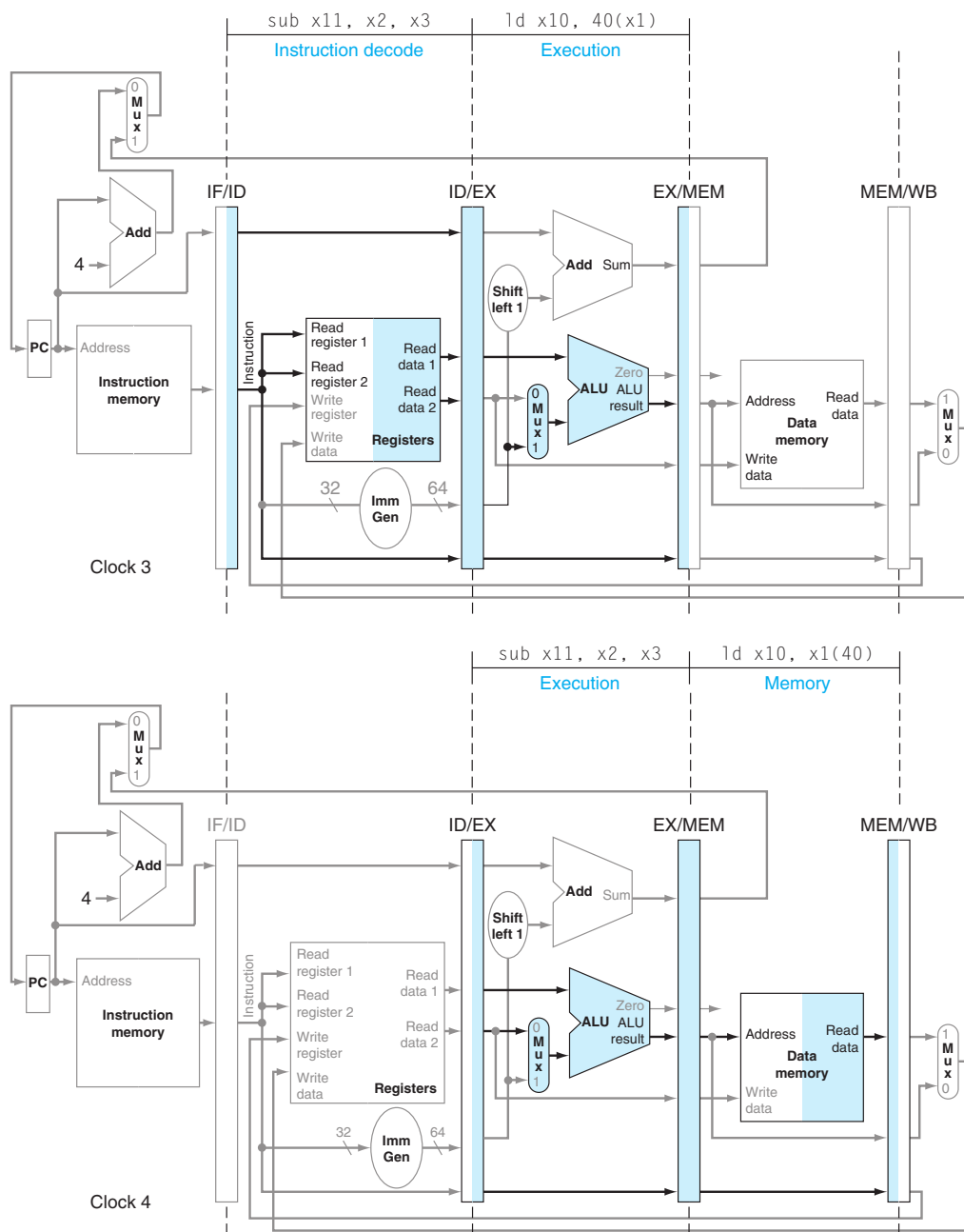


FIGURE e4.13.9 Single-cycle pipeline diagrams for clock cycles 3 (top diagram) and 4 (bottom diagram). In the third clock cycle in the top diagram, `ld` enters the EX stage. At the same time, `sub` enters ID. In the fourth clock cycle (bottom datapath), `ld` moves into MEM stage, reading memory using the address found in EX/MEM at the beginning of clock cycle 4. At the same time, the ALU subtracts and then places the difference into EX/MEM at the end of the clock cycle.

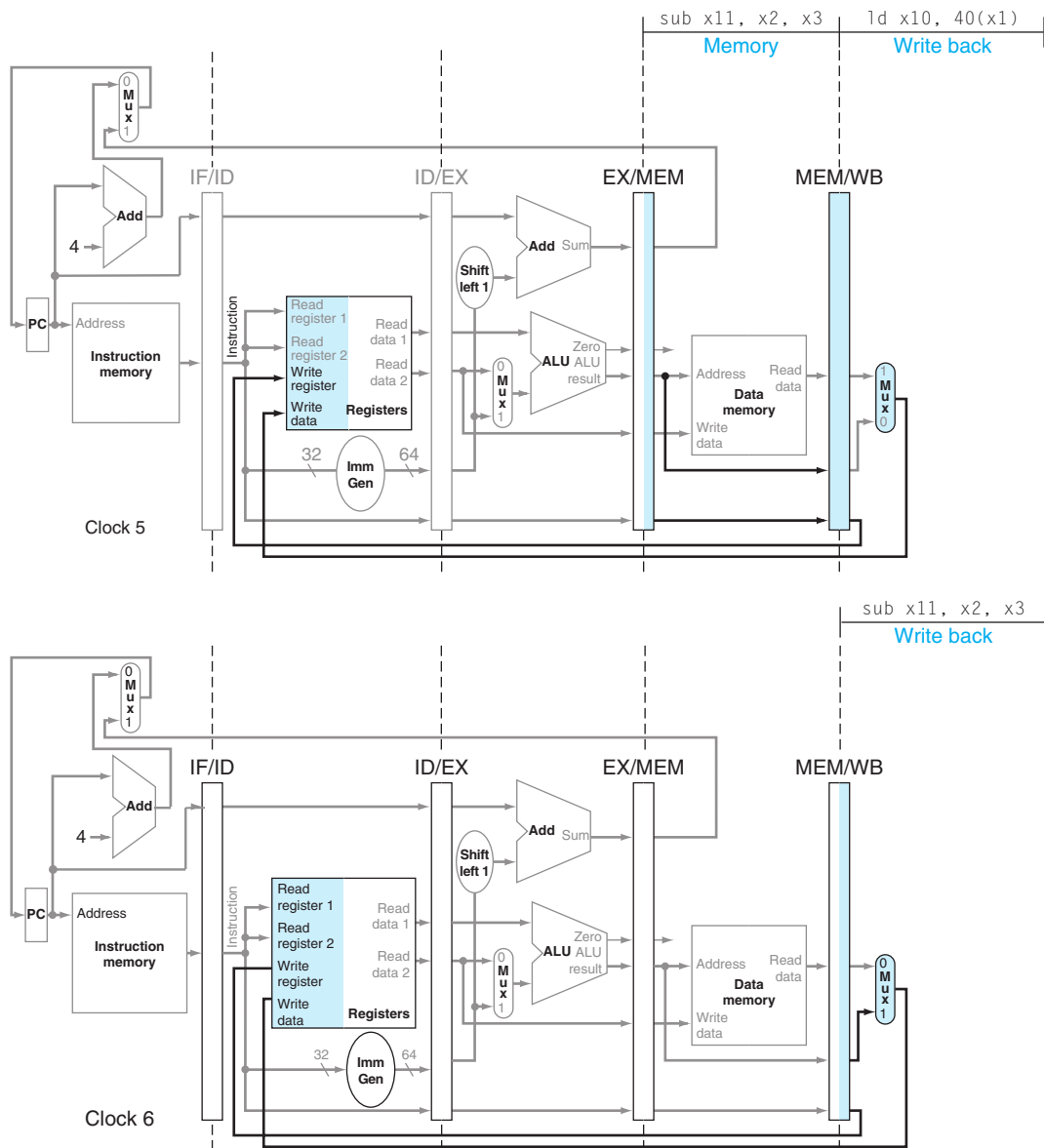


FIGURE e4.13.10 Single-cycle pipeline diagrams for clock cycles 5 (top diagram) and 6 (bottom diagram). In clock cycle 5, `ld` completes by writing the data in MEM/WB into register 10, and `sub` sends the difference in EX/MEM to MEM/WB. In the next clock cycle, `sub` writes the value in MEM/WB to register 11.

Figures e4.13.11 through e4.13.15 show these instructions proceeding through the nine clock cycles it takes them to complete execution, highlighting what is active in a stage and identifying the instruction associated with each stage during a clock cycle. If you examine them carefully, you may notice:

- In Figure e4.13.13 you can see the sequence of the destination register numbers from left to right at the bottom of the pipeline registers. The numbers advance to the right during each clock cycle, with the MEM/WB pipeline register supplying the number of the register written during the WB stage.
- When a stage is inactive, the values of control lines that are deasserted are shown as 0 or X (for don't care).
- Sequencing of control is embedded in the pipeline structure itself. First, all instructions take the same number of clock cycles, so there is no special control for instruction duration. Second, all control information is computed during instruction decode and then passed along by the pipeline registers.

Forwarding Illustrations

We can use the single-clock-cycle pipeline diagrams to show how forwarding operates, as well as how the control activates the forwarding paths. Consider the following code sequence in which the dependences have been highlighted:

```
sub  x2, x1, x3
and  x4, x2, x5
or   x4, x4, x2
add  x9, x4, x2
```

Figures e4.13.16 and e4.13.17 show the events in clock cycles 3–6 in the execution of these instructions.

Thus, in clock cycle 5, the forwarding unit selects the EX/MEM pipeline register for the upper input to the ALU and the MEM/WB pipeline register for the lower input to the ALU. The following `add` instruction reads both register `x4`, the target of the `and` instruction, and register `x2`, which the `sub` instruction has already written. Notice that the prior two instructions both write register `x4`, so the forwarding unit must pick the immediately preceding one (MEM stage).

In clock cycle 6, the forwarding unit thus selects the EX/MEM pipeline register, containing the result of the `or` instruction, for the upper ALU input but uses the non-forwarding register value for the lower input to the ALU.

Illustrating Pipelines with Stalls and Forwarding

We can use the single-clock-cycle pipeline diagrams to show how the control for stalls works. Figures e4.13.18 through e4.13.20 show the single-cycle diagram for clocks 2 through 7 for the following code sequence (dependences highlighted):

```
ld   x2, 40(x1)
and  x4, x2, x5
or   x4, x4, x2
add  x9, x4, x2
```

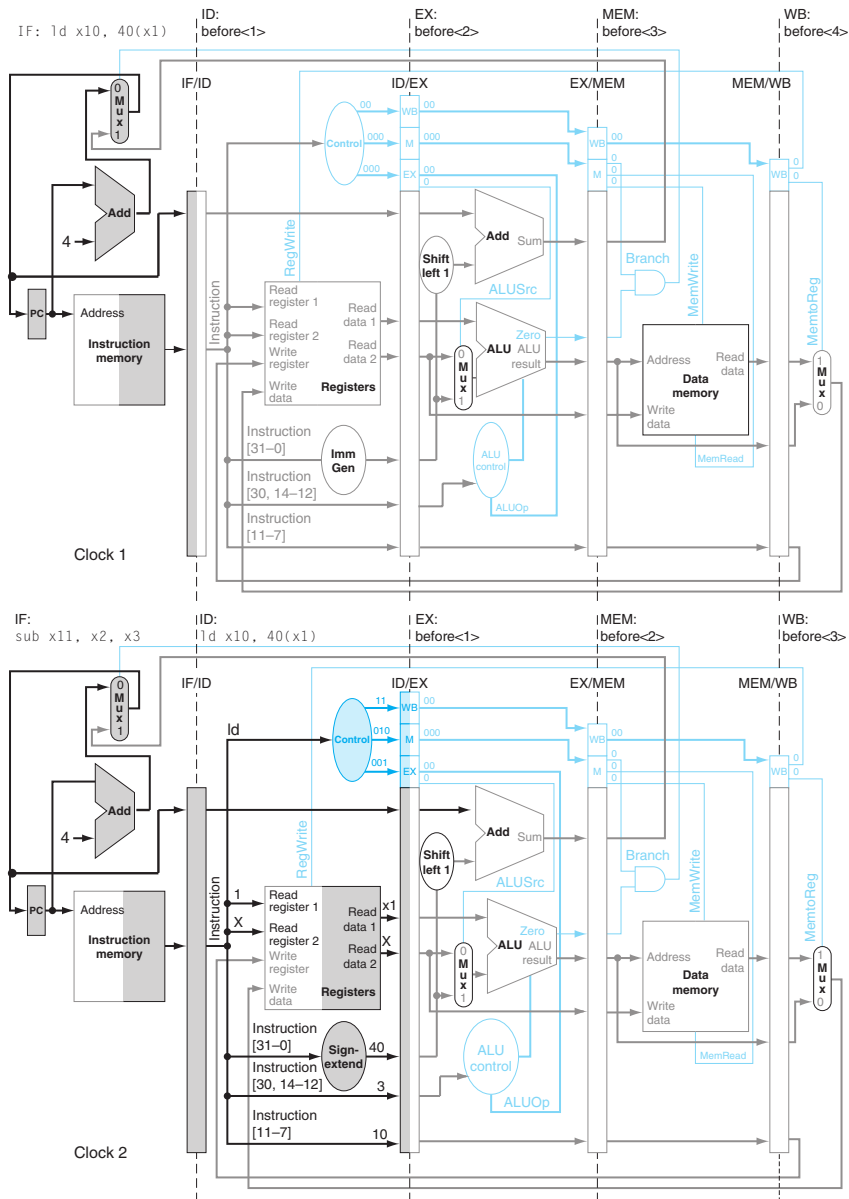


FIGURE e4.13.11 Clock cycles 1 and 2. The phrase “before i ” means the i th instruction before `ld`. The `ld` instruction in the top datapath is in the IF stage. At the end of the clock cycle, the `ld` instruction is in the IF/ID pipeline registers. In the second clock cycle, seen in the bottom datapath, the `ld` moves to the ID stage, and `sub` enters in the IF stage. Note that the values of the instruction fields and the selected source registers are shown in the ID stage. Hence, register `x1` and the constant 40, the operands of `ld`, are written into the ID/EX pipeline register. The number 10, representing the destination register number of `ld`, is also placed in ID/EX. The top of the ID/EX pipeline register shows the control values for `ld` to be used in the remaining stages. These control values can be read from the `ld` row of the table in Figure e4.18.

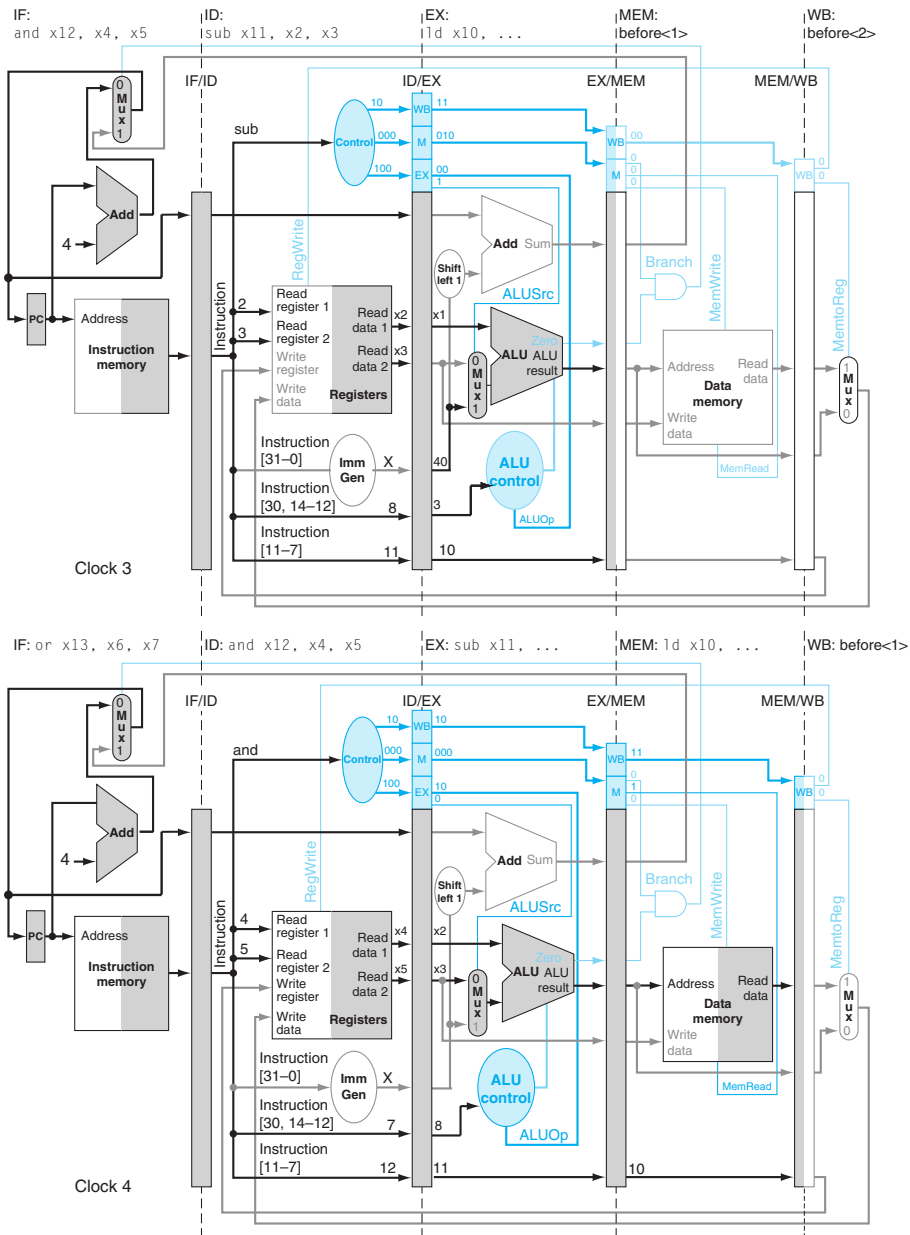


FIGURE e4.13.12 Clock cycles 3 and 4. In the top diagram, `ld` enters the EX stage in the third clock cycle, adding `x1` and `40` to form the address in the EX/MEM pipeline register. (The `ld` instruction is written `ld x10, ...` upon reaching EX, because the identity of instruction operands is not needed by EX or the subsequent stages. In this version of the pipeline, the actions of EX, MEM, and WB depend only on the instruction and its destination register or its target address.) At the same time, `sub` enters ID, reading registers `x2` and `x3`, and the `and` instruction starts IF. In the fourth clock cycle (bottom datapath), `ld` moves into MEM stage, reading memory using the value in EX/MEM as the address. In the same clock cycle, the ALU subtracts `x3` from `x2` and places the difference into EX/MEM, reads registers `x4` and `x5` during ID, and the `or` instruction enters IF. The two diagrams show the control signals being created in the ID stage and peeled off as they are used in subsequent pipe stages.

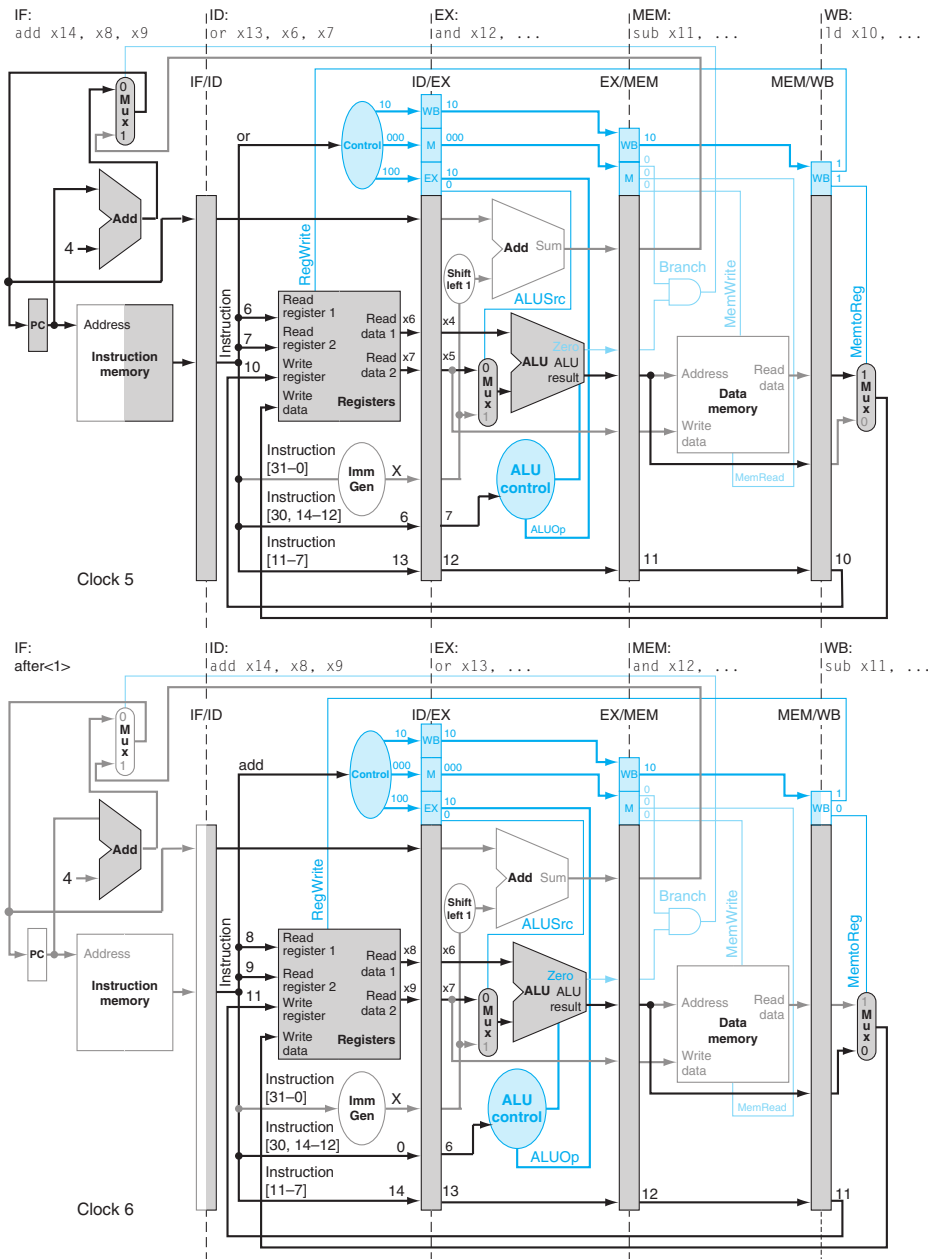


FIGURE e4.13.13 Clock cycles 5 and 6. With `add`, the final instruction in this example, entering IF in the top datapath, all instructions are engaged. By writing the data in MEM/WB into register 10, `ld` completes; both the data and the register number are in MEM/WB. In the same clock cycle, `sub` sends the difference in EX/MEM to MEM/WB, and the rest of the instructions move forward. In the next clock cycle, `sub` selects the value in MEM/WB to write to register number 11, again found in MEM/WB. The remaining instructions play follow-the-leader: the ALU calculates the OR of `x6` and `x7` for the `or` instruction in the EX stage, and registers `x8` and `x9` are read in the ID stage for the `add` instruction. The instructions after `add` are shown as inactive just to emphasize what occurs for the five instructions in the example. The phrase “after $\langle i \rangle$ ” means the i th instruction after `add`.

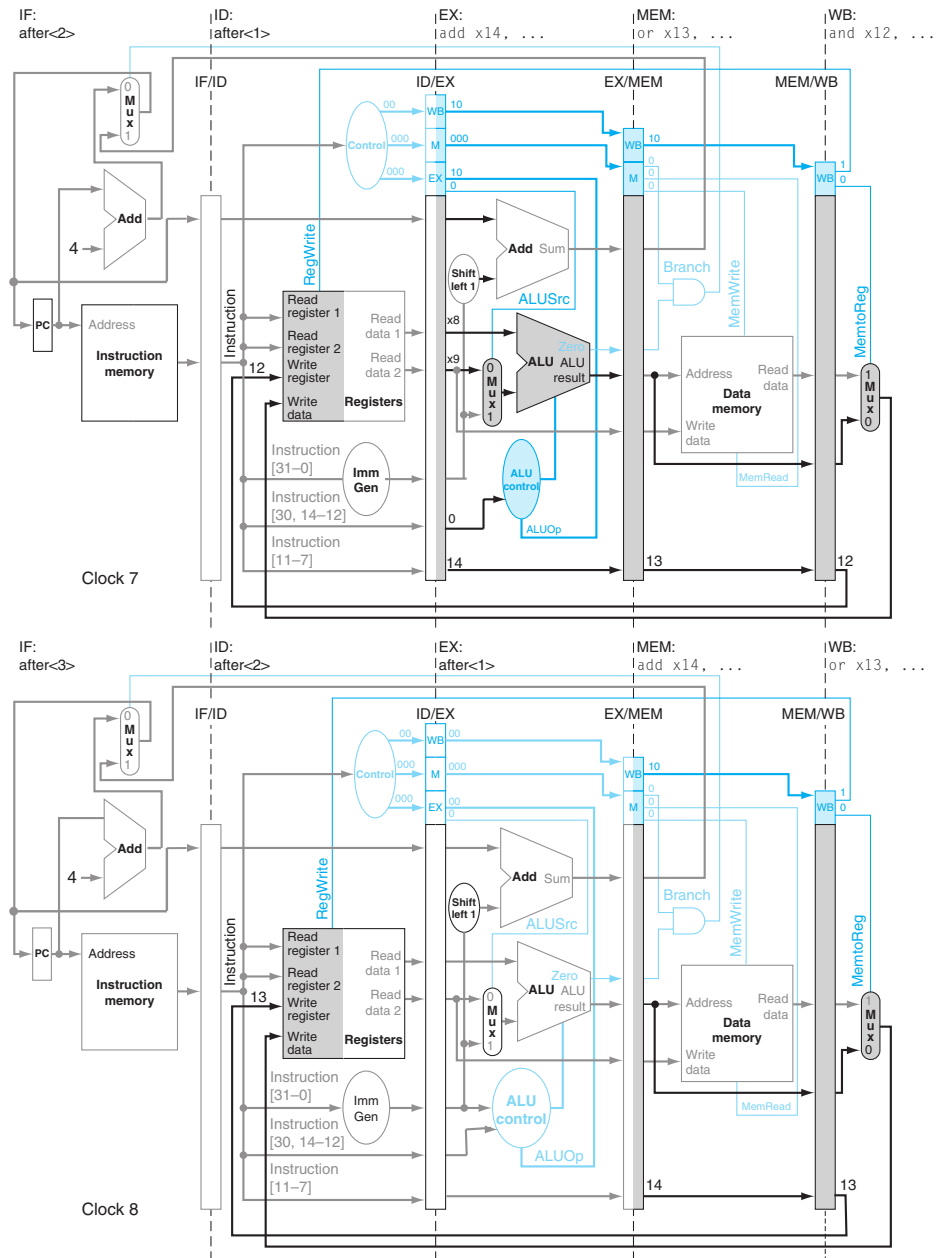


FIGURE e4.13.14 Clock cycles 7 and 8. In the top datapath, the `add` instruction brings up the rear, adding the values corresponding to registers x8 and x9 during the EX stage. The result of the `or` instruction is passed from EX/MEM to MEM/WB in the MEM stage, and the WB stage writes the result of the `and` instruction in MEM/WB to register x12. Note that the control signals are deasserted (set to 0) in the ID stage, since no instruction is being executed. In the following clock cycle (lower drawing), the WB stage writes the result to register x13, thereby completing `or`, and the MEM stage passes the sum from the `add` in EX/MEM to MEM/WB. The instructions after `add` are shown as inactive for pedagogical reasons.

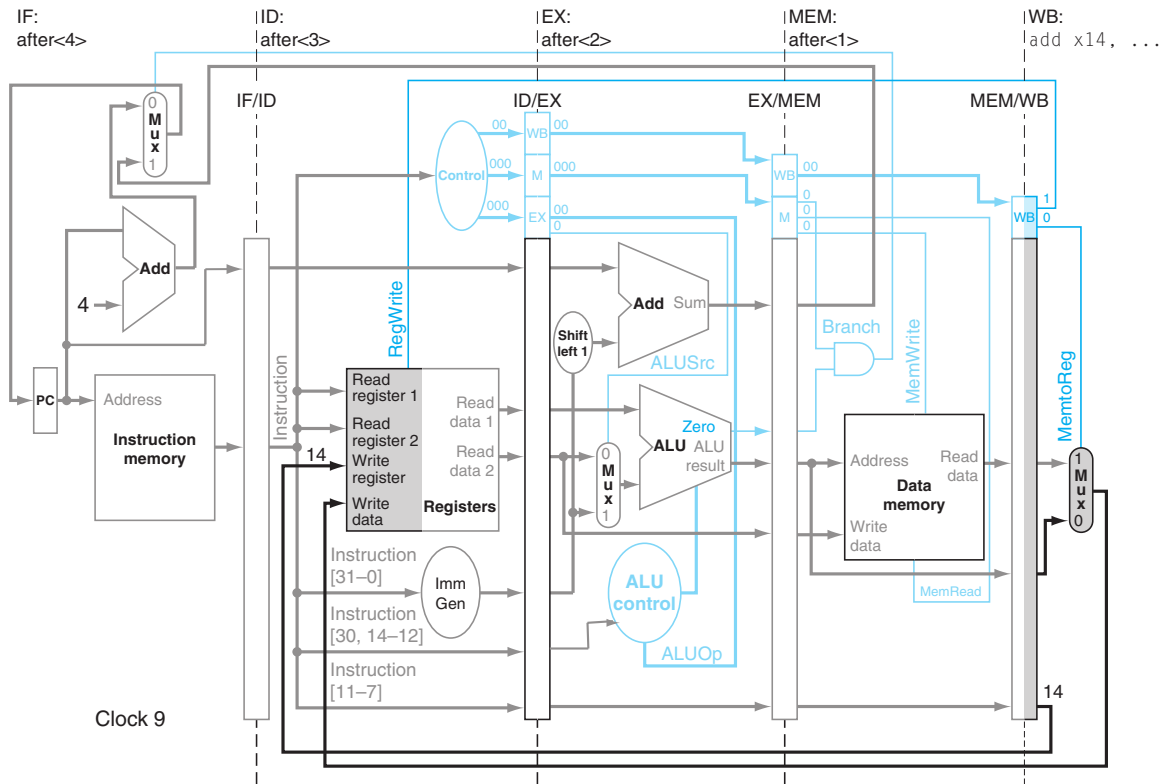


FIGURE e4.13.15 Clock cycle 9. The WB stage writes the ALU result in MEM/WB into register x14, completing add and the five-instruction sequence. The instructions after add are shown as inactive for pedagogical reasons.

 


FIGURE e4.13.16 Clock cycles 3 and 4 of the instruction sequence on page 366.e26. The bold lines are those active in a clock cycle, and the italicized register numbers in color indicate a hazard. The forwarding unit is highlighted by shading it when it is forwarding data to the ALU. The instructions before `sub` are shown as inactive just to emphasize what occurs for the four instructions in the example. Operand names are used in EX for control of forwarding; thus they are included in the instruction label for EX. Operand names are not needed in MEM or WB, so ... is used. Compare this with Figures e4.13.12 through e4.13.15, which show the datapath without forwarding where ID is the last stage to need operand information.

 


FIGURE e4.13.17 Clock cycles 5 and 6 of the instruction sequence on page 366.e26. The forwarding unit is highlighted when it is forwarding data to the ALU. The two instructions after *add* are shown as inactive just to emphasize what occurs for the four instructions in the example. The bold lines are those active in a clock cycle, and the italicized register numbers in color indicate a hazard.

 


FIGURE e4.13.18 Clock cycles 2 and 3 of the instruction sequence on page 366.e26 with a load replacing `sub`. The bold lines are those active in a clock cycle, the italicized register numbers in color indicate a hazard, and the ... in the place of operands means that their identity is information not needed by that stage. The values of the significant control lines, registers, and register numbers are labeled in the figures. The `and` and `or` instructions want to read the value created by the `ld` instruction in clock cycle 3, so the hazard detection unit stalls the `and` and `or` instructions. Hence, the hazard detection unit is highlighted.

 


FIGURE e4.13.19 Clock cycles 4 and 5 of the instruction sequence on page 366.e26 with a load replacing `sub`. The bubble is inserted in the pipeline in clock cycle 4, and then the `and` instruction is allowed to proceed in clock cycle 5. The forwarding unit is highlighted in clock cycle 5 because it is forwarding data from `ld` to the ALU. Note that in clock cycle 4, the forwarding unit forwards the address of the `ld` as if it were the contents of register `x2`; this is rendered harmless by the insertion of the bubble. The bold lines are those active in a clock cycle, and the italicized register numbers in color indicate a hazard.

 



FIGURE e4.13.20 Clock cycles 6 and 7 of the instruction sequence on page 366.e26 with a load replacing sub. Note that unlike in Figure e4.13.17, the stall allows the ld to complete, and so there is no forwarding from MEM/WB in clock cycle 6. Register x4 for the add in the EX stage still depends on the result from or in EX/MEM, so the forwarding unit passes the result to the ALU. The bold lines show ALU input lines active in a clock cycle, and the italicized register numbers indicate a hazard. The instructions after add are shown as inactive for pedagogical reasons.

Many of the difficulties of pipelining arise because of instruction set complications. Here are some examples:

- Widely variable instruction lengths and running times can lead to imbalance among pipeline stages and severely complicate hazard detection in a design pipelined at the instruction set level. This problem was overcome, initially in the DEC VAX 8500 in the late 1980s, using the micro-operations and micropipelined scheme that the Intel Core i7 employs today. Of course, the overhead of translation and maintaining correspondence between the micro-operations and the actual instructions remains.
- Sophisticated-addressing modes can lead to different sorts of problems. Addressing modes that update registers complicate hazard detection. Other addressing modes that require multiple memory accesses substantially complicate pipeline control and make it difficult to keep the pipeline flowing smoothly.
- Perhaps the best example is the DEC Alpha and the DEC NVAX. In comparable technology, the newer instruction set architecture of the Alpha allowed an implementation whose performance is more than twice as fast as NVAX. In another example, Bhandarkar and Clark [1991] compared the MIPS M/2000 and the DEC VAX 8700 by counting clock cycles of the SPEC benchmarks; they concluded that although the MIPS M/2000 executes more instructions, the VAX on average executes 2.7 times as many clock cycles, so the MIPS is faster.

*Nine-tenths of wisdom
consists of being wise
in time.*

American proverb

 

PIPELINING

instruction latency The inherent execution time for an instruction.

4.15 Concluding Remarks

As we have seen in this chapter, both the datapath and control for a processor can be designed starting with the instruction set architecture and an understanding of the basic characteristics of the technology. In [Section 4.3](#), we saw how the datapath for an RISC-V processor could be constructed based on the architecture and the decision to build a single-cycle implementation. Of course, the underlying technology also affects many design decisions by dictating what components can be used in the datapath, as well as whether a single-cycle implementation even makes sense.


Pipelining improves throughput but not the inherent execution time, or **instruction latency**, of instructions; for some instructions, the latency is similar in length to the single-cycle approach. Multiple instruction issue adds additional datapath hardware to allow multiple instructions to begin every clock cycle, but at an increase in effective latency. Pipelining was presented as reducing the clock cycle time of the simple single-cycle datapath. Multiple instruction issue, in comparison, clearly focuses on reducing *clock cycles per instruction* (CPI).

Pipelining and multiple issue both attempt to exploit instruction-level parallelism. The presence of data and control dependences, which can become hazards, are the primary limitations on how much parallelism can be exploited. Scheduling and speculation via **prediction**, both in hardware and in software, are the primary techniques used to reduce the performance impact of dependences.


We showed that unrolling the DGEMM loop four times exposed more instructions that could take advantage of the out-of-order execution engine of the Core i7 to more than double performance.

The switch to longer pipelines, multiple instruction issue, and dynamic scheduling in the mid-1990s helped sustain the 60% per year processor performance increase that started in the early 1980s. As mentioned in [Chapter 1](#), these microprocessors preserved the sequential programming model, but they eventually ran into the power wall. Thus, the industry was forced to switch to multiprocessors, which exploit parallelism at much coarser levels (the subject of [Chapter 6](#)). This trend has also caused designers to reassess the energy-performance implications of some of the inventions since the mid-1990s, resulting in a simplification of pipelines in the more recent versions of microarchitectures.

 To sustain the advances in processing performance via parallel processors, Amdahl's law suggests that another part of the system will become the bottleneck. That bottleneck is the topic of the next chapter: the **memory hierarchy**.



PREDICTION

 

HIERARCHY



Historical Perspective and Further Reading

This section, which appears online, discusses the history of the first pipelined processors, the earliest superscalars, and the development of out-of-order and speculative techniques, as well as important developments in the accompanying compiler technology.

4.17

Exercises

4.1 Consider the following instruction:

Instruction: `and rd, rs1, rs2`

Interpretation: `Reg[rd] = Reg[rs1] AND Reg[rs2]`

4.1.1 [5] <§4.3> What are the values of control signals generated by the control in [Figure 4.10](#) for this instruction?



Historical Perspective and Further Reading

supercomputer: *Any machine still on the drawing board.*

Stan Kelly-Bootle, *The Devil's DP Dictionary*, 1981

This section discusses the history of the original pipelined processors, the earliest superscalars, and the development of out-of-order and speculative techniques, as well as important developments in the accompanying compiler technology.

It is generally agreed that one of the first general-purpose pipelined computers was Stretch, the IBM 7030 (Figure e4.16.1). Stretch followed the IBM 704 and had a goal of being 100 times faster than the 704. The goals were a “stretch” of the state of the art at that time—hence the nickname. The plan was to obtain a factor of 1.6 from overlapping fetch, decode, and execute by using a four-stage pipeline. Apparently, the rest was to come from much more hardware and faster logic. Stretch was also a training ground for both the architects of the IBM 360, Gerrit Blaauw and Fred Brooks, Jr., and the architect of the IBM RS/6000, John Cocke.



FIGURE e4.16.1 The Stretch computer, one of the first pipelined computers.

Control Data Corporation (CDC) delivered what is considered to be the first supercomputer, the CDC 6600, in 1964 (Figure e4.16.2). The core instructions of Cray's subsequent computers have many similarities to those of the original CDC 6600. The CDC 6600 was unique in many ways. The interaction between pipelining and instruction set design was understood, and the instruction set was kept simple to promote pipelining. The CDC 6600 also used an advanced packaging technology. James Thornton's book [1970] provides an excellent description of the entire computer, from technology to architecture, and includes a foreword by Seymour Cray. (Unfortunately, this book is currently out of print.) Jim Smith, then working at CDC, developed the original 2-bit branch prediction scheme and explored several techniques for enhancing instruction issue for the CDC Cyber 180/990. Cray, Thornton, and Smith have each won the ACM Eckert-Mauchly Award (in 1989, 1994, and 1999, respectively).

The IBM 360/91 introduced many new concepts, including dynamic detection of memory hazards, generalized forwarding, and reservation stations (Figure e4.16.3). The approach is normally named *Tomasulo's algorithm*, after an engineer who worked on the project. The team that created the 360/91 was led by Michael Flynn, who was given the 1992 ACM Eckert-Mauchly Award, in part for his contributions to the IBM 360/91; in 1997, the same award went to Robert Tomasulo for his pioneering work on out-of-order processing.

The internal organization of the 360/91 shares many features with the Pentium III and Pentium 4, as well as with several other microprocessors. One major



FIGURE e4.16.2 The CDC 6600, the first supercomputer.



FIGURE e4.16.3 The IBM 360/91 pushed the state of the art in pipelined execution when it was unveiled in 1966.

difference was that there was no branch prediction in the 360/91 and hence no speculation. Another major difference was that there was no commit unit, so once the instructions finished execution, they updated the registers. Out-of-order instruction commit led to *imprecise interrupts*, which proved to be unpopular and led to the commit units in dynamically scheduled pipelined processors since that time. Although the 360/91 was not a success, its key ideas were resurrected later and exist in some form in the majority of microprocessors of the last decade.

Improving Pipelining Effectiveness and Adding Multiple Issue

The RISC processors refined the notion of compiler-scheduled pipelines in the early 1980s. The concepts of delayed branches and delayed loads—common in microprogramming—were extended into the high-level architecture. In fact, the Stanford processor that led to the commercial MIPS architecture was called “Microprocessor without Interlocked Pipelined Stages” because it was up to the assembler or compiler to avoid data hazards.

In addition to its contribution to the development of the RISC concepts, IBM did pioneering work on multiple issue. In the 1960s, a project called ACS was underway. It included multiple-instruction issue concepts and the notion of integrated compiler and architecture design, but it never reached product stage. The earliest proposal for a superscalar processor that dynamically makes issue decisions was

by John Cocke; he described the key ideas in several talks in the mid-1980s and, with Tilak Agarwala, coined the name *superscalar*. This original design was a two-issue machine named Cheetah, which was followed by a more widely discussed four-issue machine named America. The IBM Power-1 architecture, used in the RS/6000 line, is based on these ideas, and the PowerPC is a variation of the Power-1 architecture. Cocke won the Turing Award, the highest award in computer science and engineering, for his architecture work.

Static multiple issue, as exemplified by the *long instruction word* (LIW) or sometimes *very long instruction word* (VLIW) approaches, appeared in real designs before the superscalar approach. In fact, the earliest multiple-issue machines were special-purpose attached processors designed for scientific applications. Culler Scientific and Floating Point Systems were two of the most prominent manufacturers of such computers. Another inspiration for the use of multiple operations per instruction came from those working on microcode compilers. Such inspiration led to a research project at Yale led by Josh Fisher, who coined the term VLIW. Cydrome and Multiflow were two early companies involved in building mini-supercomputers using processors with multiple-issue capability. These processors, built with bit-slice and multiple-chip gate array implementations, arrived on the market at the same time as the initial RISC microprocessors. Despite some promising performance on high-end scientific codes, the much better cost/performance of the microprocessor-based computers doomed the first generation of VLIW computers. Bob Rau and Josh Fisher won the Eckert-Mauchly Award in 2002 and 2003, respectively, for their contributions to the development of multiple processors and software techniques to exploit ILP.

The very beginning of the 1990s saw the first superscalar processors using static scheduling and no speculation, including versions of the MIPS and PowerPC architectures. The early 1990s also saw important research at a number of universities, including Wisconsin, Stanford, Illinois, and Michigan, focused on techniques for exploiting additional ILP through multiple issue with and without speculation. These research insights were used to build dynamically scheduled, speculative processors, including the Motorola 88110, MIPS R10000, DEC Alpha 21264, PowerPC 603, and the Intel Pentium Pro, Pentium III, and Pentium 4.

In 2001, Intel introduced the IA-64 architecture and its first implementation, Itanium. Itanium represented a return to a more compiler-intensive approach that they called EPIC. EPIC represented a considerable enhancement over the early VLIW architectures, removing many of their drawbacks. It has had modest sales. In 2013, the IA-64 architecture is used only in low-volume, high-end servers and is outnumbered by x86 processors by more than 100:1.

Compiler Technology for Exploiting ILP

Successful development of processors to exploit ILP has depended on progress in compiler technology. The concept of loop unrolling was understood early, and a number of companies and researchers—including Floating Point Systems, Cray, and the Stanford MIPS project—developed compilers that made use of loop

unrolling and pipeline scheduling to improve instruction throughput. A special-purpose processor called WARP, designed at Carnegie Mellon University, inspired the development of software pipelining, an approach that symbolically unrolls loops.

To exploit higher levels of ILP, more aggressive compiler technology was needed. The VLIW project at Yale developed the concept of trace scheduling that Multiflow implemented in their compilers. Trace scheduling relies on aggressive loop unrolling and path prediction to compile favored execution traces efficiently. The Cydrome designers created early versions of predication and support for software pipelining. Hwu at Illinois worked on extended versions of loop unrolling, called *superblocks*, and techniques for compiling with predication. The concepts from Multiflow, Cydrome, and the research group at Illinois served as the architectural and compiler basis for the IA-64 architecture.

Further Reading

Bhandarkar, D. and D.W. Clark [1991]. “Performance from architecture: Comparing a RISC and a CISC with similar hardware organizations,” *Proc. Fourth Conf. on Architectural Support for Programming Languages and Operating Systems*, IEEE/ACM (April), Palo Alto, CA, 310–19.

A quantitative comparison of RISC and CISC written by scholars who argued for CISCs as well as built them; they conclude that MIPS is between 2 and 4 times faster than a VAX built with similar technology, with a mean of 2.7.

Fisher, J.A. and B.R. Rau [1993]. *Journal of Supercomputing* (January), Kluwer.

This entire issue is devoted to the topic of exploiting ILP. It contains papers on both the architecture and software and is a wonderful source for further references.

Hennessy, J. L. and D. A. Patterson [2001]. *Computer Architecture: A Quantitative Approach*, fourth edition, Morgan Kaufmann, San Francisco.

Chapter 2 and Appendix A go into considerably more detail about pipelined processors (almost 200 pages), including superscalar processors and VLIW processors. Appendix G describes Itanium.

Jouppi, N.P. and D.W. Wall [1989]. “Available instruction-level parallelism for superscalar and superpipelined processors,” *Proc. Third Conf. on Architectural Support for Programming Languages and Operating Systems*, IEEE/ACM (April), Boston, 272–82.

A comparison of deeply pipelined (also called superpipelined) and superscalar systems.

Kogge, P. M. [1981]. *The Architecture of Pipelined Computers*, McGraw-Hill, New York.

A formal text on pipelined control, with emphasis on underlying principles.

Russell, R. M. [1978]. “The CRAY-1 computer system,” *Comm. of the ACM* 21:1 (January), 63–72.

A short summary of a classic computer that uses vectors of operations to remove pipeline stalls.

Smith, A. and J. Lee [1984]. “Branch prediction strategies and branch target buffer design,” *Computer* 17:1 (January), 6–22.

An early survey on branch prediction.

Smith, J. E. and A. R. Plezkun [1988]. "Implementing precise interrupts in pipelined processors", *IEEE Trans. on Computers* 37:5 (May), 562–73.

Covers the difficulties in interrupting pipelined computers.

Thornton, J. E. [1970]. *Design of a Computer. The Control Data 6600*, Glenview, IL: Scott, Foresman.

A classic book describing a classic computer, considered the first supercomputer.

4.1.2 [5] <§4.3> Which resources (blocks) perform a useful function for this instruction?

4.1.3 [10] <§4.3> Which resources (blocks) produce no output for this instruction? Which resources produce output that is not used?

4.2 [10] <§4.4> Explain each of the “don’t cares” in [Figure 4.18](#).

4.3 Consider the following instruction mix:

R-type	I-type (non-ld)	Load	Store	Branch	Jump
24%	28%	25%	10%	11%	2%

4.3.1 [5] <§4.4> What fraction of all instructions use data memory?

4.3.2 [5] <§4.4> What fraction of all instructions use instruction memory?

4.3.3 [5] <§4.4> What fraction of all instructions use the sign extend?

4.3.4 [5] <§4.4> What is the sign extend doing during cycles in which its output is not needed?

4.4 When silicon chips are fabricated, defects in materials (e.g., silicon) and manufacturing errors can result in defective circuits. A very common defect is for one signal wire to get “broken” and always register a logical 0. This is often called a “stuck-at-0” fault.

4.4.1 [5] <§4.4> Which instructions fail to operate correctly if the MemToReg wire is stuck at 0?

4.4.2 [5] <§4.4> Which instructions fail to operate correctly if the ALUSrc wire is stuck at 0?

4.5 In this exercise, we examine in detail how an instruction is executed in a single-cycle datapath. Problems in this exercise refer to a clock cycle in which the processor fetches the following instruction word: 0x00c6ba23.

4.5.1 [10] <§4.4> What are the values of the ALU control unit’s inputs for this instruction?

4.5.2 [5] <§4.4> What is the new PC address after this instruction is executed? Highlight the path through which this value is determined.

4.5.3 [10] <§4.4> For each mux, show the values of its inputs and outputs during the execution of this instruction. List values that are register outputs at Reg [xn].

4.5.4 [10] <§4.4> What are the input values for the ALU and the two add units?

4.5.5 [10] <§4.4> What are the values of all inputs for the registers unit?

4.6 Section 4.4 does not discuss I-type instructions like `addi` or `andi`.

4.6.1 [5] <§4.4> What additional logic blocks, if any, are needed to add I-type instructions to the CPU shown in Figure 4.21? Add any necessary logic blocks to Figure 4.21 and explain their purpose.

4.6.2 [10] <§4.4> List the values of the signals generated by the control unit for `addi`. Explain the reasoning for any “don’t care” control signals.

4.7 Problems in this exercise assume that the logic blocks used to implement a processor’s datapath have the following latencies:

I-Mem / D-Mem	Register File	Mux	ALU	Adder	Single gate	Register Read	Register Setup	Sign extend	Control
250 ps	150 ps	25 ps	200 ps	150 ps	5 ps	30 ps	20 ps	50 ps	50 ps

“Register read” is the time needed after the rising clock edge for the new register value to appear on the output. This value applies to the PC only. “Register setup” is the amount of time a register’s data input must be stable before the rising edge of the clock. This value applies to both the PC and Register File.

4.7.1 [5] <§4.4> What is the latency of an R-type instruction (i.e., how long must the clock period be to ensure that this instruction works correctly)?

4.7.2 [10] <§4.4> What is the latency of `ld`? (Check your answer carefully. Many students place extra muxes on the critical path.)

4.7.3 [10] <§4.4> What is the latency of `sd`? (Check your answer carefully. Many students place extra muxes on the critical path.)

4.7.4 [5] <§4.4> What is the latency of `beq`?

4.7.5 [5] <§4.4> What is the latency of an I-type instruction?

4.7.6 [5] <§4.4> What is the minimum clock period for this CPU?

4.8 [10] <§4.4> Suppose you could build a CPU where the clock cycle time was different for each instruction. What would the speedup of this new CPU be over the CPU presented in Figure 4.21 given the instruction mix below?

R-type/I-type (non-ld)	ld	sd	beq
52%	25%	11%	12%

4.9 Consider the addition of a multiplier to the CPU shown in Figure 4.21. This addition will add 300 ps to the latency of the ALU, but will reduce the number of instructions by 5% (because there will no longer be a need to emulate the multiply instruction).

4.9.1 [5] <\$4.4> What is the clock cycle time with and without this improvement?

4.9.2 [10] <\$4.4> What is the speedup achieved by adding this improvement?

4.9.3 [10] <\$4.4> What is the slowest the new ALU can be and still result in improved performance?

4.10 When processor designers consider a possible improvement to the processor datapath, the decision usually depends on the cost/performance trade-off. In the following three problems, assume that we are beginning with the datapath from Figure 4.21, the latencies from Exercise 4.7, and the following costs:

I-Mem	Register File	Mux	ALU	Adder	D-Mem	Single Register	Sign extend	Single gate	Control
1000	200	10	100	30	2000	5	100	1	500

Suppose doubling the number of general purpose registers from 32 to 64 would reduce the number of `ld` and `sd` instruction by 12%, but increase the latency of the register file from 150 ps to 160 ps and double the cost from 200 to 400. (Use the instruction mix from Exercise 4.8 and ignore the other effects on the ISA discussed in Exercise 2.18.)

4.10.1 [5] <\$4.4> What is the speedup achieved by adding this improvement?

4.10.2 [10] <\$4.4> Compare the change in performance to the change in cost.

4.10.3 [10] <\$4.4> Given the cost/performance ratios you just calculated, describe a situation where it makes sense to add more registers and describe a situation where it doesn't make sense to add more registers.

4.11 Examine the difficulty of adding a proposed `lwi.d rd, rs1, rs2` (“Load With Increment”) instruction to RISC-V.

Interpretation: $\text{Reg}[\text{rd}] = \text{Mem}[\text{Reg}[\text{rs1}] + \text{Reg}[\text{rs2}]]$

4.11.1 [5] <\$4.4> Which new functional blocks (if any) do we need for this instruction?

4.11.2 [5] <\$4.4> Which existing functional blocks (if any) require modification?

4.11.3 [5] <\$4.4> Which new data paths (if any) do we need for this instruction?

4.11.4 [5] <\$4.4> What new signals do we need (if any) from the control unit to support this instruction?

4.12 Examine the difficulty of adding a proposed `swap rs1, rs2` instruction to RISC-V.

Interpretation: `Reg[rs2]=Reg[rs1]; Reg[rs1]=Reg[rs2]`

4.12.1 [5] <§4.4> Which new functional blocks (if any) do we need for this instruction?

4.12.2 [10] <§4.4> Which existing functional blocks (if any) require modification?

4.12.3 [5] <§4.4> What new data paths do we need (if any) to support this instruction?

4.12.4 [5] <§4.4> What new signals do we need (if any) from the control unit to support this instruction?

4.12.5 [5] <§4.4> Modify [Figure 4.21](#) to demonstrate an implementation of this new instruction.

4.13 Examine the difficulty of adding a proposed `ss rs1, rs2, imm` (Store Sum) instruction to RISC-V.

Interpretation: `Mem[Reg[rs1]]=Reg[rs2]+immediate`

4.13.1 [10] <§4.4> Which new functional blocks (if any) do we need for this instruction?

4.13.2 [10] <§4.4> Which existing functional blocks (if any) require modification?

4.13.3 [5] <§4.4> What new data paths do we need (if any) to support this instruction?

4.13.4 [5] <§4.4> What new signals do we need (if any) from the control unit to support this instruction?

4.13.5 [5] <§4.4> Modify [Figure 4.21](#) to demonstrate an implementation of this new instruction.

4.14 [5] <§4.4> For which instructions (if any) is the Imm Gen block on the critical path?

4.15 `ld` is the instruction with the longest latency on the CPU from [Section 4.4](#). If we modified `ld` and `sd` so that there was no offset (i.e., the address to be loaded from/stored to must be calculated and placed in `rs1` before calling `ld/sd`), then no instruction would use both the ALU and Data memory. This would allow us to reduce the clock cycle time. However, it would also increase the number of instructions, because many `ld` and `sd` instructions would need to be replaced with `ld/add` or `sd/add` combinations.

4.15.1 [5] <§4.4> What would the new clock cycle time be?

4.15.2 [10] <§4.4> Would a program with the instruction mix presented in Exercise 4.7 run faster or slower on this new CPU? By how much? (For simplicity, assume every `ld` and `sd` instruction is replaced with a sequence of two instructions.)

4.15.3 [5] <§4.4> What is the primary factor that influences whether a program will run faster or slower on the new CPU?

4.15.4 [5] <§4.4> Do you consider the original CPU (as shown in [Figure 4.21](#)) a better overall design; or do you consider the new CPU a better overall design? Why?

4.16 In this exercise, we examine how pipelining affects the clock cycle time of the processor. Problems in this exercise assume that individual stages of the datapath have the following latencies:

IF	ID	EX	MEM	WB
250 ps	350 ps	150 ps	300 ps	200 ps

Also, assume that instructions executed by the processor are broken down as follows:

ALU/Logic	Jump/Branch	Load	Store
45%	20%	20%	15%

4.16.1 [5] <§4.5> What is the clock cycle time in a pipelined and non-pipelined processor?

4.16.2 [10] <§4.5> What is the total latency of an `ld` instruction in a pipelined and non-pipelined processor?

4.16.3 [10] <§4.5> If we can split one stage of the pipelined datapath into two new stages, each with half the latency of the original stage, which stage would you split and what is the new clock cycle time of the processor?

4.16.4 [10] <§4.5> Assuming there are no stalls or hazards, what is the utilization of the data memory?

4.16.5 [10] <§4.5> Assuming there are no stalls or hazards, what is the utilization of the write-register port of the “Registers” unit?

4.17 [10] <§4.5> What is the minimum number of cycles needed to completely execute n instructions on a CPU with a k stage pipeline? Justify your formula.

4.18 [5] <§4.5> Assume that `x11` is initialized to 11 and `x12` is initialized to 22. Suppose you executed the code below on a version of the pipeline from [Section 4.5](#) that does not handle data hazards (i.e., the programmer is responsible for

addressing data hazards by inserting NOP instructions where necessary). What would the final values of registers x13 and x14 be?

```
addi    x11, x12, 5
add     x13, x11, x12
addi    x14, x11, 15
```

4.19 [10] <§4.5> Assume that x11 is initialized to 11 and x12 is initialized to 22. Suppose you executed the code below on a version of the pipeline from [Section 4.5](#) that does not handle data hazards (i.e., the programmer is responsible for addressing data hazards by inserting NOP instructions where necessary). What would the final values of register x15 be? Assume the register file is written at the beginning of the cycle and read at the end of a cycle. Therefore, an ID stage will return the results of a WB state occurring during the same cycle. See [Section 4.7](#) and [Figure 4.51](#) for details.

```
addi    x11, x12, 5
add     x13, x11, x12
addi    x14, x11, 15
add     x15, x11, x11
```

4.20 [5] <§4.5> Add NOP instructions to the code below so that it will run correctly on a pipeline that does not handle data hazards.

```
addi    x11, x12, 5
add     x13, x11, x12
addi    x14, x11, 15
add     x15, x13, x12
```

4.21 Consider a version of the pipeline from [Section 4.5](#) that does not handle data hazards (i.e., the programmer is responsible for addressing data hazards by inserting NOP instructions where necessary). Suppose that (after optimization) a typical n -instruction program requires an additional $4*n$ NOP instructions to correctly handle data hazards.

4.21.1 [5] <§4.5> Suppose that the cycle time of this pipeline without forwarding is 250 ps. Suppose also that adding forwarding hardware will reduce the number of NOPs from $.4*n$ to $.05*n$, but increase the cycle time to 300 ps. What is the speedup of this new pipeline compared to the one without forwarding?

4.21.2 [10] <§4.5> Different programs will require different amounts of NOPs. How many NOPs (as a percentage of code instructions) can remain in the typical program before that program runs slower on the pipeline with forwarding?

4.21.3 [10] <§4.5> Repeat 4.21.2; however, this time let x represent the number of NOP instructions relative to n . (In 4.21.2, x was equal to $.4$.) Your answer will be with respect to x .

4.21.4 [10] <\$4.5> Can a program with only $.075 \cdot n$ NOPs possibly run faster on the pipeline with forwarding? Explain why or why not.

4.21.5 [10] <\$4.5> At minimum, how many NOPs (as a percentage of code instructions) must a program have before it can possibly run faster on the pipeline with forwarding?

4.22 [5] <\$4.5> Consider the fragment of RISC-V assembly below:

```
sd    x29, 12(x16)
ld    x29, 8(x16)
sub   x17, x15, x14
beqz  x17, label
add   x15, x11, x14
sub   x15, x30, x14
```

Suppose we modify the pipeline so that it has only one memory (that handles both instructions and data). In this case, there will be a structural hazard every time a program needs to fetch an instruction during the same cycle in which another instruction accesses data.

4.22.1 [5] <\$4.5> Draw a pipeline diagram to show where the code above will stall.

4.22.2 [5] <\$4.5> In general, is it possible to reduce the number of stalls/NOPs resulting from this structural hazard by reordering code?

4.22.3 [5] <\$4.5> Must this structural hazard be handled in hardware? We have seen that data hazards can be eliminated by adding NOPs to the code. Can you do the same with this structural hazard? If so, explain how. If not, explain why not.

4.22.4 [5] <\$4.5> Approximately how many stalls would you expect this structural hazard to generate in a typical program? (Use the instruction mix from Exercise 4.8.)

4.23 If we change load/store instructions to use a register (without an offset) as the address, these instructions no longer need to use the ALU. (See Exercise 4.15.) As a result, the MEM and EX stages can be overlapped and the pipeline has only four stages.

4.23.1 [10] <\$4.5> How will the reduction in pipeline depth affect the cycle time?

4.23.2 [5] <\$4.5> How might this change improve the performance of the pipeline?

4.23.3 [5] <\$4.5> How might this change degrade the performance of the pipeline?

4.24 [10] <§4.7> Which of the two pipeline diagrams below better describes the operation of the pipeline's hazard detection unit? Why?

Choice 1:

```
ld x11, 0(x12):    IF ID EX ME WB
add x13, x11, x14:  IF ID EX..ME WB
or x15, x16, x17:   IF ID..EX ME WB
```

Choice 2:

```
ld x11, 0(x12):    IF ID EX ME WB
add x13, x11, x14:  IF ID..EX ME WB
or x15, x16, x17:   IF..ID EX ME WB
```

4.25 Consider the following loop.

```
LOOP: ld    x10, 0(x13)
      ld    x11, 8(x13)
      add   x12, x10, x11
      subi  x13, x13, 16
      bnez  x12, LOOP
```

Assume that perfect branch prediction is used (no stalls due to control hazards), that there are no delay slots, that the pipeline has full forwarding support, and that branches are resolved in the EX (as opposed to the ID) stage.

4.25.1 [10] <§4.7> Show a pipeline execution diagram for the first two iterations of this loop.

4.25.2 [10] <§4.7> Mark pipeline stages that do not perform useful work. How often while the pipeline is full do we have a cycle in which all five pipeline stages are doing useful work? (Begin with the cycle during which the `subi` is in the IF stage. End with the cycle during which the `bnez` is in the IF stage.)

4.26 This exercise is intended to help you understand the cost/complexity/performance trade-offs of forwarding in a pipelined processor. Problems in this exercise refer to pipelined datapaths from [Figure 4.53](#). These problems assume that, of all the instructions executed in a processor, the following fraction of these instructions has a particular type of RAW data dependence. The type of RAW data dependence is identified by the stage that produces the result (EX or MEM) and the next instruction that consumes the result (1st instruction that follows the one that produces the result, 2nd instruction that follows, or both). We assume that the register write is done in the first half of the clock cycle and that register reads are done in the second half of the cycle, so “EX to 3rd” and “MEM to 3rd” dependences

are not counted because they cannot result in data hazards. We also assume that branches are resolved in the EX stage (as opposed to the ID stage), and that the CPI of the processor is 1 if there are no data hazards.

EX to 1 st Only	MEM to 1 st Only	EX to 2 nd Only	MEM to 2 nd Only	EX to 1 st and EX to 2 nd
5%	20%	5%	10%	10%

Assume the following latencies for individual pipeline stages. For the EX stage, latencies are given separately for a processor without forwarding and for a processor with different kinds of forwarding.

IF	ID	EX (no FW)	EX (full FW)	EX (FW from EX/MEM only)	EX (FW from MEM/WB only)	MEM	WB
120 ps	100 ps	110 ps	130 ps	120 ps	120 ps	120 ps	100 ps

4.26.1 [5] <§4.7> For each RAW dependency listed above, give a sequence of at least three assembly statements that exhibits that dependency.

4.26.2 [5] <§4.7> For each RAW dependency above, how many NOPs would need to be inserted to allow your code from 4.26.1 to run correctly on a pipeline with no forwarding or hazard detection? Show where the NOPs could be inserted.

4.26.3 [10] <§4.7> Analyzing each instruction independently will over-count the number of NOPs needed to run a program on a pipeline with no forwarding or hazard detection. Write a sequence of three assembly instructions so that, when you consider each instruction in the sequence independently, the sum of the stalls is larger than the number of stalls the sequence actually needs to avoid data hazards.

4.26.4 [5] <§4.7> Assuming no other hazards, what is the CPI for the program described by the table above when run on a pipeline with no forwarding? What percent of cycles are stalls? (For simplicity, assume that all necessary cases are listed above and can be treated independently.)

4.26.5 [5] <§4.7> What is the CPI if we use full forwarding (forward all results that can be forwarded)? What percent of cycles are stalls?

4.26.6 [10] <§4.7> Let us assume that we cannot afford to have three-input multiplexors that are needed for full forwarding. We have to decide if it is better to forward only from the EX/MEM pipeline register (next-cycle forwarding) or only from the MEM/WB pipeline register (two-cycle forwarding). What is the CPI for each option?

4.26.7 [5] <§4.7> For the given hazard probabilities and pipeline stage latencies, what is the speedup achieved by each type of forwarding (EX/MEM, MEM/WB, for full) as compared to a pipeline that has no forwarding?

4.26.8 [5] <§4.7> What would be the additional speedup (relative to the fastest processor from 4.26.7) be if we added “time-travel” forwarding that eliminates all data hazards? Assume that the yet-to-be-invented time-travel circuitry adds 100ps to the latency of the full-forwarding EX stage.

4.26.9 [5] <§4.7> The table of hazard types has separate entries for “EX to 1st” and “EX to 1st and EX to 2nd”. Why is there no entry for “MEM to 1st and MEM to 2nd”?

4.27 Problems in this exercise refer to the following sequence of instructions, and assume that it is executed on a five-stage pipelined datapath:

```
add  x15, x12, x11
ld   x13, 4(x15)
ld   x12, 0(x2)
or   x13, x15, x13
sd   x13, 0(x15)
```

4.27.1 [5] <§4.7> If there is no forwarding or hazard detection, insert NOPs to ensure correct execution.

4.27.2 [10] <§4.7> Now, change and/or rearrange the code to minimize the number of NOPs needed. You can assume register x17 can be used to hold temporary values in your modified code.

4.27.3 [10] <§4.7> If the processor has forwarding, but we forgot to implement the hazard detection unit, what happens when the original code executes?

4.27.4 [20] <§4.7> If there is forwarding, for the first seven cycles during the execution of this code, specify which signals are asserted in each cycle by hazard detection and forwarding units in [Figure 4.59](#).

4.27.5 [10] <§4.7> If there is no forwarding, what new input and output signals do we need for the hazard detection unit in [Figure 4.59](#)? Using this instruction sequence as an example, explain why each signal is needed.

4.27.6 [20] <§4.7> For the new hazard detection unit from 4.26.5, specify which output signals it asserts in each of the first five cycles during the execution of this code.

4.28 The importance of having a good branch predictor depends on how often conditional branches are executed. Together with branch predictor accuracy, this will determine how much time is spent stalling due to mispredicted branches. In this exercise, assume that the breakdown of dynamic instructions into various instruction categories is as follows:

R-type	beqz/bnez	jal	ld	sd
40%	25%	5%	25%	5%

Also, assume the following branch predictor accuracies:

Always-Taken	Always-Not-Taken	2-Bit
45%	55%	85%

4.28.1 [10] <\$4.8> Stall cycles due to mispredicted branches increase the CPI. What is the extra CPI due to mispredicted branches with the always-taken predictor? Assume that branch outcomes are determined in the ID stage and applied in the EX stage that there are no data hazards, and that no delay slots are used.

4.28.2 [10] <\$4.8> Repeat 4.28.1 for the “always-not-taken” predictor.

4.28.3 [10] <\$4.8> Repeat 4.28.1 for the 2-bit predictor.

4.28.4 [10] <\$4.8> With the 2-bit predictor, what speedup would be achieved if we could convert half of the branch instructions to some ALU instruction? Assume that correctly and incorrectly predicted instructions have the same chance of being replaced.

4.28.5 [10] <\$4.8> With the 2-bit predictor, what speedup would be achieved if we could convert half of the branch instructions in a way that replaced each branch instruction with two ALU instructions? Assume that correctly and incorrectly predicted instructions have the same chance of being replaced.

4.28.6 [10] <\$4.8> Some branch instructions are much more predictable than others. If we know that 80% of all executed branch instructions are easy-to-predict loop-back branches that are always predicted correctly, what is the accuracy of the 2-bit predictor on the remaining 20% of the branch instructions?

4.29 This exercise examines the accuracy of various branch predictors for the following repeating pattern (e.g., in a loop) of branch outcomes: T, NT, T, T, NT.

4.29.1 [5] <\$4.8> What is the accuracy of always-taken and always-not-taken predictors for this sequence of branch outcomes?

4.29.2 [5] <\$4.8> What is the accuracy of the 2-bit predictor for the first four branches in this pattern, assuming that the predictor starts off in the bottom left state from [Figure 4.61](#) (predict not taken)?

4.29.3 [10] <\$4.8> What is the accuracy of the 2-bit predictor if this pattern is repeated forever?

4.29.4 [30] <\$4.8> Design a predictor that would achieve a perfect accuracy if this pattern is repeated forever. Your predictor should be a sequential circuit with one output that provides a prediction (1 for taken, 0 for not taken) and no inputs other than the clock and the control signal that indicates that the instruction is a conditional branch.

4.29.5 [10] <§4.8> What is the accuracy of your predictor from 4.29.4 if it is given a repeating pattern that is the exact opposite of this one?

4.29.6 [20] <§4.8> Repeat 4.29.4, but now your predictor should be able to eventually (after a warm-up period during which it can make wrong predictions) start perfectly predicting both this pattern and its opposite. Your predictor should have an input that tells it what the real outcome was. Hint: this input lets your predictor determine which of the two repeating patterns it is given.

4.30 This exercise explores how exception handling affects pipeline design. The first three problems in this exercise refer to the following two instructions:

Instruction 1	Instruction 2
beqz x11, LABEL	ld x11, 0(x12)

4.30.1 [5] <§4.9> Which exceptions can each of these instructions trigger? For each of these exceptions, specify the pipeline stage in which it is detected.

4.30.2 [10] <§4.9> If there is a separate handler address for each exception, show how the pipeline organization must be changed to be able to handle this exception. You can assume that the addresses of these handlers are known when the processor is designed.

4.30.3 [10] <§4.9> If the second instruction is fetched immediately after the first instruction, describe what happens in the pipeline when the first instruction causes the first exception you listed in Exercise 4.30.1. Show the pipeline execution diagram from the time the first instruction is fetched until the time the first instruction of the exception handler is completed.

4.30.4 [20] <§4.9> In vectored exception handling, the table of exception handler addresses is in data memory at a known (fixed) address. Change the pipeline to implement this exception handling mechanism. Repeat Exercise 4.30.3 using this modified pipeline and vectored exception handling.

4.30.5 [15] <§4.9> We want to emulate vectored exception handling (described in Exercise 4.30.4) on a machine that has only one fixed handler address. Write the code that should be at that fixed address. Hint: this code should identify the exception, get the right address from the exception vector table, and transfer execution to that handler.

4.31 In this exercise we compare the performance of 1-issue and 2-issue processors, taking into account program transformations that can be made to optimize for 2-issue execution. Problems in this exercise refer to the following loop (written in C):

```
for(i=0; i!=j; i+=2)
    b[i]=a[i]-a[i+1];
```

A compiler doing little or no optimization might produce the following RISC-V assembly code:

```

        li    x12, 0
        jal   ENT
TOP:    slli   x5, x12, 3
        add   x6, x10, x5
        ld    x7, 0(x6)
        ld    x29, 8(x6)
        sub   x30, x7, x29
        add   x31, x11, x5
        sd    x30, 0(x31)
        addi  x12, x12, 2
ENT:    bne    x12, x13, TOP
```

The code above uses the following registers:

i	j	a	b	Temporary values
x12	x13	x10	x11	x5–x7, x29–x31

Assume the two-issue, statically scheduled processor for this exercise has the following properties:

- 1. One instruction must be a memory operation; the other must be an arithmetic/logic instruction or a branch.
- 2. The processor has all possible forwarding paths between stages (including paths to the ID stage for branch resolution).
- 3. The processor has perfect branch prediction.
- 4. Two instruction may not issue together in a packet if one depends on the other. (See page 324.)
- 5. If a stall is necessary, both instructions in the issue packet must stall. (See page 324.)

As you complete these exercises, notice how much effort goes into generating code that will produce a near-optimal speedup.

4.31.1 [30] <§4.10> Draw a pipeline diagram showing how RISC-V code given above executes on the two-issue processor. Assume that the loop exits after two iterations.

4.31.2 [10] <§4.10> What is the speedup of going from a one-issue to a two-issue processor? (Assume the loop runs thousands of iterations.)

4.31.3 [10] <§4.10> Rearrange/rewrite the RISC-V code given above to achieve better performance on the one-issue processor. Hint: Use the instruction “beqz x13,DONE” to skip the loop entirely if j = 0.

4.31.4 [20] <§4.10> Rearrange/rewrite the RISC-V code given above to achieve better performance on the two-issue processor. (Do not unroll the loop, however.)

4.31.5 [30] <§4.10> Repeat Exercise 4.31.1, but this time use your optimized code from Exercise 4.31.4.

4.31.6 [10] <§4.10> What is the speedup of going from a one-issue processor to a two-issue processor when running the optimized code from Exercises 4.31.3 and 4.31.4.

4.31.7 [10] <§4.10> Unroll the RISC-V code from Exercise 4.31.3 so that each iteration of the unrolled loop handles two iterations of the original loop. Then, rearrange/rewrite your unrolled code to achieve better performance on the one-issue processor. You may assume that j is a multiple of 4.

4.31.8 [20] <§4.10> Unroll the RISC-V code from Exercise 4.31.4 so that each iteration of the unrolled loop handles two iterations of the original loop. Then, rearrange/rewrite your unrolled code to achieve better performance on the two-issue processor. You may assume that j is a multiple of 4. (Hint: Re-organize the loop so that some calculations appear both outside the loop and at the end of the loop. You may assume that the values in temporary registers are not needed after the loop.)

4.31.9 [10] <§4.10> What is the speedup of going from a one-issue processor to a two-issue processor when running the unrolled, optimized code from Exercises 4.31.7 and 4.31.8?

4.31.10 [30] <§4.10> Repeat Exercises 4.31.8 and 4.31.9, but this time assume the two-issue processor can run two arithmetic/logic instructions together. (In other words, the first instruction in a packet can be any type of instruction, but the second must be an arithmetic or logic instruction. Two memory operations cannot be scheduled at the same time.)

4.32 This exercise explores energy efficiency and its relationship with performance. Problems in this exercise assume the following energy consumption for activity in Instruction memory, Registers, and Data memory. You can assume that the other components of the datapath consume a negligible amount of energy. (“Register Read” and “Register Write” refer to the register file only.)

I-Mem	1 Register Read	Register Write	D-Mem Read	D-Mem Write
140pJ	70pJ	60pJ	140pJ	120pJ

Assume that components in the datapath have the following latencies. You can assume that the other components of the datapath have negligible latencies.

I-Mem	Control	Register Read or Write	ALU	D-Mem Read or Write
200ps	150ps	90ps	90ps	250ps

4.32.1 [5] <§§4.3, 4.6, 4.14> How much energy is spent to execute an `add` instruction in a single-cycle design and in the five-stage pipelined design?

4.32.2 [10] <§§4.6, 4.14> What is the worst-case RISC-V instruction in terms of energy consumption? What is the energy spent to execute it?

4.32.3 [10] <§§4.6, 4.14> If energy reduction is paramount, how would you change the pipelined design? What is the percentage reduction in the energy spent by an `ld` instruction after this change?

4.32.4 [10] <§§4.6, 4.14> What other instructions can potentially benefit from the change discussed in Exercise 4.32.3?

4.32.5 [10] <§§4.6, 4.14> How do your changes from Exercise 4.32.3 affect the performance of a pipelined CPU?

4.32.6 [10] <§§4.6, 4.14> We can eliminate the `MemRead` control signal and have the data memory be read in every cycle, i.e., we can permanently have `MemRead=1`. Explain why the processor still functions correctly after this change. If 25% of instructions are loads, what is the effect of this change on clock frequency and energy consumption?

4.33 When silicon chips are fabricated, defects in materials (e.g., silicon) and manufacturing errors can result in defective circuits. A very common defect is for one wire to affect the signal in another. This is called a “cross-talk fault”. A special class of cross-talk faults is when a signal is connected to a wire that has a constant logical value (e.g., a power supply wire). These faults, where the affected signal always has a logical value of either 0 or 1 are called “stuck-at-0” or “stuck-at-1” faults. The following problems refer to bit 0 of the Write Register input on the register file in [Figure 4.21](#).

4.33.1 [10] <§§4.3, 4.4> Let us assume that processor testing is done by (1) filling the PC, registers, and data and instruction memories with some values (you can choose which values), (2) letting a single instruction execute, then (3) reading the PC, memories, and registers. These values are then examined to determine if a particular fault is present. Can you design a test (values for PC, memories, and registers) that would determine if there is a stuck-at-0 fault on this signal?

4.33.2 [10] <§§4.3, 4.4> Repeat Exercise 4.33.1 for a stuck-at-1 fault. Can you use a single test for both stuck-at-0 and stuck-at-1? If yes, explain how; if no, explain why not.

4.33.3 [10] <§§4.3, 4.4> If we know that the processor has a stuck-at-1 fault on this signal, is the processor still usable? To be usable, we must be able to convert any program that executes on a normal RISC-V processor into a program that works on this processor. You can assume that there is enough free instruction memory and data memory to let you make the program longer and store additional data.

4.33.4 [10] <§§4.3, 4.4> Repeat Exercise 4.33.1; but now the fault to test for is whether the MemRead control signal becomes 0 if the branch control signal is 0, no fault otherwise.

4.33.5 [10] <§§4.3, 4.4> Repeat Exercise 4.33.1; but now the fault to test for is whether the MemRead control signal becomes 1 if RegRd control signal is 1, no fault otherwise. Hint: This problem requires knowledge of operating systems. Consider what causes segmentation faults.

§4.1, page 240: 3 of 5: Control, Datapath, Memory. Input and Output are missing.
 §4.2, page 243: false. Edge-triggered state elements make simultaneous reading and writing both possible and unambiguous.
 §4.3, page 250: I. a. II. c.
 §4.4, page 262: Yes, Branch and ALUOp0 are identical. In addition, you can use the flexibility of the don't care bits to combine other signals together. ALUSrc and MemtoReg can be made the same by setting the two don't care bits of MemtoReg to 1 and 0. ALUOp1 and MemtoReg can be made to be inverses of one another by setting the don't care bit of MemtoReg to 1. You don't need an inverter; simply use the other signal and flip the order of the inputs to the MemtoReg multiplexor!
 §4.5, page 275: 1. Stall due to a load-use data hazard of the `ld` result. 2. Avoid stalling in the third instruction for the read-after-write data hazard on `x11` by forwarding the `add` result. 3. It need not stall, even without forwarding.
 §4.6, page 288: Statements 2 and 4 are correct; the rest are incorrect.
 §4.8, page 314: 1. Predict not taken. 2. Predict taken. 3. Dynamic prediction.
 §4.9, page 321: The first instruction, since it is logically executed before the others.
 §4.10, page 334: 1. Both. 2. Both. 3. Software. 4. Hardware. 5. Hardware. 6. Hardware. 7. Both. 8. Hardware. 9. Both.
 §4.12, page 344: First two are false and the last two are true.

**Answers to
Check Yourself**